


# SOLUTION 8B.3

1. • T+ Gates: CIRCUIT IN LECTURE 16, LAST SLIDE  
(4p) (or equivalent)

• Domino:

$$C_0 = AB + BC_i + AC_i$$
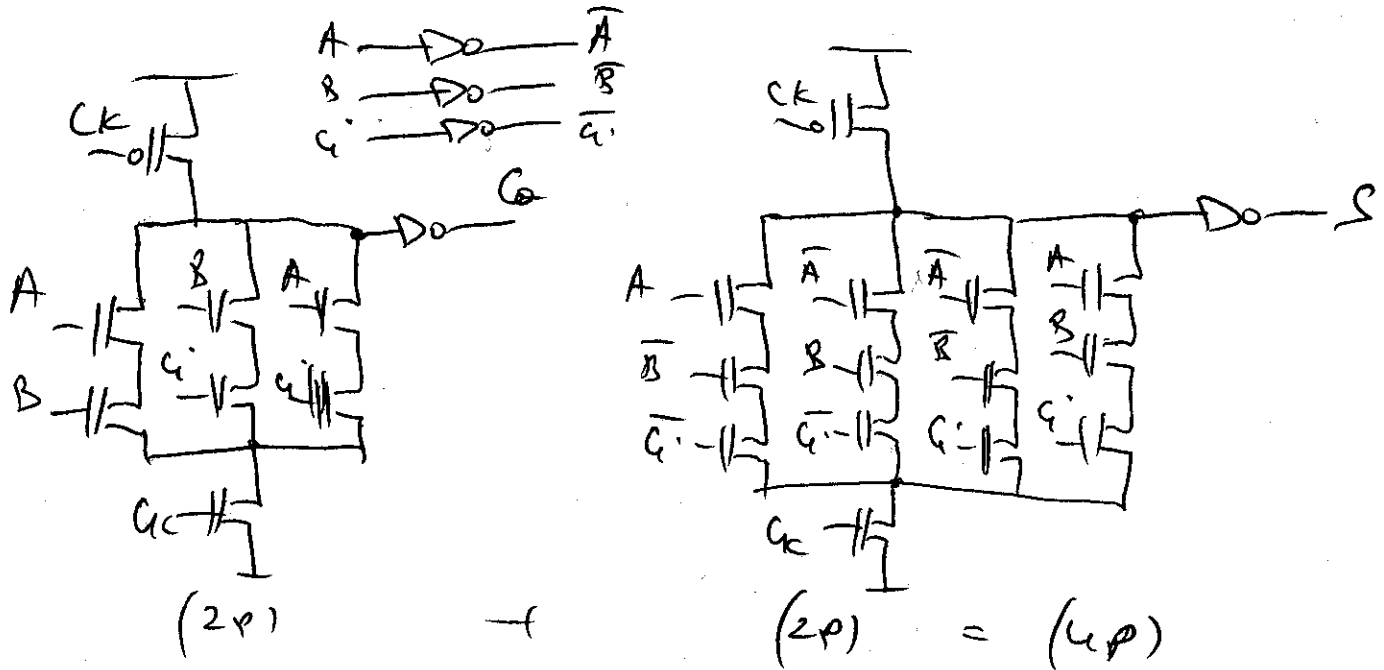
$$S = A \oplus B \oplus C_i = A\bar{B}\bar{C}_i + \bar{A}BC_i + \bar{A}\bar{B}C_i + ABC_i$$



Other solutions are possible.

NOTE: 1p/4p if your circuit contains illegal connections.

b) (4p) 1. XOR is difficult to implement in domino and cannot guarantee monotonicity.

( $\Rightarrow$  need multiple clocks to implement!)

(2p) 2. Multiple paths with unequal lengths  $\Rightarrow$  glitching  $\rightarrow$  fatal for dynamic gates

NOTE // Half credit for: ~~power~~ power, need to distribute clocks etc.  
 $\rightarrow$  No credit for: area, number of transistors, etc.