
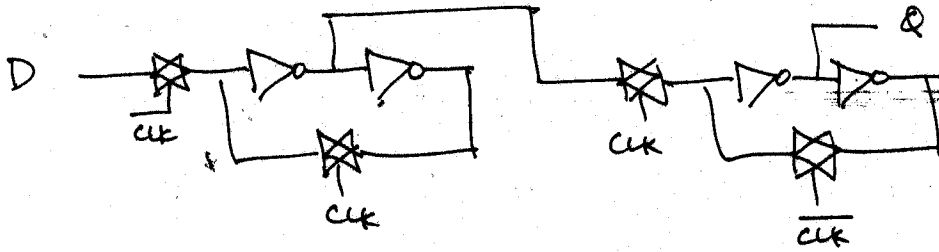


Part 1:

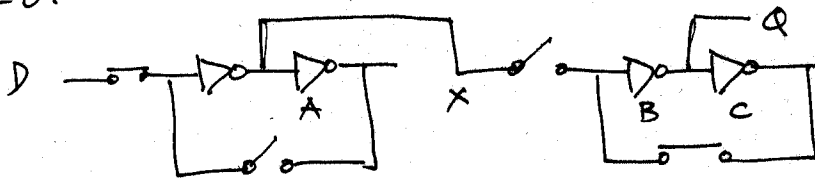


CLK=0:



D is sampled into node X and the previous value is held in Q.

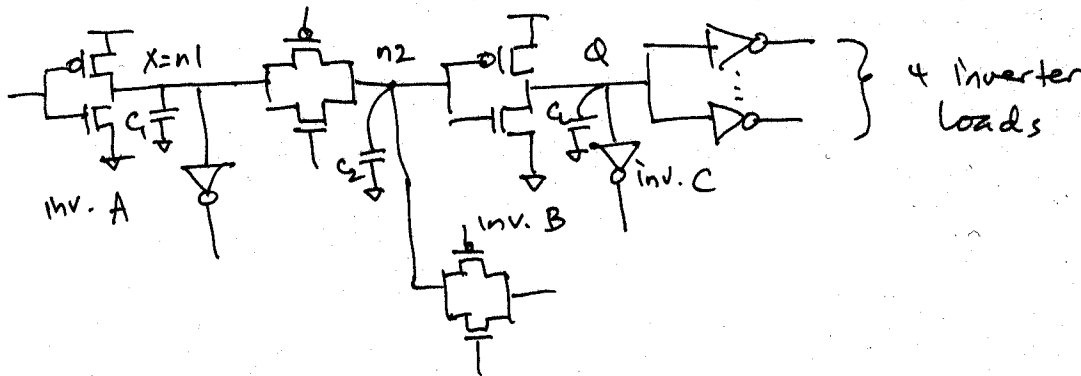At the rising edge of the clock (CLK), X is isolated from the input D, and is stored in the slave latch. Thus, t_{clk-Q} is the time it takes for X to propagate to Q.



Since X (or n1) is already charged to the input value, the only capacitances we need to consider are C_2 and C_L .

$$C_2 = 0.8 \text{ fF} + 2(0.52 \text{ fF}) = 1.84 \text{ fF}$$

$$C_L = 0.52 \text{ fF} + 5(0.8 \text{ fF}) = 4.52 \text{ fF}$$

note: $C_{int, inv} = 0.52 \text{ fF}$
 $C_{a, inv} = 0.8 \text{ fF}$
 $R_{eq, ave} = 15 \text{ k}\Omega$
 (min nmos)


$$t_{p, LUT} = t_{p, HL} = t_{clk-Q, ave} = \ln(2) \left[R + \frac{R}{2} \right] C_2 + \ln(2) R C_L$$

$$= \ln(2) \frac{3}{2} (15 \text{ k}\Omega) (1.84 \text{ fF}) + \ln(2) (15 \text{ k}\Omega) (4.52 \text{ fF})$$

$$= 76 \text{ ps}$$

From simulations: $t_{clk-Q, HL} = \frac{67 \text{ ps}}{80 \text{ ps}}$, $t_{clk-Q, HL} = \frac{69 \text{ ps}}{69 \text{ ps}}$
 $t_{clk-Q, ave} = \frac{68 \text{ ps}}{68 \text{ ps}}$

Part 2:

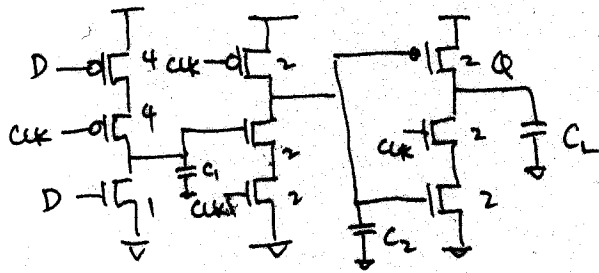

note:

- $C_{jn} = 0.17 \text{ fF}$ ($w=1$)
- $C_{jp} = 0.35 \text{ fF}$ ($w=2$)
- ~~$C_{jn} = 0.27 \text{ fF}$ ($w=1$)~~
- $C_{jp} = 0.53 \text{ fF}$ ($w=2$)
- $R_{eq} = 15 \text{ k}\Omega$ ($n, w=1$)


node capacitances:

$$C_1 = 2(0.35)(2) + 2(0.53) = 2.46 \text{ fF}$$

$$C_2 = 2(0.17) + 0.35 + 0.53 + 2(0.27) = 1.76 \text{ fF}$$


$$C_L = 0.35 + 2(0.17) + 4(0.5) = 3.89 \text{ fF}$$

when $clk = 0$:

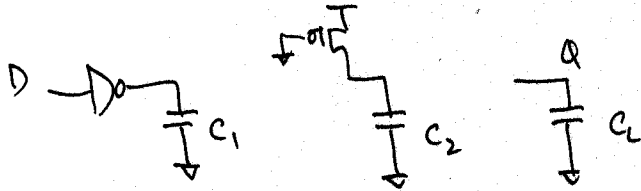

D is sampled onto C_1
 C_2 is precharged to V_{DD}
 C_L maintains previous value of Q

when $clk = 0 \rightarrow 1$:

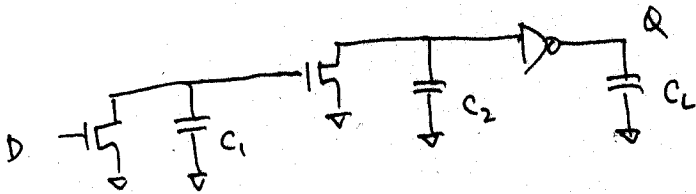

Depending on the value of C_1 ,
the output Q changes accordingly.

the clock-to-Q delay is the time needed to charge/discharge C_2 and C_L (low to high transition) or C_L (high to low transition)

$$t_{clk \rightarrow Q_{HH}} = (\ln 2)(15 \text{ k}\Omega)(1.76 \text{ fF}) + (\ln 2)(15 \text{ k}\Omega)(3.89 \text{ fF}) = 58.7 \text{ ps}$$


$$t_{clk \rightarrow Q_{HL}} = (\ln 2)(15 \text{ k}\Omega)(3.89 \text{ fF}) = 40.4 \text{ ps}$$

Simulation results:

$$t_{clk \rightarrow Q_{HH}} = 58.16 \text{ ps}$$

$$t_{clk \rightarrow Q_{HL}} = 24.35 \text{ ps}$$

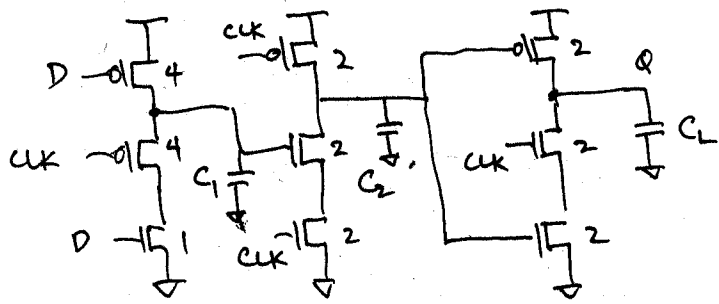Part 2: (alternate solution if you used the det. below)



note: $C_{j\text{unit}} = \frac{0.52}{3} = 0.17 \text{ fF}$

$C_{jp\text{unit}} = 0.35 \text{ fF}$

$C_{gn\text{unit}} = \frac{0.8}{3} = 0.27 \text{ fF}$

$C_{gp\text{unit}} = 0.53 \text{ fF}$

unit nmos = 1/2 unit pmos size

$R_{eq\text{unit}} = 15 \text{ k}\Omega$


Estimate the node capacitances:

$C_1 = 2(0.35)2 + 2(0.53) = 2.46 \text{ fF}$

$C_2 = 2(0.17) + 0.35 + 0.53 + 2(0.27) = 1.76 \text{ fF}$


$C_L = 0.35 + 2(0.17) + 4(0.8) = 3.89 \text{ fF}$

when $clk = 0$:

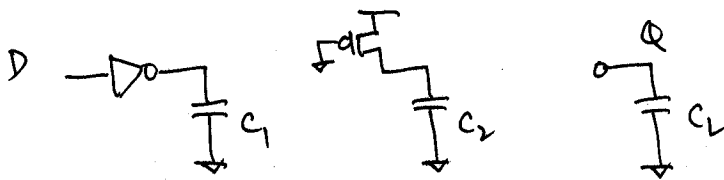

D is sampled on C_1 ,
 C_2 is pre-charged to V_{DD} ,
 C_L maintains previous value of Q .

when $clk: 0 \rightarrow 1$:

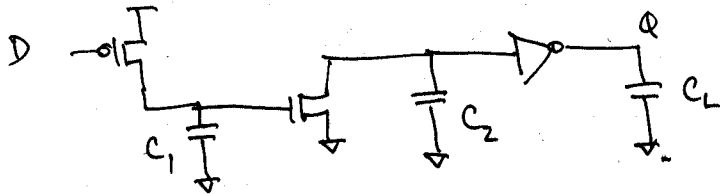

Depending on the value stored on C_1 , the output Q changes.

the clock-to-Q delay is the time needed to charge/discharge C_2 and C_L (low to high transition) or C_L (high to low transition).

$t_{clk-Q_{LH}} = \ln(2)(15 \text{ k}\Omega)(1.76 \text{ fF}) + \ln(2)(15 \text{ k}\Omega)(3.89 \text{ fF}) = 58.7 \text{ ps}$

$t_{clk-Q_{HL}} = \ln(2)(15 \text{ k}\Omega)(3.89 \text{ fF}) = 40.4 \text{ ps}$



Simulation results:

$t_{clk-Q_{LH}} = 58.16 \text{ ps}$

$t_{clk-Q_{HL}} = 24.35 \text{ ps}$

Part 3:


Simplified schematic:

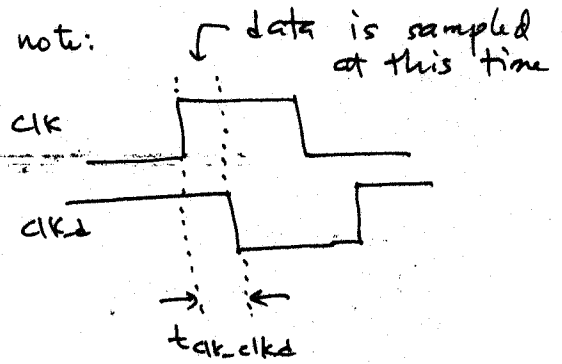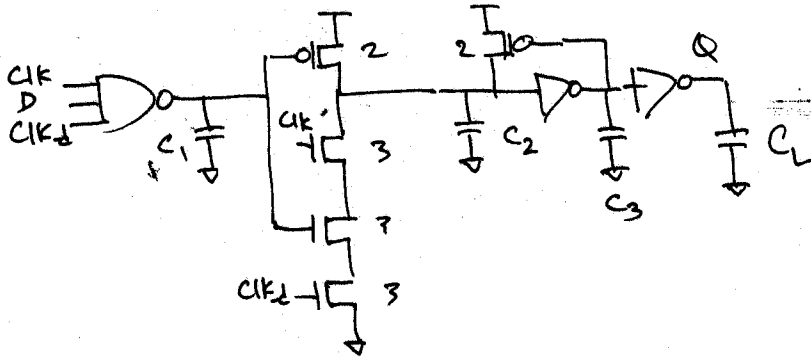

$$C_x = 6(0.27) + 0.53 + 0.52 = 2.67 \text{ fF}$$

$$t_{clk-clk-d} = \ln 2 (15k\Omega) (2.67 \text{ fF}) + 4 \ln 2 (15k) (1.32 \text{ fF}) = 82.6 \text{ ps}$$

For the L → H Q transition:

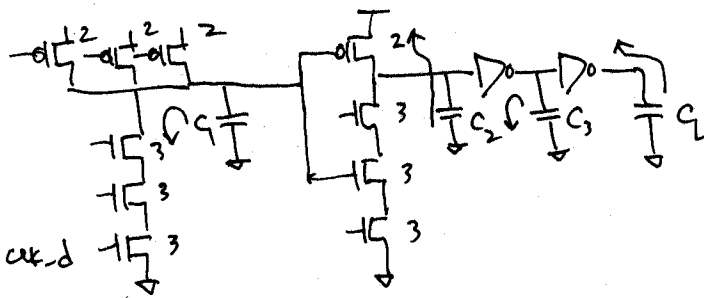

$$C_1 = 3(0.17) + 3(0.35) + 0.53 + 3(0.27) = 2.9 \text{ fF}$$

$$C_2 = 3(0.17) + 0.35 + 0.17 + 0.8 = 1.83 \text{ fF}$$


$$C_3 = 0.8 + 0.52 + 0.27 = 1.59 \text{ fF}$$

$$C_L = 0.52 + 4(0.8) = 3.72 \text{ fF}$$

$$t_{clk-d \text{ to } Q} = (\ln 2) (15k\Omega) [2.9 \text{ fF} + 1.83 \text{ fF} + 1.59 \text{ fF} + 3.72 \text{ fF}] = 104.4 \text{ ps}$$

$$t_{clk-Q} = 104.4 \text{ ps} + 82.6 \text{ ps} = 187 \text{ ps}$$

For the H → L Q transition:

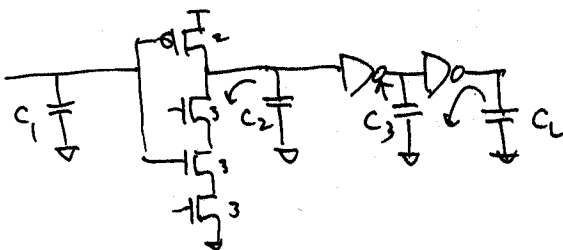

$$t_{clk-d \text{ to } Q} = (\ln 2) (15k\Omega) [1.83 + 1.59 + 3.72] = (\ln 2) (15k\Omega) (7.14 \text{ fF}) = 74.2 \text{ ps}$$

$$t_{clk-Q} = 74.2 \text{ ps} + 82.6 \text{ ps} = 156.8 \text{ ps}$$

Simulation results

$$t_{clk-Q_{LH}} = 102 \text{ ps}$$

$$t_{clk-Q_{HL}} = 65 \text{ ps}$$

Simulation Results

MS FF (part 1):

$$t_{su} = 51.4 \text{ ps}$$

$$t_{hold} = -4.95 \text{ ps}$$

TSPC (part 2)

$$t_{su} = 37.5 \text{ ps}$$

$$t_{hold} = 20.6 \text{ ps}$$

Pulse-based FF (part 3)

$$t_{su} = 8.2 \text{ ps}$$

$$t_{hold} = 43.4 \text{ ps}$$