

Digital Integrated Circuits— A Design Perspective (2nd Ed)

Table of Contents

PREFACE

PART I. THE FOUNDATIONS

CHAPTER 1: INTRODUCTION

- 1.1 A Historical Perspective
- 1.2 Issues in Digital Integrated Circuit Design
- 1.3 Quality Metrics of a Digital Design
 - 1.3.1 Cost of an Integrated Circuit
 - 1.3.2 Functionality and Robustness
 - 1.3.3 Performance
 - 1.3.4 Power and Energy Consumption
- 1.4 Summary
- 1.5 To Probe Further

Chapter 2: THE MANUFACTURING PROCESS

- 2.1 Introduction
- 2.2 Manufacturing CMOS Integrated Circuits
 - 2.2.1 The Silicon Wafer
 - 2.2.2 Photolithography
 - 2.2.3 Some Recurring Process Steps
 - 2.2.4 Simplified CMOS Process Flow
- 2.3 Design Rules — The Contract between Designer and Process Engineer
- 2.4 Packaging Integrated Circuits
 - 2.4.1 Package Materials
 - 2.4.2 Interconnect Levels
 - 2.4.3 Thermal Considerations in Packaging

- 2.5 Perspective — Trends in Process Technology
 - 2.5.1 Short-Term Developments
 - 2.5.2 In the Longer Term
- 2.6 Summary
- 2.7 To Probe Further

DESIGN METHODOLOGY INSERT A: IC LAYOUT

CHAPTER 3: THE DEVICES

- 3.1 Introduction
- 3.2 The Diode
 - 3.2.1 A First Glance at the Diode — The Depletion Region
 - 3.2.2 Static Behavior
 - 3.2.3 Dynamic, or Transient, Behavior
 - 3.2.4 The Actual Diode—Secondary Effects
 - 3.2.5 The SPICE Diode Model
- 3.3 The MOS(FET) Transistor
 - 3.3.1 A First Glance at the Device
 - 3.3.2 The MOS Transistor under Static Conditions
 - 3.3.3 Dynamic Behavior
 - 3.3.4 The Actual MOS Transistor—Some Secondary Effects
 - 3.3.5 SPICE Models for the MOS Transistor
- 3.4 A Word on Process Variations
- 3.5 Perspective: Technology Scaling
- 3.6 Summary
- 3.7 To Probe Further

DESIGN METHODOLOGY INSERT B: CIRCUIT SIMULATION

CHAPTER 4: THE WIRE

- 4.1 Introduction
- 4.2 A First Glance
- 4.3 Interconnect Parameters — Capacitance, Resistance, and Inductance

- 4.3.1 Capacitance
- 4.3.2 Resistance
- 4.3.3 Inductance
- 4.4 Electrical Wire Models
 - 4.4.1 The Ideal Wire
 - 4.4.2 The Lumped Model
 - 4.4.3 The Lumped RC model
 - 4.4.4 The Distributed rc_{Line}
 - 4.4.5 The Transmission Line
- 4.5 SPICE Wire Models
 - 4.5.1 Distributed rc Lines in SPICE
 - 4.5.2 Transmission Line Models in SPICE
- 4.6 Perspective: A Look into the Future
- 4.7 Summary
- 4.8 To Probe Further

PART II. A CIRCUIT PERSPECTIVE

Chapter 5: THE CMOS INVERTER

- 5.1 Introduction
- 5.2 The Static CMOS Inverter — An Intuitive Perspective
- 5.3 Evaluating the Robustness of the CMOS Inverter: The Static Behavior
 - 5.3.1 Switching Threshold
 - 5.3.2 Noise Margins
 - 5.3.3 Robustness Revisited
- 5.4 Performance of CMOS Inverter: The Dynamic Behavior
 - 5.4.1 Computing the Capacitances
 - 5.4.2 Propagation Delay: First-Order Analysis
 - 5.4.3 Propagation Delay from a Design Perspective
- 5.5 Power, Energy, and Energy-Delay
 - 5.5.1 Dynamic Power Consumption
 - 5.5.2 Static Consumption
 - 5.5.3 Putting It All Together
 - 5.5.4 Analyzing Power Consumption Using SPICE

- 5.6 Perspective: Technology Scaling and its Impact on the Inverter Metrics
- 5.7 Summary
- 5.8 To Probe Further

CHAPTER 6: DESIGNING COMBINATIONAL LOGIC GATES IN CMOS

- 6.1 Introduction
- 6.2 Static CMOS Design
 - 6.2.1 Complementary CMOS
 - 6.2.2 Ratioed Logic
 - 6.2.3 Pass-Transistor Logic
- 6.3 Dynamic CMOS Design
 - 6.3.1 Dynamic Logic: Basic Principles
 - 6.3.2 Speed and Power Dissipation of Dynamic Logic
 - 6.3.3 Issues in Dynamic Design
 - 6.3.4 Cascading Dynamic Gates
- 6.4 Perspectives
 - 6.4.1 How to Choose a Logic Style?
 - 6.4.2 Designing Logic for Reduced Supply Voltages
- 6.5 Summary
- 6.6 To Probe Further

DESIGN METHODOLOGY INSERT C: HOW TO SIMULATE COMPLEX LOGIC GATES

- C.1 Representing Digital Data as a Continuous Entity
- C.2 Representing Data as a Discrete Entity
- C.3 Using Higher-Level Data Models
- C.4 To Probe Further

DESIGN METHODOLOGY INSERT D: LAYOUT TECHNIQUES FOR COMPLEX GATES

CHAPTER 7: DESIGNING SEQUENTIAL LOGIC CIRCUITS

- 7.1 Introduction
 - 7.1.1 Timing Metrics for Sequential Circuits
 - 7.1.2 Classification of Memory Elements
- 7.2 Static Latches and Registers
 - 7.2.1 The Bistability Principle
 - 7.2.2 Multiplexer-Based Latches
 - 7.2.3 Master-Slave Edge-Triggered Register
 - 7.2.4 Low-Voltage Static Latches
 - 7.2.5 Static SR Flip-Flops—Writing Data by Pure Force
- 7.3 Dynamic Latches and Registers
 - 7.3.1 Dynamic Transmission-Gate Edge-triggered Registers
 - 7.3.2 C2MOS—A Clock-Skew Insensitive Approach
 - 7.3.3 True Single-Phase Clocked Register (TSPCR)
- 7.4 Alternative Register Styles*
 - 7.4.1 Pulse Registers
 - 7.4.2 Sense-Amplifier Based Registers
- 7.5 Pipelining: An approach to optimize sequential circuits
 - 7.5.1 Latch- vs. Register-Based Pipelines
 - 7.5.2 NORA-CMOS—A Logic Style for Pipelined Structures
- 7.6 Non-Bistable Sequential Circuits
 - 7.6.1 The Schmitt Trigger
 - 7.6.2 Monostable Sequential Circuits
 - 7.6.3 Astable Circuits
- 7.7 Perspective: Choosing a Clocking Strategy
- 7.8 Summary
- 7.9 To Probe Further

PART III. A SYSTEM PERSPECTIVE

CHAPTER 8: IMPLEMENTATION STRATEGIES FOR DIGITAL ICS

- 8.1 Introduction
- 8.2 From Custom to Semicustom and Structured Array Design Approaches
- 8.3 Custom Circuit Design
- 8.4 Cell-Based Design Methodology
 - 8.4.1 Standard Cell
 - 8.4.2 Compiled Cells
 - 8.4.3 Macrocells, Megacells and Intellectual Property
 - 8.4.4 Semi-Custom Design Flow
- 8.5 Array-Based Implementation Approaches
 - 8.5.1 Pre-diffused (or Mask-Programmable) Arrays
 - 8.5.2 Pre-wired Arrays
- 8.6 Perspective—The Implementation Platform of the Future
- 8.7 Summary
- 8.8 To Probe Further

DESIGN METHODOLOGY INSERT E: CHARACTERIZING LOGIC AND SEQUENTIAL CELLS

DESIGN METHODOLOGY INSERT F: DESIGN SYNTHESIS

CHAPTER 9: COPING WITH INTERCONNECT

- 9.1 Introduction
- 9.2 Capacitive Parasitics
 - 9.2.1 Capacitance and Reliability—Cross Talk
 - 9.2.2 Capacitance and Performance in CMOS
- 9.3 Resistive Parasitics
 - 9.3.1 Resistance and Reliability—Ohmic Voltage Drop
 - 9.3.2 Electromigration
 - 9.3.3 Resistance and Performance—RC Delay
- 9.4 Inductive Parasitics

- 9.4.1 Inductance and Reliability— Voltage Drop
- 9.4.2 Inductance and Performance—Transmission Line Effects
- 9.5 Advanced Interconnect Techniques
 - 9.5.1 Reduced-Swing Circuits
 - 9.5.2 Current-Mode Transmission Techniques
- 9.6 Perspective: Networks-on-a-Chip
- 9.7 Chapter Summary
- 9.8 To Probe Further

CHAPTER 10: TIMING ISSUES IN DIGITAL CIRCUITS

- 10.1 Introduction
- 10.2 Timing Classification of Digital Systems
 - 10.2.1 Synchronous Interconnect
 - 10.2.2 Mesochronous interconnect
 - 10.2.3 Plesiochronous Interconnect
 - 10.2.4 Asynchronous Interconnect⁹
 - 10.3 Synchronous Design — An In-depth Perspective
 - 10.3.1 Synchronous Timing Basics
 - 10.3.2 Sources of Skew and Jitter
 - 10.3.3 Clock-Distribution Techniques
 - 10.3.4 Latch-Based Clocking *
 - 10.4 Self-Timed Circuit Design*
 - 10.4.1 Self-Timed Logic - An Asynchronous Technique
 - 10.4.2 Completion-Signal Generation
 - 10.4.3 Self-Timed Signaling
 - 10.4.4 Practical Examples of Self-Timed Logic
 - 10.5 Synchronizers and Arbiters*
 - 10.5.1 Synchronizers—Concept and Implementation
 - 10.5.2 Arbiters
 - 10.6 Clock Synthesis and Synchronization Using a Phase-Locked Loop
 - 10.6.1 Basic Concept
 - 10.6.2 Building Blocks of a PLL
 - 10.7 Future Directions and Perspectives
 - 10.7.1 Distributed Clocking Using DLLs

- 10.7.2 Optical Clock Distribution
- 10.7.3 Synchronous versus Asynchronous Design
- 10.8 Summary
- 10.9 To Probe Further

DESIGN METHODOLOGY INSERT G: DESIGN VERIFICATION

CHAPTER 11: DESIGNING ARITHMETIC BUILDING BLOCKS

- 11.1 Introduction
- 11.2 Datapaths in Digital Processor Architectures
- 11.3 The Adder
 - 11.3.1 The Binary Adder: Definitions
 - 11.3.2 The Full Adder: Circuit Design Considerations
 - 11.3.3 The Binary Adder: Logic Design Considerations
- 11.4 The Multiplier
 - 11.4.1 The Multiplier: Definitions
 - 11.4.2 Partial-Product Generation
 - 11.4.3 Partial Product Accumulation
 - 11.4.4 Final Addition
 - 11.4.5 Multiplier Summary
- 11.5 The Shifter
 - 11.5.1 Barrel Shifter
 - 11.5.2 Logarithmic Shifter
- 11.6 Other Arithmetic Operators
- 11.7 Power and Speed Trade-off's in Datapath Structures
 - 11.7.1 Design Time Power-Reduction Techniques
 - 11.7.2 Run-Time Power Management
 - 11.7.3 Reducing the Power in Standby (or Sleep) Mode
- 11.8 Perspective: Design as a Trade-off
- 11.9 Summary
- 11.10 To Probe Further

CHAPTER 12: DESIGNING MEMORY AND ARRAY STRUCTURES

- 12.1 Introduction
 - 12.1.1 Memory Classification
 - 12.1.2 Memory Architectures and Building Blocks
- 12.2 The Memory Core
 - 12.2.1 Read-Only Memories
 - 12.2.2 Nonvolatile Read-Write Memories
 - 12.2.3 Read-Write Memories (RAM)
 - 12.2.4 Contents-Addressable or Associative Memory (CAM)
- 12.3 Memory Peripheral Circuitry
 - 12.3.1 The Address Decoders
 - 12.3.2 Sense Amplifiers
 - 12.3.3 Voltage References
 - 12.3.4 Drivers/Buffers
 - 12.3.5 Timing and Control
- 12.4 Memory Reliability and Yield
 - 12.4.1 Signal-To-Noise Ratio
 - 12.4.2 Memory yield
- 12.5 Power Dissipation in Memories
 - 12.5.1 Sources of Power Dissipation in Memories
 - 12.5.2 Partitioning of the memory
 - 12.5.3 Addressing the Active Power Dissipation
 - 12.5.4 Data-retention dissipation
 - 12.5.5 Summary
- 12.6 Case Studies in Memory Design
 - 12.6.1 The Programmable Logic Array (PLA)
 - 12.6.2 A 4 Mbit SRAM
 - 12.6.3 A 1 Gbit NAND Flash Memory
- 12.7 Perspective: Semiconductor Memory Trends and Evolutions
- 12.8 Summary
- 12.9 To Probe Further

DESIGN METHODOLOGY INSERT H: VALIDATION AND TEST OF MANUFACTURED CIRCUITS

- H.1 Introduction
- H.2 Test Procedure
- H.3 Design for Testability
 - H.3.1 Issues in Design for Testability
 - H.3.2 Ad Hoc Testing
 - H.3.3 Scan-Based Test
 - H.3.4 Boundary-Scan Design
 - H.3.5 Built-in Self-Test (BIST)
- H.4 Test-Pattern Generation
 - H.4.1 Fault Models
 - H.4.2 Automatic Test-Pattern Generation (ATPG)
 - H.4.3 Fault Simulation
- H.5 To Probe Further

INDEX