

UNIVERSITY OF CALIFORNIA AT BERKELEY
College of Engineering
Department of Electrical Engineering and Computer Science

R. W. Brodersen
Johan Vanderhaegen

Homework #2
(Due 9/9/02)

EECS 140
Fall 2002

- 1) Consider the structure shown in figure 1. Determine I_{DS} as a function of V_{GS} and V_{DS} . This structure is equivalent to a single transistor having a different W/L ratio (than the W/L ratio of the individual transistors). Find the W/L ratio and show that this is true. Assume $\gamma = \lambda = 0$.

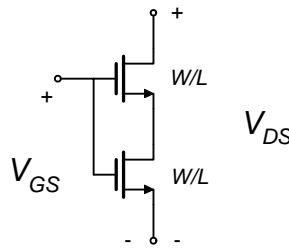


Figure 1.

- 2) Sketch I_{DS} for M1 from the circuit shown in figure 2 as a function of V_{in} as V_{in} varies from 0 to V_{DD} . Indicate and calculate all the breakpoints (the values of V_{in} and I_{DS}) where the transistor changes region of operation. Do not solve for the exact $I_{DS}-V_{in}$ curve, but indicate whether and explain why the different parts of the curve are approximately a constant, linear or quadratic function of V_{in} . Assume $V_{T0} = 0.5$ V, $k'W/L = 8$ mA/V², $\gamma = \lambda = 0$, $V_{DD} = 3$ V, $I1 = 4$ mA, $R1 = 1$ k Ω .

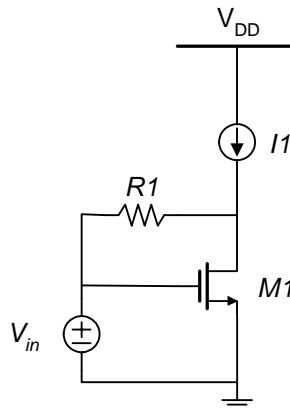


Figure 2.

- 3) For each of the two circuits figure 3, perform the calculations a and b by hand.
 Assume $V_{T0} = 0.5 \text{ V}$, $k'W/L = 4 \text{ mA/V}^2$, $\gamma = 0.5 \text{ V}^{1/2}$, $\lambda = 0.25 \text{ V}^{-1}$,
 $R1 = 1 \text{ k}\Omega$, $R2 = 300 \Omega$, $V_{DD} = 3$.
- Determine the dc voltage V_{IN} , so that the output V_{OUT} is at 1.5 V. Assume that V_{IN} is between 0 and V_{DD} .
 - Calculate the operating point parameters I_{DS} , V_T and V_{DSAT} and the small signal device parameters g_m , g_{mbs} and r_o .

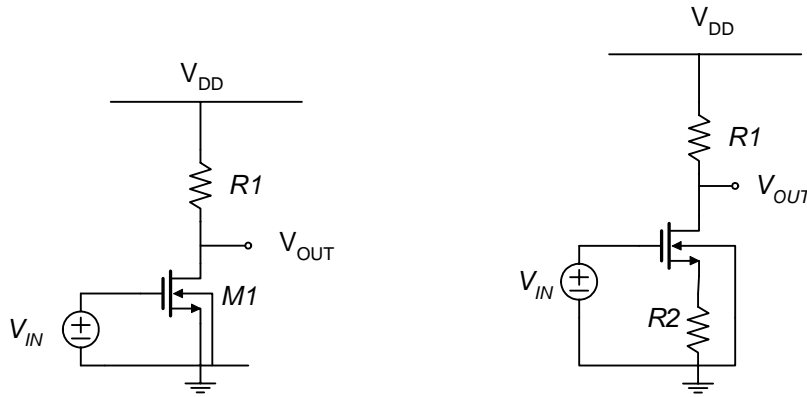


Figure 3.