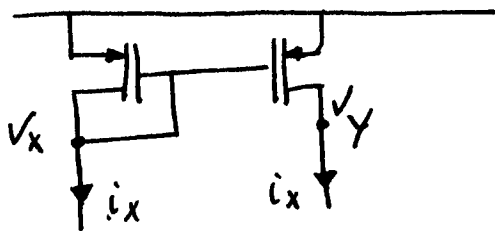


HOMEWORK #7 SOLUTION

- 1) • Even though the circuit topology is asymmetric, the circuit behaves symmetrically for a common mode input:




We will calculate the voltages v_x and v_y , and show that they are equal when we draw the same current i_x from both sides.

$$v_x = i_x \left[\frac{1}{g_m} \parallel r_o \right] = \frac{i_x r_o}{1 + g_m r_o}$$

(transistor on the left is diode-connected)

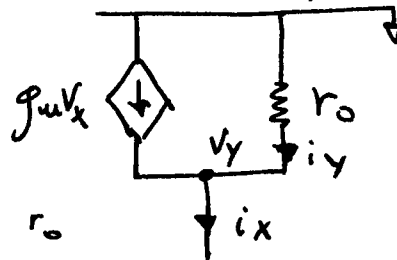Small signal equivalent circuit of the transistor on the right:




Let i_y be the current through r_o

$$\Rightarrow i_y = i_x - g_m v_x = \frac{i_x}{1 + g_m r_o}$$

$$\Rightarrow v_y = r_o i_y = \frac{i_x r_o}{1 + g_m r_o} = i_x \left[\frac{1}{g_m} \parallel r_o \right] = v_x$$


$$\Rightarrow \boxed{v_y = v_x}$$

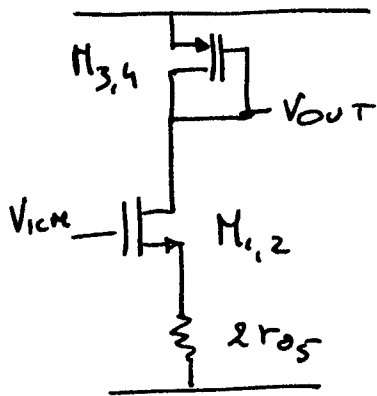- Since the circuit behaves symmetrically for common mode inputs, we can draw a common-mode half-circuit



$$A_{cm} = - \frac{g_{m_{1,2}}}{g_{m_{3,4}}} \cdot \frac{1}{1 + g_{m_{1,2}} \cdot 2r_{os}}$$

2) (a) Small signal equivalent circuit:

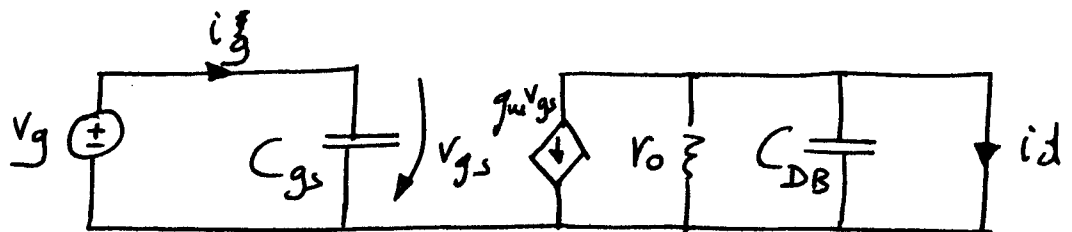

$$\left. \begin{aligned} i_g &= j\omega C_{gs} v_{gs} \\ i_d &= -g_m v_{gs} \end{aligned} \right\} \frac{i_d}{i_g} = \frac{-g_m}{j\omega C_{gs}}$$

$$\left| \frac{i_d}{i_g} \right| = \frac{g_m}{\omega C_{gs}} = \frac{g_m}{2\pi f C_{gs}} = 1 \iff \boxed{f_T = \frac{g_m}{2\pi C_{gs}}}$$

(Ignoring C_{gb} and C_{gd})

$$(b) \quad f_T = \frac{g_m}{2\pi C_{gs}} = \frac{\mu_n C_{ox} W/L (V_{GS} - V_T)}{2\pi \frac{2}{3} WL C_{ox}}$$

$$\Rightarrow \boxed{f_T = \frac{3}{4\pi} \frac{\mu_n (V_{GS} - V_T)}{L^2}}$$