

HOMEWORK # 8

SOLUTION

- 1) Time-constants associated with capacitors C_1 & C_2 , assuming the other capacitor behaves like an open circuit:

$$\tau = C \cdot \langle R \text{ seen by } C \rangle$$

$$\tau_1 = C_1 \cdot \frac{1}{g_{m2}}$$

$$\tau_2 = C_2 \cdot r_{o1} // r_{o2}$$

② $\tau_1 \gg \tau_2 \Rightarrow \boxed{\omega_{p1} = \frac{1}{\tau_1} = \frac{g_{m2}}{C_1}}$

Since this pole cuts off half of our current flowing to the output, there will also be a zero at twice the pole frequency:


$$i_{out, total} = \underbrace{\frac{i_d}{2}}_{\text{current through } M_{1b}} + \underbrace{\frac{i_d}{2} \cdot \frac{1}{1 + s\tau_1}}_{\text{current through } M_{1a} \text{ and mirror}}$$

$$= i_d \frac{1 + s\tau_1/2}{1 + s\tau_1} \quad \text{where } i_d = g_m V_{in}$$

$$\Rightarrow \boxed{\omega_z = \frac{2}{\tau_1} = \frac{2g_{m2}}{C_1}}$$

For $\omega \gg \omega_{p1}$, the current mirror is shorted out by C_1 and the impedance seen by C_2 becomes $r_{o2} \parallel 2r_{o1}$
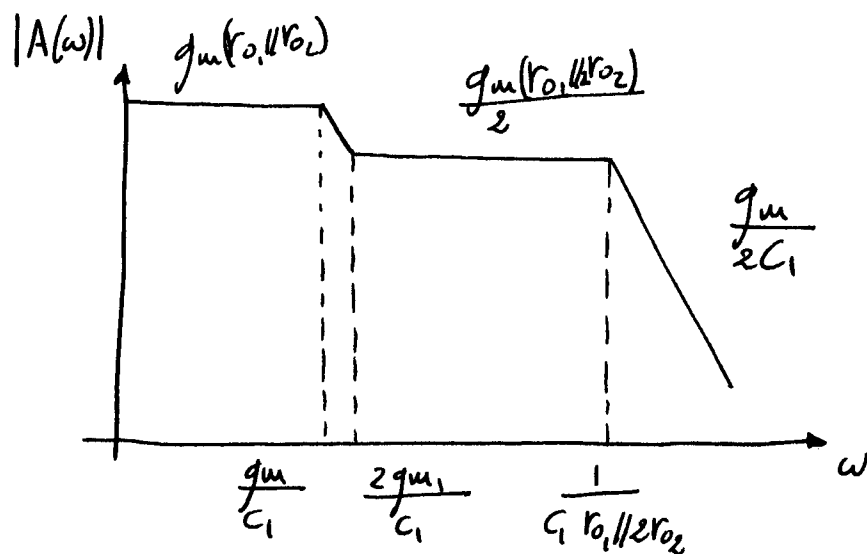
$$\Rightarrow \omega_{p2} = \frac{1}{C_1 (r_{o1} \parallel 2r_{o2})}$$




$$\textcircled{b} \quad z_2 \gg z_1 \Rightarrow \boxed{\omega_{p1} = \frac{1}{z_2} = \frac{1}{C_2 r_{o1} \parallel r_{o2}}}$$

Even for $\omega \gg \omega_{p1}$, when C_2 looks like a short, the resistance seen by C_1 is still $\frac{1}{g_{m2}}$

$$\Rightarrow \boxed{\omega_{p2} = \frac{1}{z_1} = \frac{g_{m2}}{C_1}}$$
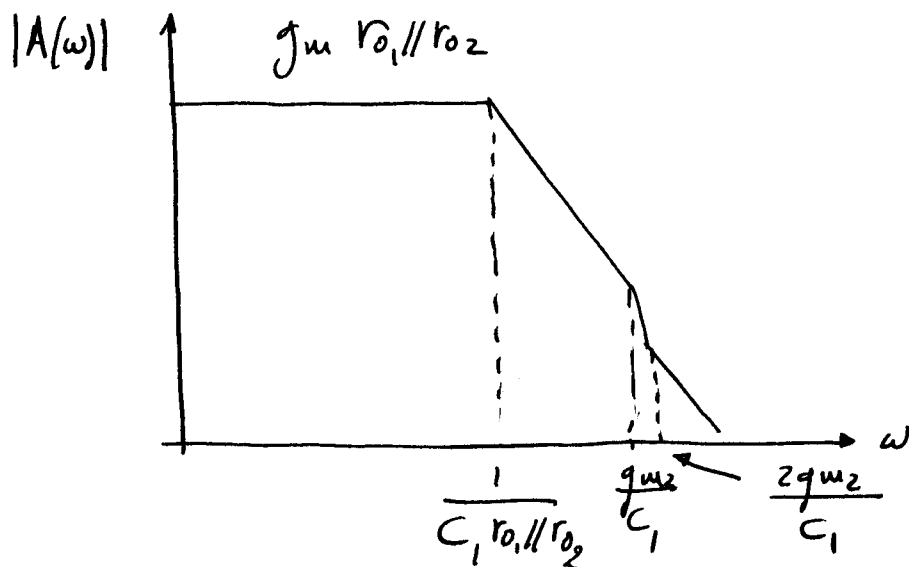
$$\boxed{\omega_z = \frac{2}{z_1} = \frac{2g_{m2}}{C_1}}$$



$$2) \text{ (a) } A_{dm} = -\frac{1}{2} g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{o1} \parallel r_{o2} \right) g_{m3} (R_D \parallel r_{o3})$$

$$V_{DSat1} \approx V_{DSat3} \approx \sqrt{\frac{2I_{D5}}{\mu_n' W/L_{eff}}} = \sqrt{\frac{2 \cdot 200 \mu A}{\frac{332 \mu A}{\sqrt{2}} \frac{4}{0.08}}} \approx 185 \text{ mV}$$

$$V_{DSat2} \approx \sqrt{\frac{2I_{D5}}{\mu_p' W/L_{eff}}} = \sqrt{\frac{2 \cdot 200 \mu A}{\frac{133 \mu A}{\sqrt{2}} \frac{4}{0.08}}} = 245 \text{ mV}$$

$$g_{m1} \approx g_{m3} \approx \frac{2I_{D5}}{V_{DSat1,3}} = 2.6 \text{ mS}$$



$$g_{m2} \approx \frac{2I_{D5}}{V_{DSat2}} = 1.6 \text{ mS}$$

$$r_{o1} \approx r_{o3} \approx \frac{1}{\lambda_n I_{D5}} = 25 \text{ k}\Omega$$

$$r_{o2} \approx \frac{1}{\lambda_p I_{D5}} = 33 \text{ k}\Omega$$

$$\Rightarrow A_{dm} = -6.9 \quad (\text{SPICE: } -6.7)$$

Differential mode half-circuit:

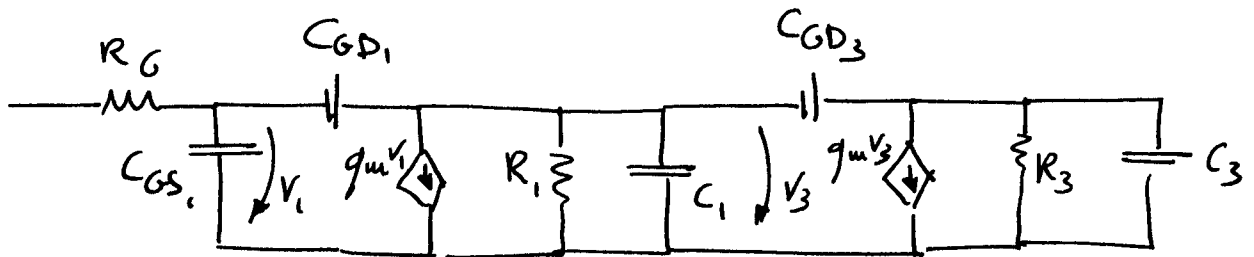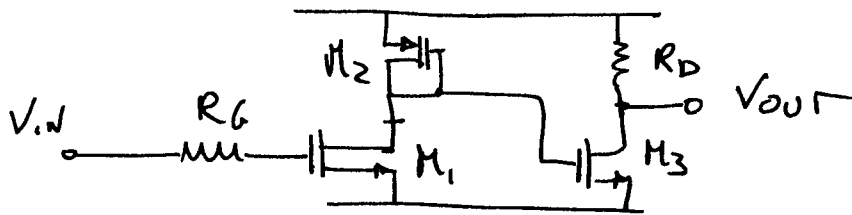

$$\text{where } R_1 = \frac{1}{g_{m2}} \parallel r_{o1} \parallel r_{o2} \approx 590 \Omega$$

$$R_3 = r_{o2} \parallel R_D = 3.4 \text{ k}\Omega$$

$$C_1 = C_{DB1} + C_{DB2} + C_{GS2} + C_{GS3}$$

Resistance seen by C_{GD1} :

$$R_{C_{GD1}} = R_G + R_1 + g_{m1} R_1 R_G = 3.1 \text{ k}\Omega$$

Resistance seen by C_{GD3} :

$$R_{C_{GD3}} = R_1 + R_3 + g_{m3} R_1 R_3 = 9.2 \text{ k}\Omega$$

$$C_{GS} = \frac{2}{3} W(L - 2L_D) C_{ox} + WL_D C_{ox} = 4.77 \text{ fF}$$

$$C_{GD} = WL_D C_{ox} = 1.33 \text{ fF}$$

$$\begin{aligned} V_{DB_1} &= V_{D_1} - V_{B_1} = (V_{DD} - V_{GS_2}) - (V_{IN,CH} - V_{GS_1}) \\ &= (1.2V - 300\text{mV} - 245\text{mV}) - (0.9V - 300\text{mV} - 155\text{mV}) \\ &= 210\text{mV} \end{aligned}$$

$$\begin{aligned} C_{DB_1} &= \frac{C_J \cdot W \cdot 2HDIF}{\left(1 + \frac{V_{DB_1}}{P_J}\right)^{m_j}} + \frac{C_{Jsw} \cdot (W + 4HDIF) + C_{JG} \cdot W}{\left(1 + \frac{V_{DB_1}}{P_{Jsw}}\right)^{m_{Jsw}}} \\ &= 1.47 \text{ fF} \end{aligned}$$

Similarly: $|V_{DB_2}| = |V_{GS_2}| = 545\text{mV}$

$$C_{DB_2} = 1.29\text{mV}$$

$$\begin{aligned} V_{DB_3} &= V_{D_3} - V_{B_3} = (V_{DD} - R_D \cdot I_{OS}) - (V_{DD} - V_{GS_2} - V_{GS_3}) \\ &\approx (1.2V - 0.8V) - (1.2V - 0.155V - 0.3V - 0.245V - 0.7V) \\ &= 0.4V - 0.2V \\ &= 200\text{mV} \approx V_{DB_1} \end{aligned}$$

$$\Rightarrow C_{DB_3} \approx C_{DB_1} = 1.47 \text{ fF}$$

$$\Rightarrow C_1 = C_{DB_1} + C_{DB_2} + C_{GS_2} + C_{GS_3} = 12.5 \text{ fF}$$

$$C_3 = C_{DB_3} = 1.47 \text{ fF}$$

$$\begin{aligned}
 \tau &= R_G C_{GS_1} + R_{C_{GD_1}} C_{GD_1} + R_1 C_1 + R_{C_{GD_3}} C_{GD_3} + R_3 R_3 \\
 &= 4.7 \text{ ps} + 4.1 \text{ ps} + 7.4 \text{ ps} + 12 \text{ ps} + 5 \text{ ps} \\
 &= 33 \text{ ps}
 \end{aligned}$$

(Note how the largest contribution is from C_{GD_3})

$$f_{3\text{db, estimate}} = \frac{1}{2\pi\tau} = 4.8 \text{ GHz}$$

ⓑ $f_{pd} = 7 \text{ GHz}$ → much larger than our estimate 3db frequency,

$$\text{but } \left(\sum_i f_{pd_i}^{-1} \right)^{-1} = 5 \text{ GHz}$$

↪ correct expression for $\frac{1}{2\pi\tau}$
(see book)

$$\text{Ⓒ } f_{3\text{db}} = 6.5 \text{ GHz}$$

(a little lower than f_{pd} due to relatively close non-dominant poles)

1 ***** Star-HSPICE -- 2001.4 (20011215) 11:07:34 11/03/2002 solari s

homework 8 - probl em 2

***** pole/zero analysi s

tnom= 25.000 temp= 25.000

input = 0: vdm

output = v(vo2b

input = 0: vdm

output = v(vo2b

poles (rad/sec)

poles (hertz)

real	i mag	real	i mag
-44.1440g	0.	-7.0257g	0.
-104.7433g	-73.6406g	-16.6704g	-11.7203g
-104.7433g	73.6406g	-16.6704g	11.7203g
-153.3417g	0.	-24.4051g	0.
-199.3073g	0.	-31.7207g	0.
-216.4428g	-147.4541g	-34.4479g	-23.4680g
-216.4428g	147.4541g	-34.4479g	23.4680g
-380.1907g	0.	-60.5092g	0.
-469.6599g	0.	-74.7487g	0.

zeros (rad/sec)

zeros (hertz)

real	i mag	real	i mag
-104.7433g	-73.6406g	-16.6704g	-11.7203g
-104.7433g	73.6406g	-16.6704g	11.7203g
-199.3073g	0.	-31.7207g	0.
-216.4428g	-147.4541g	-34.4479g	-23.4680g
-216.4428g	147.4541g	-34.4479g	23.4680g
-469.6599g	0.	-74.7487g	0.

***** constant factor = -1.728e+34

Opening plot unit= 15

file=probl em2. ac0

homework 8 - probl em 2

***** ac analysi s

tnom= 25.000 temp= 25.000

a0= 1.6544E+01

f3db= 6.4568E+09

***** job concl uded

Wave	Symbol
D0:A0:vdb(vo2)	⊗

homework 8 - problem 2

