

HOMEWORK # 9
 SOLUTION

General assumption: $RR \gg 1, T \gg 1$


1) (a) M_2 is the forward amplifier
 M_1 is the feedback element

(b) shunt-shunt feedback


shunt at the input : current summing
 (we are feeding in current and
 feeding back current through M_1 ;
 current summing happens at the
 drain of M_1 , gate of M_2)

shunt at the output : we sample voltage


small signal model :

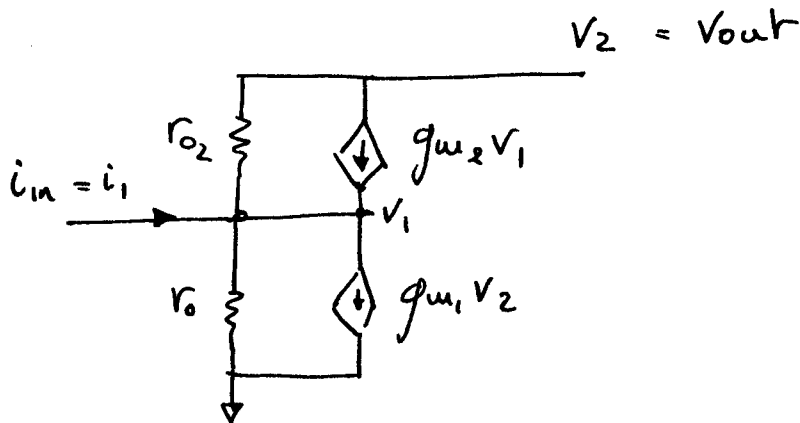

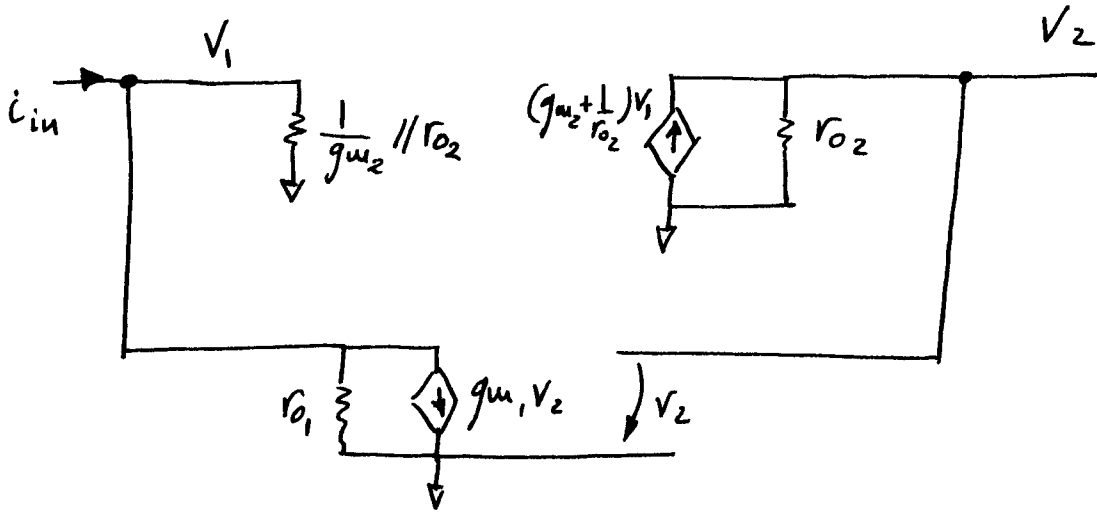Small signal model showing forward and feedback amplifier



|||

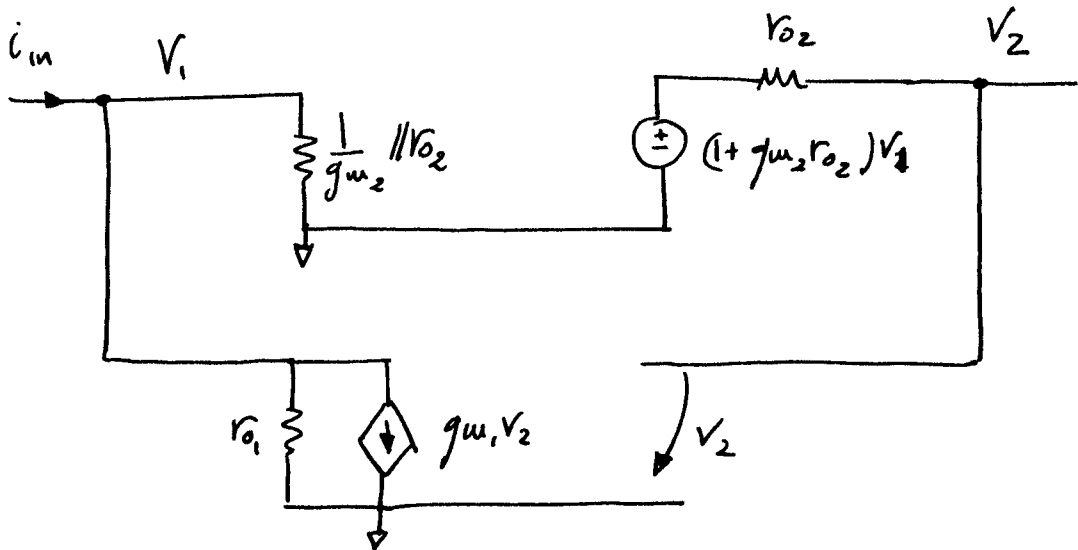


Since this is shunt-shunt feedback, the input and output resistances for the feedback and the forward amplifier have to be computed with the other terminal shorted (in small signal)

$$\text{e.g. } \frac{1}{g_{m2}} \parallel r_{o2} = \frac{i_1}{v_1} \Big|_{v_2=0} \quad (\text{only considering } H_2)$$


$$r_{o2} = \frac{i_2}{v_2} \Big|_{v_1=0} \quad (\text{only considering } H_1)$$

These parameters are called the "y-parameters", which you should use for shunt-shunt feedback to consider the loading of the feedback network when the terminal resistances of the forward amplifier depend on the other terminal

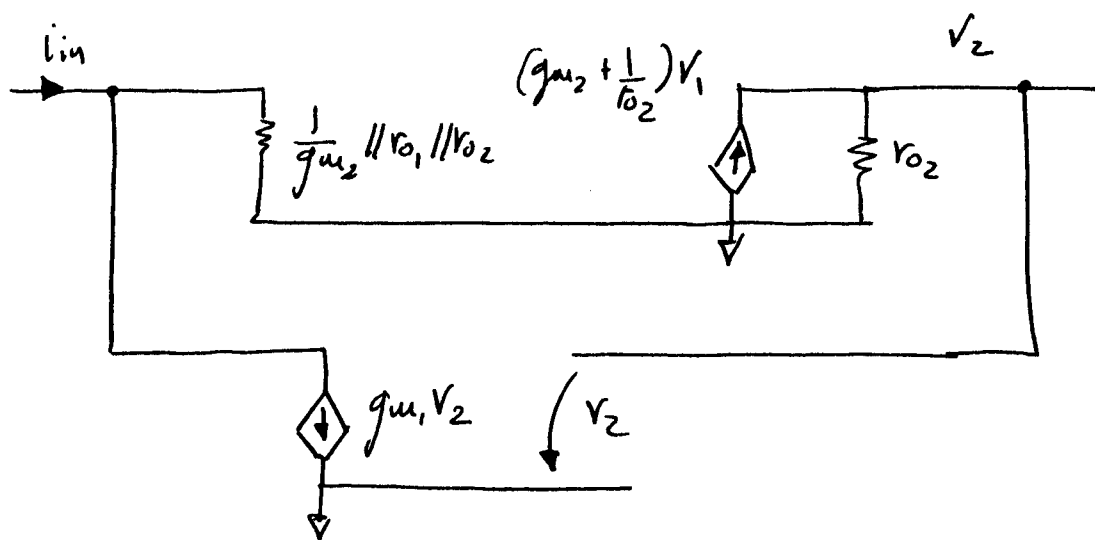Now we take the loading of the feedback network into account by moving all non-ideal elements to the forward amplifier:



|||

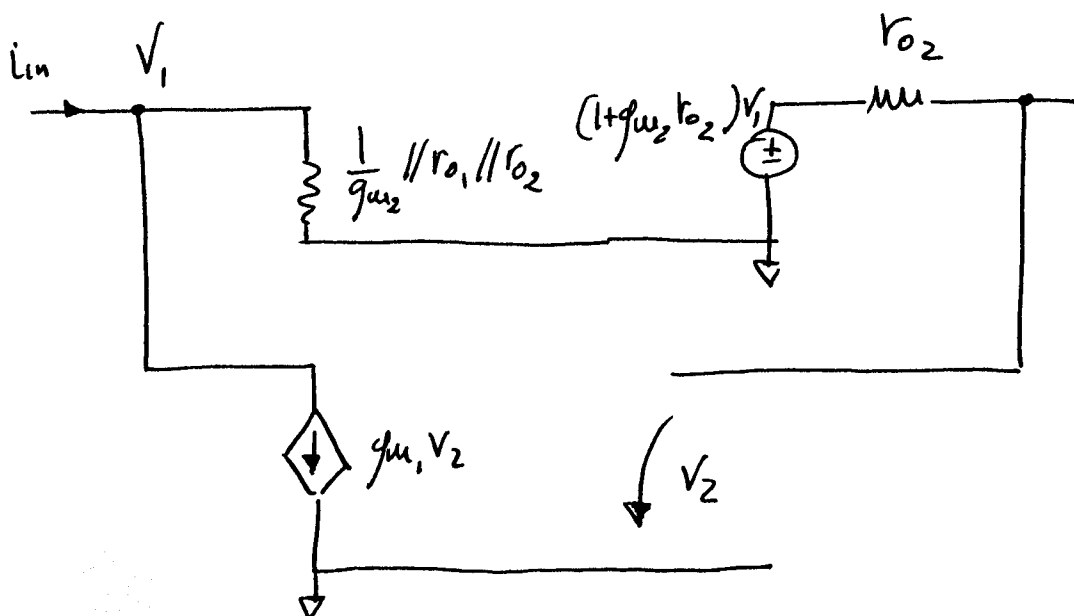

$$A_R = \left(\frac{1}{g_{m_2}} \parallel r_{o_2} \parallel r_{o_1} \right) (1 + g_{m_2} r_{o_2}) \approx r_{o_2}$$

$$f_G = -g_{m_1}$$

$$T \approx r_{o_2} g_{m_1}$$

① After feedback the overall transresistance becomes:

$$\frac{A_R}{1+T} \approx \frac{1}{g_{m_1}}$$

$$Z_{in} = \frac{1/g_{m_1} \parallel r_{o_1} \parallel r_{o_2}}{1+T} \approx \frac{1}{g_{m_1} g_{m_2} r_{o_2}}$$

$$Z_{out} = \frac{r_{o_2}}{1+T} \approx \frac{1}{g_{m_1}}$$

2) (a) Forward amplifier: G_m


Feedback: through C_F

(b) Shunt-shunt feedback

shunt at the input: current summing at the negative input node of " G_m "


shunt at the output: voltage sensing

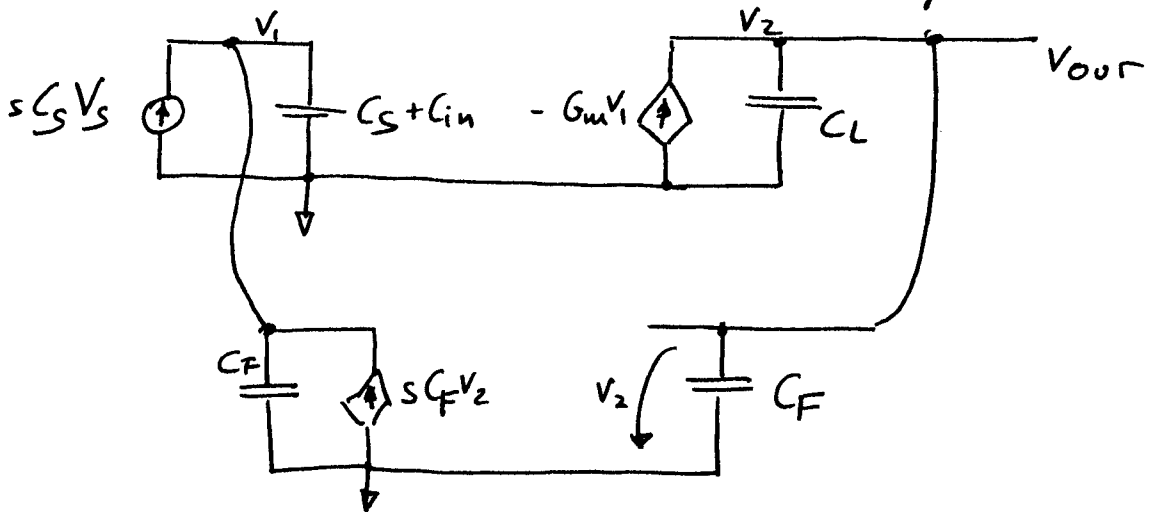(c) we can redraw the circuit as follows:



(Strictly speaking, we neglected the feedforward through the feedback capacitor; this will give a " $sC_F V_1$ " term that has to be added to " $-G_m V_1$ ")

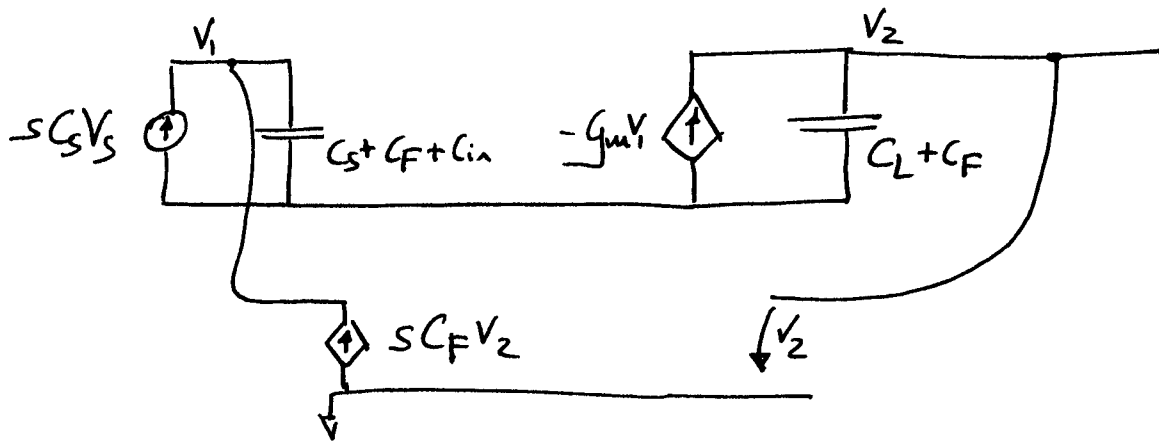Moving all the loading of the feedback network to the main amplifier, we get:



$$A_R = \frac{1}{s(C_S + C_F + C_{in})} (-g_m) \frac{1}{s(C_L + C_F)}$$

$$f_G = s C_F$$

$$T = \frac{C_F}{C_F + C_S + C_{in}} \frac{g_m}{s(C_L + C_F)}$$

④ After feedback, the transresistance gain, becomes:

$$\frac{A_R}{1+T} \approx \frac{A_R}{T} = \frac{1}{sC_F} = \frac{V_{out}}{i_{in}}$$

$$\Rightarrow \boxed{\frac{V_{out}}{V_{in}} = \frac{C_S}{C_F}} \quad (\text{since } i_{in} = sC_S V_{in})$$

$$Z_{out} = \frac{1}{s(C_L+C_F)} \frac{1}{1+T} \approx \frac{1}{s(C_L+C_F)} \frac{1}{T}$$

$$\Rightarrow \boxed{Z_{out} = \frac{1}{G_m} \frac{C_F + C_S + C_{in}}{C_F}}$$

\tilde{Z}_{in} for equivalent circuit (norton equivalent)

$$\tilde{Z}_{in} = \frac{1}{s(C_S+C_F+C_{in})} \frac{1}{1+T}$$

Real Z_{in} :


$$Z_{in} = \frac{1}{sC_S} + \left[\tilde{Z}_{in}^{-1} - sC_S \right]^{-1}$$

$$\approx \frac{1}{sC_S} \quad \text{for } f \ll \text{GBW of } T$$

- 3) (a) Forward amplifier: M_1
 Feedback: through C_1 & C_2
 (capacitive divider)

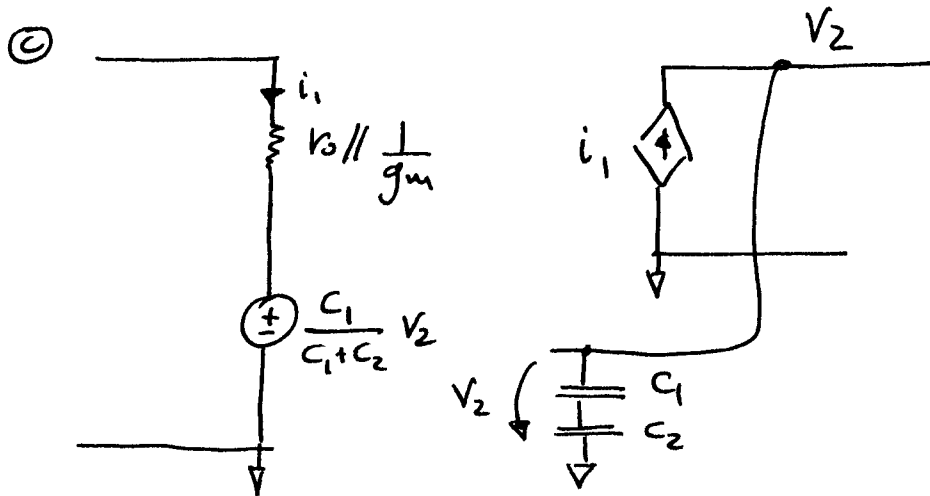(b) series - shunt

series at the input: voltage difference between v_{in} and $v_{out} \cdot \frac{C_1}{C_1 + C_2}$ drives M_1
 shunt at the output: voltage sensing



$$f = \frac{C_1}{C_1 + C_2} \quad A = \frac{1}{(r_o \parallel \frac{1}{g_m}) \parallel C_1 \parallel C_2}$$

where $C_1 \parallel C_2 = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

$$T = Af = \frac{1}{s C_2 (r_o \parallel \frac{1}{g_m})}$$

$$r_{o||} \frac{1}{g_m} = \frac{V_i}{i_i} \Big|_{V_2=0}$$

($V_2=0$, since the output is shunt)

$$\frac{i_2}{V_2} \Big|_{i_1=0} = \infty \quad \text{when only considering the forward amplifier (M.)}$$

$$\frac{i_2}{V_2} \Big|_{i_1=0} = s C_1 // C_2 \quad \text{when considering the feedback network}$$

($i_1=0$, since the input is series)

② Voltage gain with feedback:

$$\frac{A}{1+A_f} \approx 1 + \frac{C_2}{C_1}$$

$$Z_{in} = \frac{(r_{o||} // \frac{1}{g_m}) (1+A_f)}{1+A_f} = \frac{1}{s C_2}$$

$$Z_{out} = \frac{1}{s C_1 // C_2} \frac{1}{1+A_f} \approx \frac{1}{g_m} \left(1 + \frac{C_2}{C_1}\right)$$

Return Ratio Approach

① break at $g_{m1} \rightarrow$ $RR = g_{m1} r_{o1} (1 + g_{m2} r_{o2})$

$A_{\infty} = 0$ (closed-loop gain for $A_{m1} \rightarrow \infty$)

$d = r_{o1} (1 + g_{m2} r_{o2})$ (closed-loop gain for $g_{m1} \rightarrow 0$)

$$A = \frac{A_{\infty} RR}{1 + RR} + \frac{d}{1 + RR} = \frac{r_{o1} (1 + g_{m2} r_{o2})}{1 + g_{m1} r_{o1} (1 + g_{m2} r_{o2})} \approx \frac{1}{g_{m1}}$$

$$Z_{in} = Z_{in} \Big|_{g_{m1}=0} \cdot \frac{1 + RR | \text{input shorted}}{1 + RR | \text{input open}}$$

$$= r_{o1} \cdot \frac{1}{1 + RR} \approx \frac{1}{g_{m1} g_{m2} r_{o2}}$$

$$Z_{out} = Z_{out} \Big|_{g_{m1}=0} \cdot \frac{1 + RR | \text{output shorted}}{1 + RR | \text{output open}}$$

$$= \frac{r_{o1} (1 + g_{m2} r_{o2}) + r_{o2}}{1 + RR} \approx \frac{1}{g_{m1}}$$

② Break at the input of "Gm"

$$\Rightarrow RR = \frac{G_m}{s(C_L + C_F \parallel (C_S + C_{in}))} \cdot \frac{C_F}{C_F + C_S + C_{in}}$$

$$A_{\infty} = -\frac{C_S}{C_F} \quad (\text{assuming } RR \gg 1)$$

neglect s (will give a zero in the closed-loop transfer function, but not in the RR)

$$A \approx \frac{A_{\infty} RR}{1 + RR} \approx -\frac{C_S}{C_F} \quad (\text{assuming } RR \gg 1)$$

$$Z_{in} = Z_{in}|_{G_m=0} \frac{1 + RR|_{\text{input shorted}}}{1 + RR|_{\text{output open}}}$$

$$= [C_S \parallel (C_{in} + C_F \parallel C_L)]^{-1} \cdot \frac{1 + \frac{G_m}{s(C_L + C_F \parallel (C_S + C_{in}))} \cdot \frac{C_F}{C_S + C_F + C_{in}}}{1 + \frac{G_m}{s(C_L + C_F \parallel (C_S + C_{in}))} \cdot \frac{C_F}{C_F + C_{in}}}$$

$$\approx \frac{1}{s C_S} \quad (\text{assuming } RR \gg 1)$$

$$Z_{out} = Z_{out}|_{G_m=0} \frac{1 + RR|_{\text{output shorted}}}{1 + RR|_{\text{output open}}}$$

$$= \frac{1}{s(C_L + C_F \parallel (C_S + C_{in}))} \frac{1}{1 + RR} = \frac{1}{G_m} \frac{C_F + C_S + C_{in}}{C_F}$$

③ Break at the gate of M_1 :

$$RR = g_m \left[r_o \parallel \frac{1}{sC_1 \parallel C_2} \right] \frac{C_1}{C_1 + C_2}$$

$$RR = g_m \frac{r_o}{1 + s r_o C_1 \parallel C_2} \frac{C_1}{C_1 + C_2}$$

$$A_\infty = 1 + \frac{C_2}{C_1} \quad \text{neglect } d$$

$$A = \frac{A_\infty RR}{1 + RR} \approx A_\infty = 1 + \frac{C_2}{C_1}$$

$$Z_{in} = Z_{in}^\circ \frac{1 + RR(\text{input shorted})}{1 + RR(\text{input open})}$$

$$Z_{in}^\circ = \frac{\frac{1}{sC_1} + \frac{1}{sC_2} + r_o}{1 + g_m r_o} = \frac{1 + s r_o C_1 \parallel C_2}{1 + g_m r_o} \frac{1}{s C_1 \parallel C_2}$$

$$\Rightarrow Z_{in} = Z_{in}^\circ (1 + RR) \approx \frac{1}{s C_2}$$

$$Z_{out}^\circ = r_o \parallel \frac{1}{s C_1 \parallel C_2} = \frac{r_o}{1 + s r_o C_1 \parallel C_2}$$

$$Z_{out} = Z_{out}^\circ \frac{1 + RR(\text{output shorted})}{1 + RR(\text{output open})} = \frac{Z_{out}^\circ}{1 + RR}$$

$$\approx \frac{1}{g_m} \left(1 + \frac{C_2}{C_1} \right)$$