

# HW#9 solution

①

1. a)  $T_1 = R_{in} C_{GS1} = 1 \mu s \Rightarrow P_1 = 10^6 \text{ rad/sec}$

$$T_2 = r_{o2} \cdot C_{GS3} = \frac{1}{0.01 \times 100 \times 10^{-6}} \times 1 \text{ pF}$$


$$= 1 \mu s \Rightarrow P_2 = 10^6 \text{ rad/sec}$$

$$T_3 = r_{o3} \cdot C_o = 0.1 \text{ sec} \Rightarrow P_3 = 10 \text{ rad/sec}$$

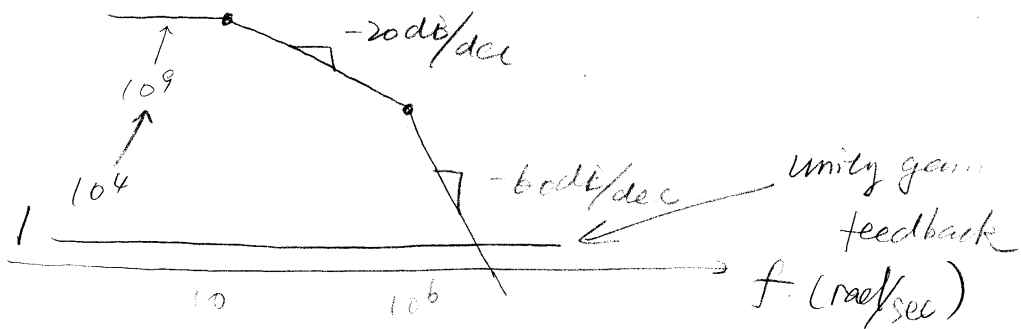b) bode plot shown below.

low frequency gain of the Amplifier =

$$A_v = -(g_{m1} r_{o1}) \cdot (g_{m2} r_{o2}) \cdot (g_{m3} r_{o3})$$
$$= -(10^3)^3 = -10^9$$




②

From the bode plot, the cross-over frequency would be above  $10^7$  rad/sec. Phase shift close to  $-270^\circ$  from that frequency. So the system would be ~~is~~ unstable!

c)  $R_F$  only affects pole #2.

Can use ZVTC for pole #2

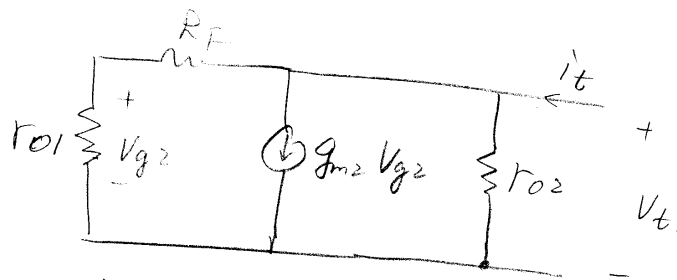

$$i_t = \frac{V_t}{r_{o2}} + \frac{V_t}{R_F + r_{o1}} + g_{m2} \frac{r_{o1}}{r_{o1} + R_F} \approx 0.99$$

$$\therefore R_{oc2} \approx \frac{r_{o2}}{2} \parallel \frac{r_{o1}}{g_{m2}}$$

$$= 500\text{k}\Omega \parallel 101\text{k}\Omega \approx 1\text{k}\Omega$$

$$\Rightarrow P_2 \approx 10^9 \text{ rad/sec} ; P_1 = 10^6, P_3 = 10 \text{ rad/sec}$$

3


d)  $G_m$  of the first two stages

$$G_{m1,2} = -g_{m1}(R_F || r_{o1}) \cdot g_{m2}$$
$$\approx -g_{m1} R_F \cdot g_{m2}$$

$$A_{v1,2} \cong g_{m1} R_F \cdot g_{m2} \cdot \frac{1}{g_{m2}} = g_{m1} \cdot R_F$$

Overall  $A_v = -g_{m1} R_F \cdot g_{m3} r_{o3}$

$$= -10^4$$

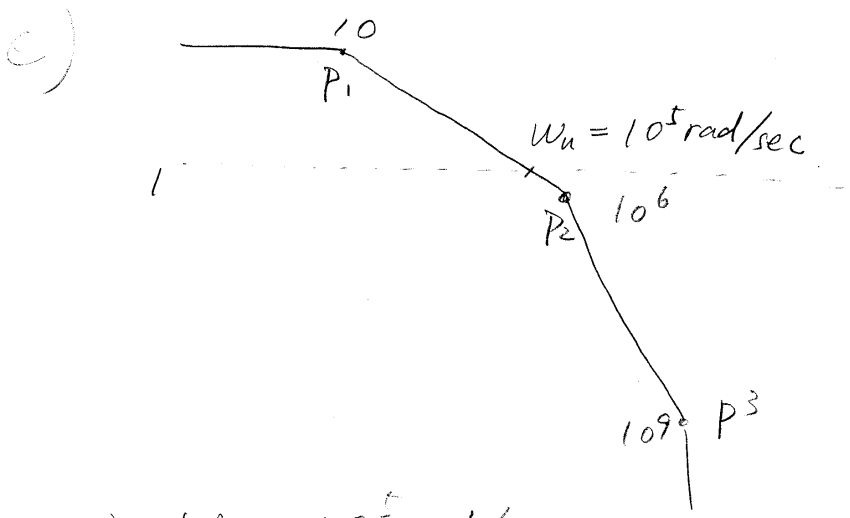

$$\therefore \omega_n = 10^5 \text{ rad/sec}$$