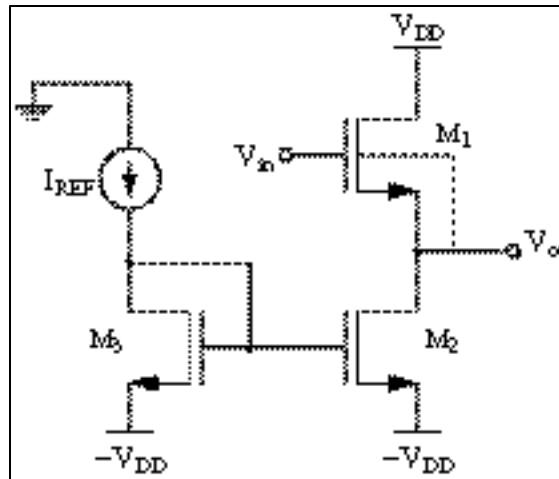


UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering
and Computer Sciences

R. W. Brodersen

EECS 140
Fall 2004

PROBLEM SET #6
(Due 11/17/04)




1) For the circuit above, assume all wells are tied to their respective sources. $V_{DD}=1.8$ V. All $W/L=6/0.18$. $I_{REF}=100$ μ A. V_{IN} is set so that the output is biased at 0 V. Use the following device model:

```
.model nch nmos LEVEL=1 TOX=25 VTO=0.5 KP=140.0e-6 LAMBDA=0.1  
+GAMMA=0.5 PHI=0.6
```

In this problem, use the feedback circuit techniques developed in class to analyze the above source follower.

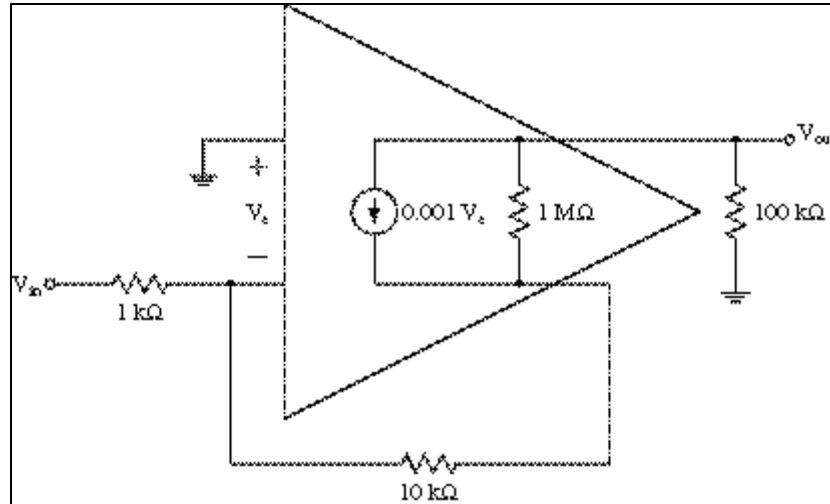- a) What kind of feedback is it?
- b) Find an expression for the feedback factor, f .
- c) Give an expression for the loop gain, T , with loading, and calculate the value.
- d) Give expressions and calculate v_{out}/v_{in} and R_{out} using the feedback formulas and compare to the exact expressions.



2) For the circuit above, determine the following:

a) What kind of feedback is it?

b) Find the feedback factor, f .

c) Find R_{out} .

d) Find v_{out}/v_{in} .

e) Use SPICE to check your answers for parts (c) and (d). Macromodel the opamp using `.subckt`.