

UNIVERSITY OF CALIFORNIA AT BERKELEY
College of Engineering
Department of Electrical Engineering and Computer Science

R. W. Brodersen,
S. Emami, and D. Sobel

Homework #8
(Due 12/10/04)

EECS140
Fall 2004

1. Consider the circuit shown in Figure 1..

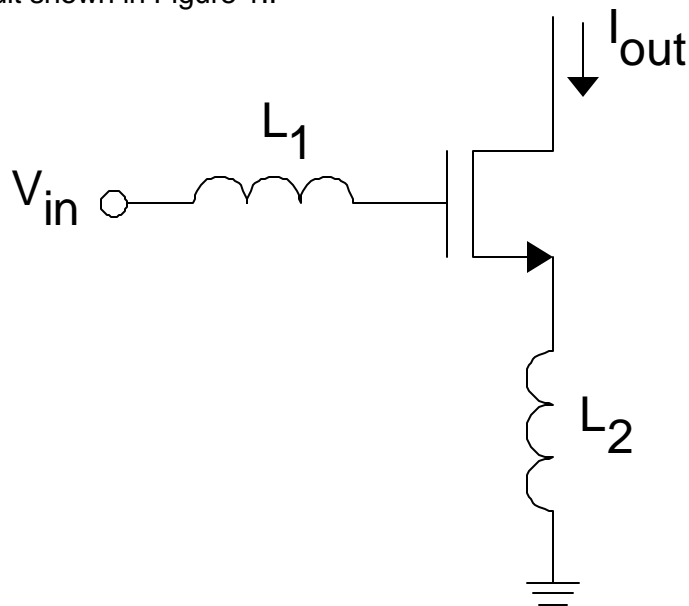


Figure 1

For the transistor above, consider only its g_m and C_{GS} . (i.e. $r_o \rightarrow \infty$, $C_{GD} = 0$, etc)

- Determine the size of L_1 and L_2 such that the input impedance is purely real and exactly 50ohms at an operating frequency of 5GHz. $g_m = 10\text{mS}$, $C_{GS} = 80\text{fF}$
- Calculate the G_M of this circuit for the parameters given and L_1 , L_2 as determined from part (a)

2. Consider the circuit in figure 2

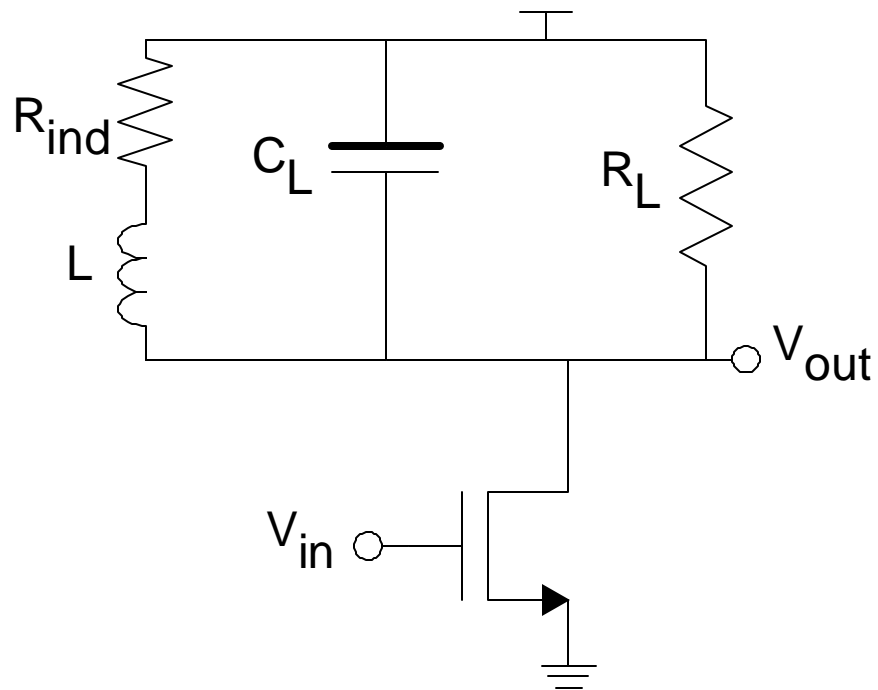


Figure 2

- a) At an operating frequency of ω_0 , we seek to use an inductor to cancel out the capacitance at the output, C_L . Determine the size of the inductor, L , that is required in terms of C_L , ω_0 , Q_{ind} , and R_L . Note that the inductor has a finite Q ($=Q_{ind}$), so that the relationship between R_{ind} and L is:

$$R_{ind} = \frac{\omega \cdot L}{Q_{ind}}$$

- b) Calculate the expression for the gain at $\omega = \omega_0$ of the circuit with and without the inductor present.

- c) Re-do parts (a) and (b) for the following device parameters:

$$\begin{aligned} g_m &= 10\text{mS} \\ R_L &= 1\text{kohm} \\ C_L &= 1\text{pF} \\ \omega_0 &= 2\pi \cdot 5\text{GHz} = 31.41 \text{ Grad/s} \\ Q_{IND} &= 10 (@ 5\text{GHz}) \end{aligned}$$

- d) Verify the gain calculations from part (b) in spice with the parameters from part (c)