
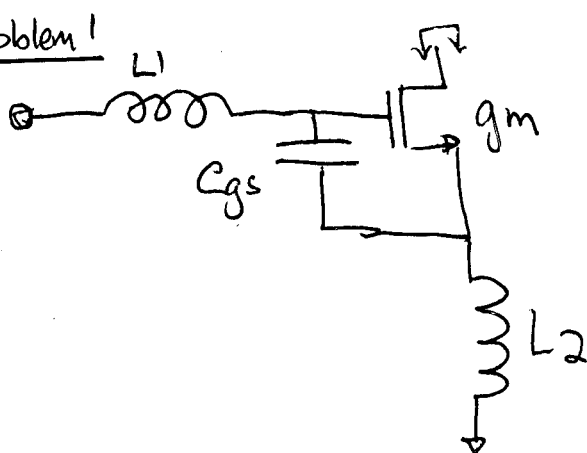


Problem 1

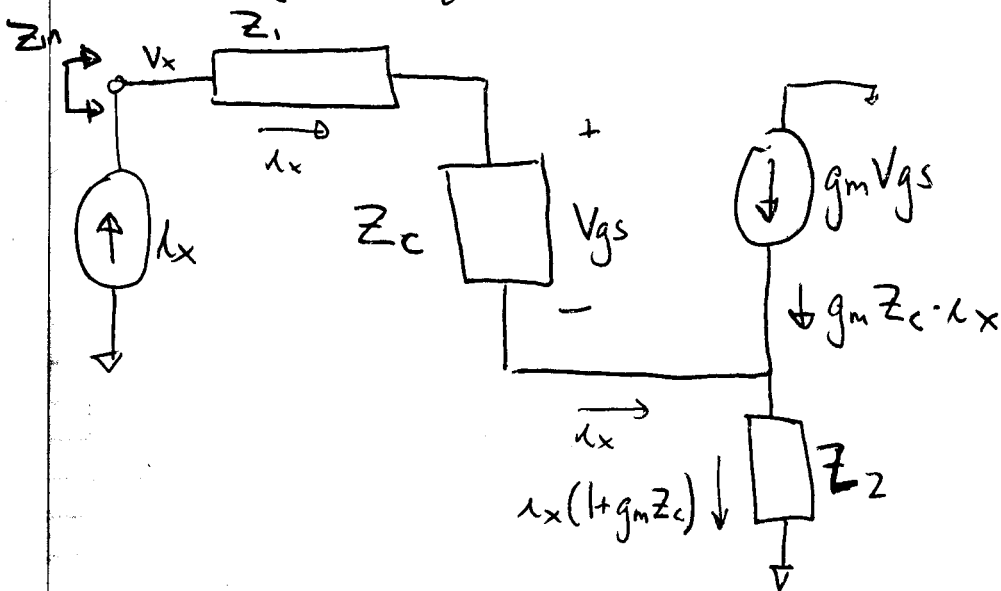

Small signal equivalent:



(a)

KVL:
$$V_x = Z_1 \cdot i_x + Z_c \cdot i_x + (1 + g_m Z_c) Z_2 \cdot i_x$$

$$Z_{IN} = \frac{V_x}{i_x} = Z_1 + Z_2 + Z_c + g_m Z_c \cdot Z_2$$

Let
$$\left. \begin{aligned} Z_1 &= j\omega_0 L_1 \\ Z_2 &= j\omega_0 L_2 \\ Z_c &= \frac{-j}{\omega_0 C_{gs}} \end{aligned} \right\}$$

$$\Rightarrow Z_{IN} = j \left[\omega_0 (L_1 + L_2) - \frac{1}{\omega_0 C_{gs}} \right] + \frac{g_m L_2}{C_{gs}}$$

$$= j \cdot X_{IN} + R_{IN}$$

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



At ω_0 , $Z_{IN} = 50 \Omega$

$\Rightarrow R_{IN} = \frac{g_m L_2}{C_{gs}} = 50 \Omega$

$\Rightarrow L_2 = \frac{50 \Omega \cdot C_{gs}}{g_m} = \frac{50 \cdot 80e-15}{10e-3} = 0.4 \text{ nH}$

~~X_{IN} = 0~~

$X_{IN} = 0 \Rightarrow \omega_0(L_1 + L_2) - \frac{1}{\omega_0 C_{gs}} = 0$

$\Rightarrow L_1 = \frac{1}{\omega_0^2 \cdot C_{gs}} - L_2 = \frac{1}{(2\pi \cdot 5e9)^2 \cdot 80e-15} - 0.4 \text{ nH}$

$\Rightarrow L_1 = 12.2 \text{ nH}$

$L_1 = 12.2 \text{ nH}$
 $L_2 = 0.4 \text{ nH}$

(b) At the operating frequency, $Z_{IN} = 50 \Omega$


$G_m = \frac{Z_c}{Z_{IN}} \cdot g_m = \frac{1}{50 \Omega} \cdot \left(\frac{-j}{\omega_0 C_{gs}} \right) \cdot g_m$

$= \frac{1}{50 \Omega} \cdot \left(\frac{-j}{(31.4 \text{ Grad/s})(80 \text{ fF})} \right) 10 \text{ mS} = -j \cdot 79.6 \text{ mS}$


$G_m = -j \cdot 79 \text{ mS}$
 i.e. 79 mS w/ a 90° phase lag

Problem 2

(a)

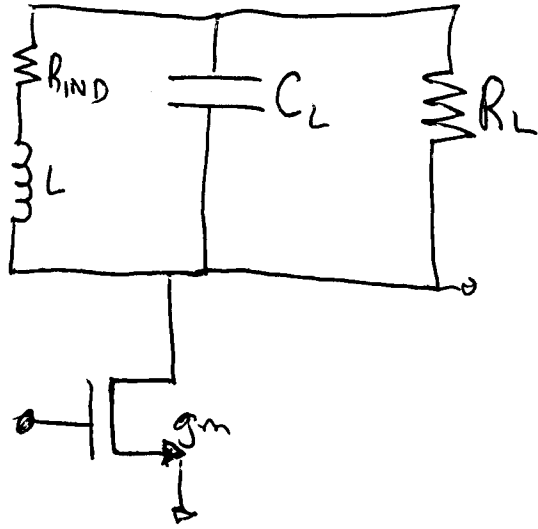


we know that

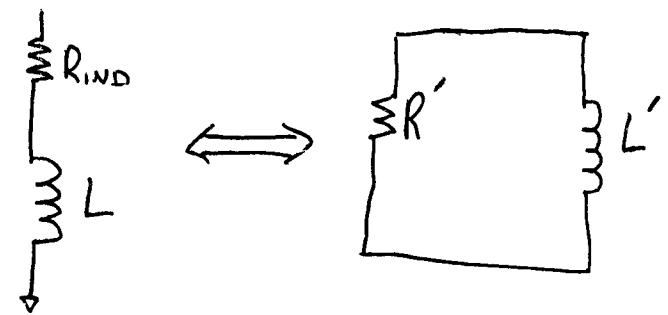

where $L' = L \cdot (1 + \frac{1}{Q_{ind}^2})$
 $R' = R_{ind} \cdot (1 + Q_{ind}^2)$

Therefore, we can represent the tank as:

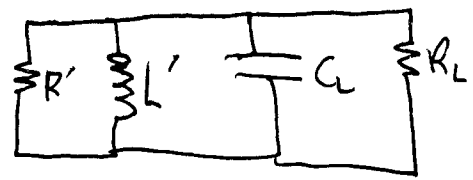


and obviously to ~~cancel~~ cancel out C_L :

$$\omega_0 L' = \frac{1}{\omega_0 C_L}$$

$$\Rightarrow L' = \frac{1}{\omega_0^2 C_L} \quad \hat{=} \quad L' = L \left(1 + \frac{1}{Q_{ind}^2}\right)$$

$$\Rightarrow L = \frac{1}{\omega_0^2 C_L} \cdot \frac{1}{1 + \frac{1}{Q_{ind}^2}}$$



without inductor present:

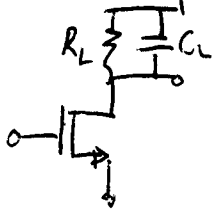

$$A_{v, \text{no inductor}} = g_m \cdot (R_L // Z_{\text{cap}})$$

$$= \frac{g_m \cdot R_L \cdot \frac{1}{j\omega_0 C_L}}{R_L + \frac{1}{j\omega_0 C_L}} = \boxed{\frac{g_m R_L}{1 + j\omega_0 R_L C_L}}$$

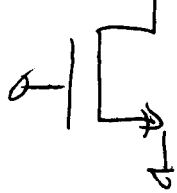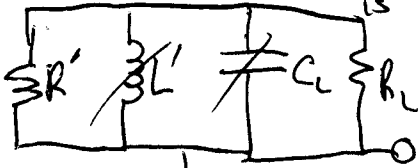with an inductor present: ~~with~~ NOTE that the inductor cancels out the capacitor, so all we are left with is R_L and R'



$$A_{v, \text{inductor}} = g_m (R_L // R')$$

$$R' = R_{\text{IND}} \cdot (1 + Q_{\text{IND}}^2) \quad \left. \begin{array}{l} R_{\text{IND}} = \frac{\omega L}{Q_{\text{IND}}} \\ \text{substitute} \end{array} \right\} R' = \omega_0 L \left(\frac{1}{Q_{\text{IND}}} + Q_{\text{IND}} \right)$$

Combine with $L = \frac{1}{\omega_0 C_L} \cdot \frac{1}{1 + \frac{1}{Q_{\text{IND}}^2}}$

$$\Rightarrow R' = \frac{\omega_0}{\omega_0^2 C_L} \cdot \frac{(1/Q_{\text{IND}} + Q_{\text{IND}})}{1 + \frac{1}{Q_{\text{IND}}^2}} = \frac{1}{\omega_0 C_L} \cdot Q_{\text{IND}} = R'$$

So, given value of R' , ~~with~~ $A_v = g_m \cdot (R_L // R')$

$$\Rightarrow A_v = \frac{g_m \cdot R_L \cdot \frac{Q_{\text{IND}}}{\omega_0 C_L}}{R_L + \frac{Q_{\text{IND}}}{\omega_0 C_L}} = \boxed{\frac{g_m R_L}{1 + \frac{\omega_0 R_L C_L}{Q_{\text{IND}}}}}$$

NOTE: How the g_m expression looks similar to part a, ~~with~~

Problem 2, part c

$$\text{Solve for } L: L = \frac{1}{\omega_0^2 C_L} \cdot \frac{1}{1 + \frac{1}{Q \cdot \omega_0^2}} = \frac{1}{(31.4 \text{ Grad})^2 \cdot 1 \text{ pf}} \cdot \frac{1}{1 + \frac{1}{100}}$$

$$L = 1.003 \text{ nH}$$

$$A_{v, \text{no inductor}} = \frac{g_m R_L}{1 + j\omega_0 R_L C_L} \xrightarrow{\text{magnitude}} |A| = \frac{g_m R_L}{\sqrt{1 + \omega_0^2 R_L^2 C_L^2}}$$

$$|A_{v, \text{no inductor}}| = \frac{10 \text{ mS} \cdot 1 \text{ k}\Omega}{\sqrt{1 + [31.4 \text{ Grad} \cdot 1 \text{ k} \cdot 1 \text{ pf}]^2}} = 0.318$$

$$|A_{v, \text{with inductor}}| = \frac{g_m R_L}{1 + \frac{\omega_0 R_L C_L}{Q_{IND}}} = \frac{10 \text{ mS} \cdot 1 \text{ k}\Omega}{1 + \frac{31.4 \text{ Grad} \cdot 1 \text{ k} \cdot 1 \text{ pf}}{10}} = 2.41$$