


University of California
 Berkeley
 College of Engineering
 Department of Electrical Engineering
 and Computer Science

Robert W. Brodersen
 EECS140

Analog Circuit Design


**Lectures
 on
 APPLICATIONS**

APP-01

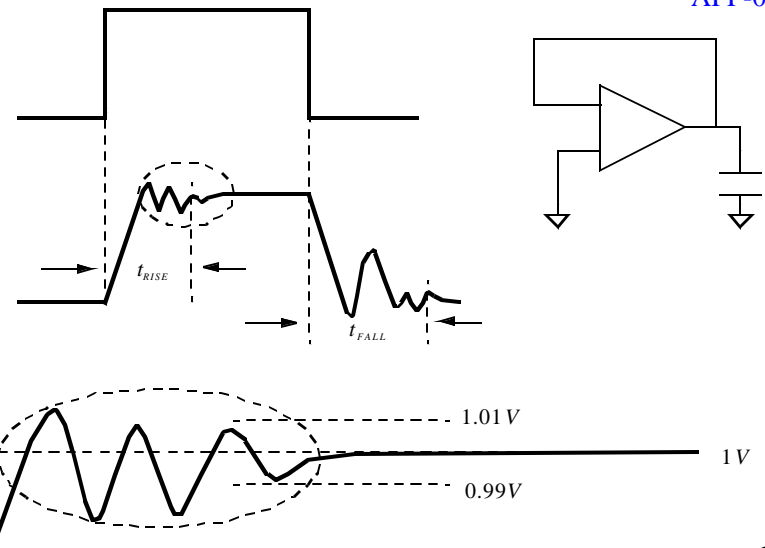


APP-02

15-20 Years Ago

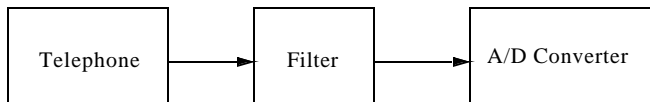

PCM Codec

APP-03

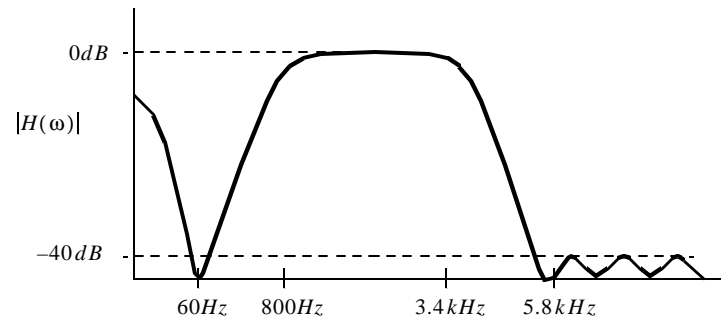


Pole - Zero Diagrams

APP-04


A convenient way of visualizing transfer functions, the Laplace Transform :
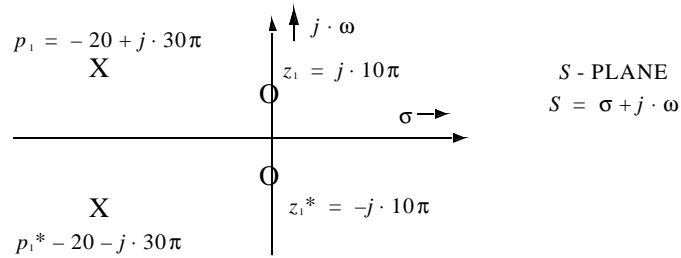
$$H_{(s)} = \frac{v_{out}(s)}{v_{in}(s)} = \frac{(s - z_1) \cdot (s - z_1^*)}{(s - p_1) \cdot (s - p_1^*)}$$



Poles - Zero Diagrams (Cont.)

APP-06

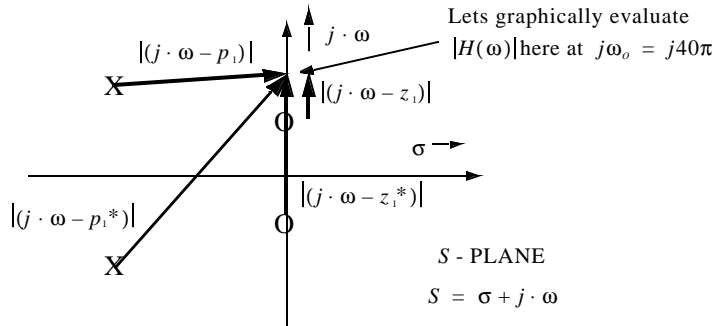

The magnitude $|H(\omega)|$ is the product of the lengths of vectors 3 & 4 divided by the product of the lengths of vectors 1 & 2.

Poles - Zero Diagrams (Cont.)

APP-05

Often what we are really interested in is $|H(\omega)|$,i.e. the magnitude and phase at frequency, ω .

$$H(\omega) = H(s) \Big|_{s=j\omega}$$


$$H(\omega) = \frac{(j \cdot \omega - z_1) \cdot (j \cdot \omega - z_1^*)}{(j \cdot \omega - p_1) \cdot (j \cdot \omega - p_1^*)}$$

To find the magnitude use the fact that magnitude of the products equals the product of the magnitudes , so that :

$$|H(\omega)| = \frac{|(j \cdot \omega - z_1) \cdot (j \cdot \omega - z_1^*)|}{|(j \cdot \omega - p_1) \cdot (j \cdot \omega - p_1^*)|} = \frac{|(j \cdot \omega - z_1)| \cdot |(j \cdot \omega - z_1^*)|}{|(j \cdot \omega - p_1)| \cdot |(j \cdot \omega - p_1^*)|}$$


Poles - Zero Diagrams (Cont.)

APP-07

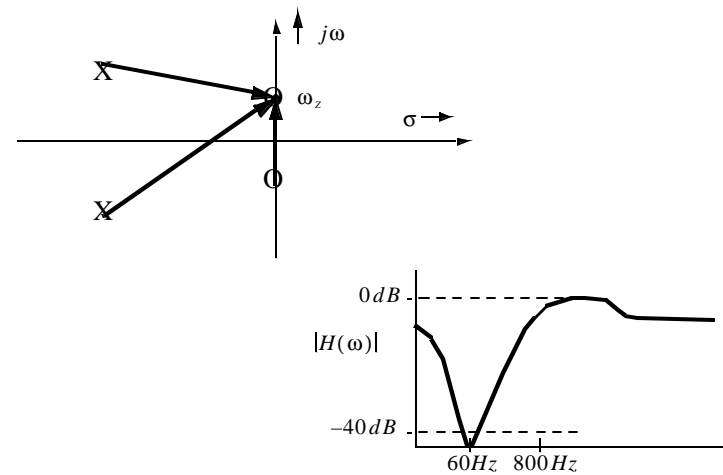


Poles - Zero Diagrams (Cont.)

APP-08

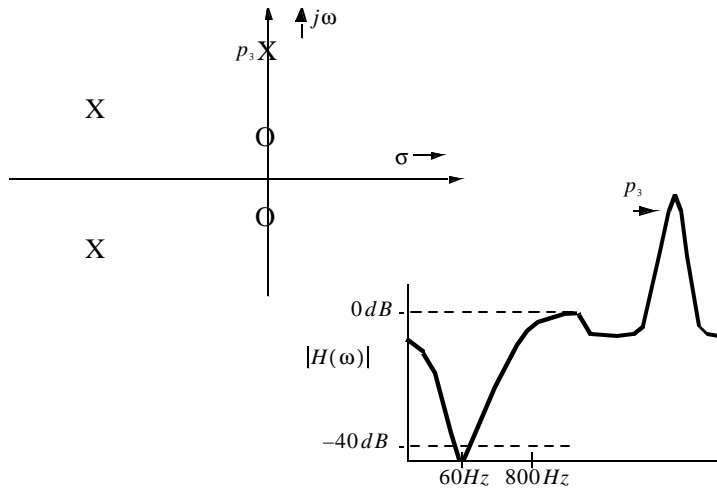


Poles - Zero Diagrams (Cont.)

APP-09

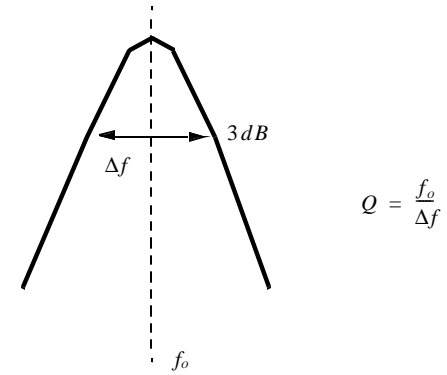



Filter Design

APP-10

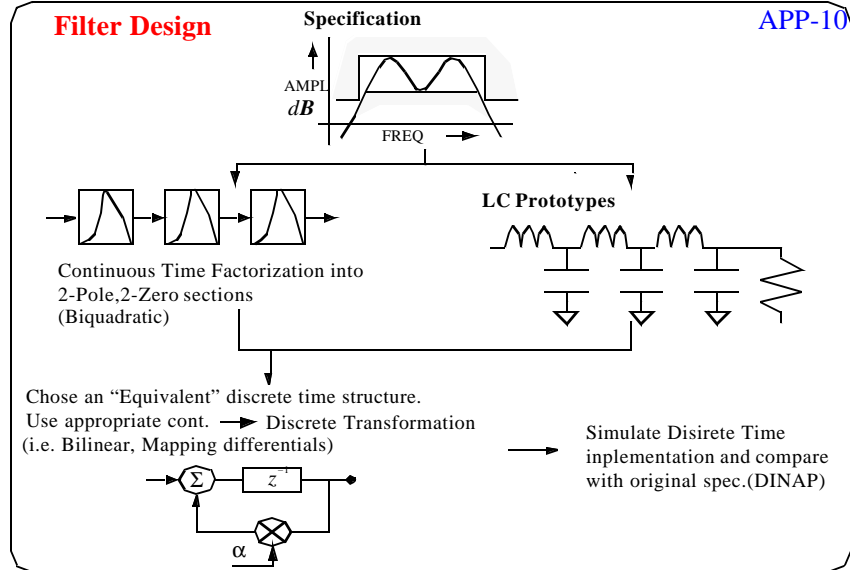


APP-11

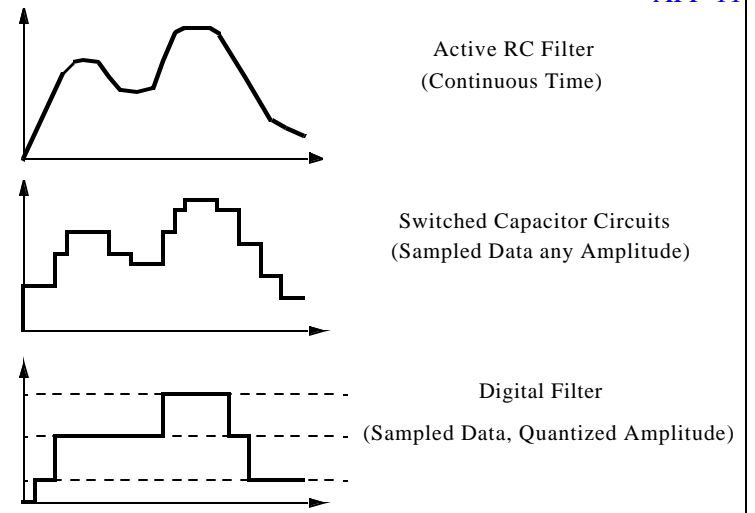

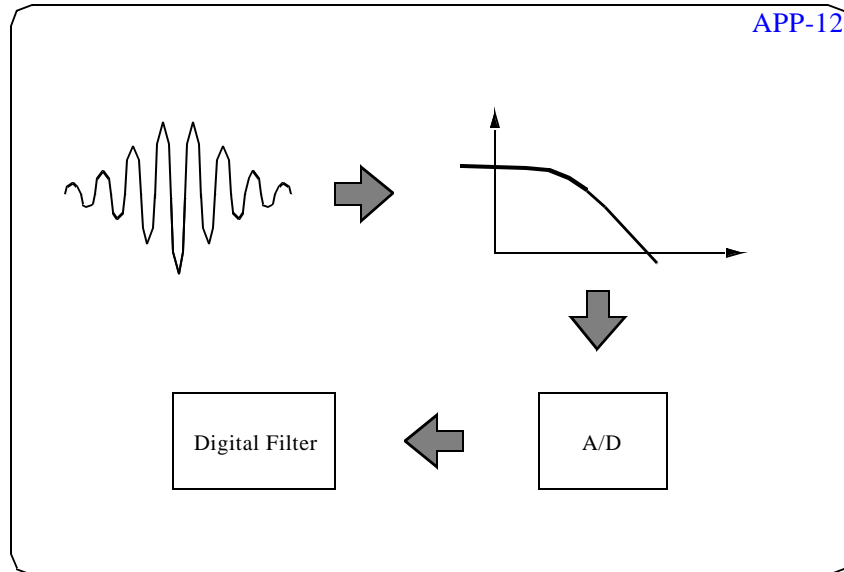


Typical Filter Specifications (Cont.)

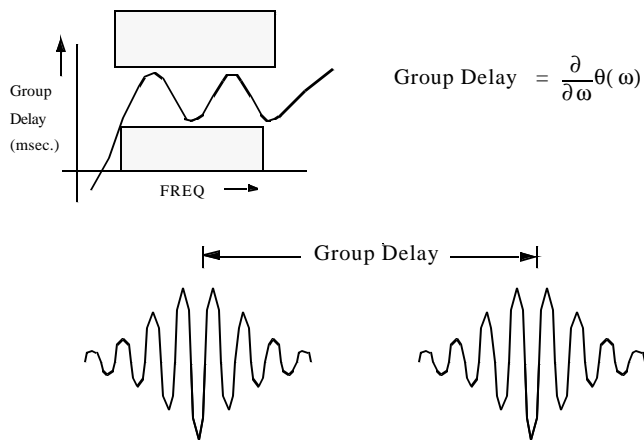

Typical Filter Specifications

Continuous time specifications of transfer function $|H(\omega)|$

$$\frac{V_{OUT}(\omega)}{V_{IN}(\omega)} = H(\omega) = |H(\omega)| \cdot e^{j\theta(\omega)}$$

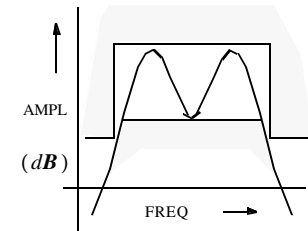


Amplitude (Magnitude in dB) = $10 \log \left[\frac{H(\omega) \cdot H^*(\omega)}{|H(\omega)|^2} \right]$

Types of 2-Pole Transfer Functions

Lowpass :
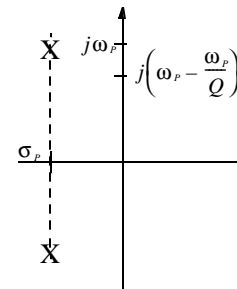
$$H(s) = \frac{\omega_c^2}{s^2 + \frac{\omega_c}{Q} \cdot s + \omega_c^2}$$




$$s_1, s_1^* = -\frac{\omega_c}{Q} \mp \sqrt{\left(\frac{\omega_c}{Q}\right)^2 - 4 \cdot \omega_c^2}$$

Types of 2-Pole Transfer Functions (Cont.)

APP-16

(Lowpass)

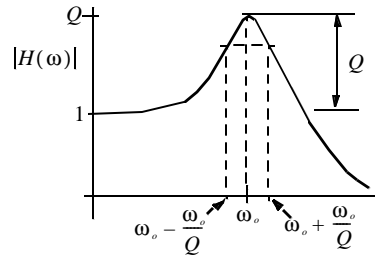

$$\omega_o \equiv |s_p| = \sqrt{s_p^2 + \omega_p^2}$$



$$Q \equiv \frac{|s_p|}{2 \cdot |s_p|} = \frac{1}{2} \cdot \sqrt{1 + \left(\frac{\omega_p}{s_p}\right)^2}$$

Types of 2-Pole Transfer Functions (Cont.)

APP-17

Bandpass :
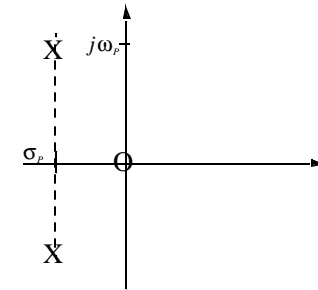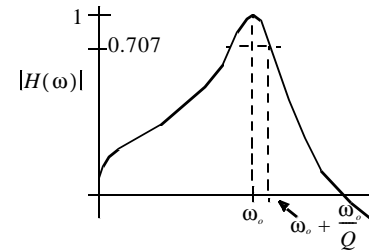
$$H(s) = \frac{\frac{\omega_o}{Q} \cdot s}{s^2 + \frac{\omega_o}{Q} \cdot s + \omega_o^2}$$




Types of 2-Pole Transfer Functions (Cont.)

APP-18

Highpass :

$$Highpass = 1 - (Lowpass) - (Bandpass)$$
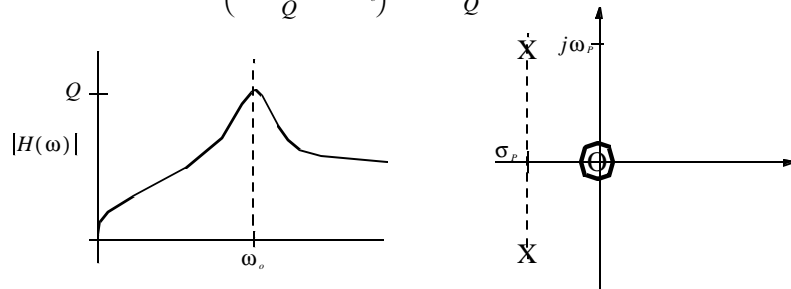
$$= 1 - \left(\frac{\frac{1}{\omega_o^2} + \frac{\omega_o}{Q} \cdot s}{s^2 + \frac{\omega_o}{Q} \cdot s + \omega_o^2} \right) = \frac{s^2}{s^2 + \frac{\omega_o}{Q} \cdot s + \omega_o^2}$$




Types of 2-Pole Transfer Functions (Cont.)

APP-19

Bandstop (or Notch) :
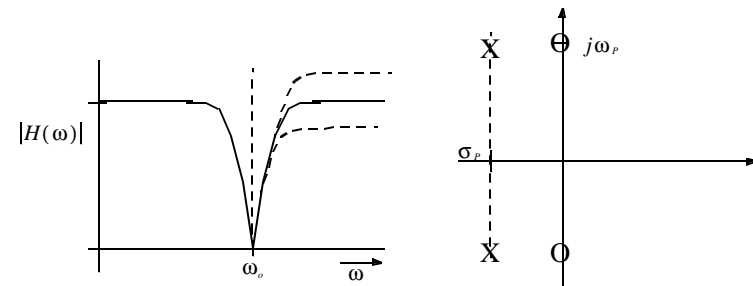
$$Bandstop = 1 - \frac{s \cdot \left(\frac{\omega_o}{Q}\right)}{s^2 + \frac{\omega_o}{Q} \cdot s + \omega_o^2} = \frac{s^2 + \omega_o^2}{s^2 + \frac{\omega_o}{Q} \cdot s + \omega_o^2}$$






Types of 2-Pole Transfer Functions (Cont.)

APP-20

All Pass (Delay Equalizer) :


$= 1 - 2 - (\text{Bandpass})$
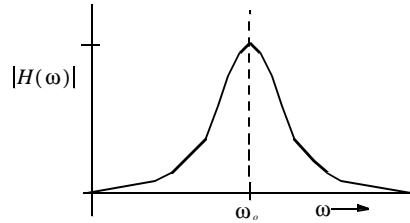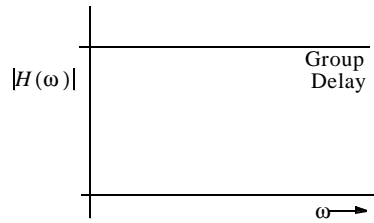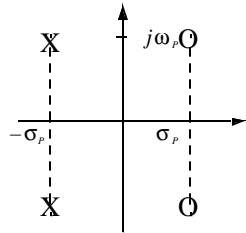
$$H(s) = 1 - \frac{2 \cdot s \cdot \frac{\omega_o}{Q}}{s^2 + \frac{\omega_o}{Q} \cdot s + \omega_o^2} = \frac{s^2 - \frac{\omega_o}{Q} \cdot s + \omega_o^2}{s^2 + \frac{\omega_o}{Q} \cdot s + \omega_o^2}$$



State Variable Active RC Filter (Cont.)

APP-22

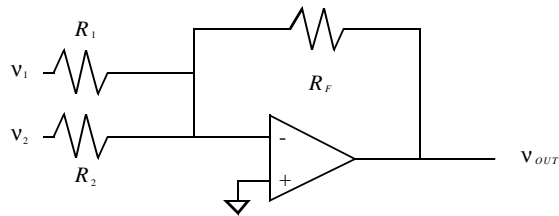


$$v_{OUT} = v_1 \frac{R_F}{R_1} + v_2 \frac{R_F}{R_2}$$

State Variable Active RC Filter


APP-21

Lowpass & Bandpass :

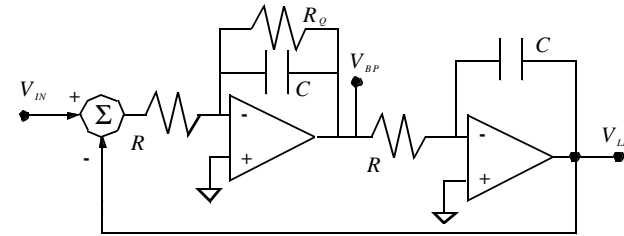

State Variable Active RC Filter (Cont.)

APP-23

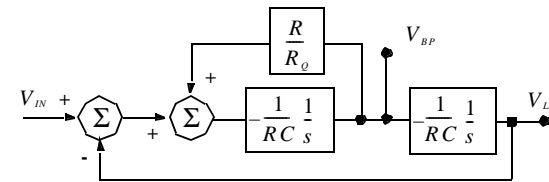

$$\frac{V_{LP}}{V_{IN}} = \frac{\left(\frac{1}{RC}\right)^2}{s^2 + \left(\frac{1}{R_c \cdot C} \cdot s\right) + \frac{1}{R_c}} = \frac{\omega_o^2}{s^2 + \frac{\omega_o}{Q} s + \omega_o^2}$$

$$\therefore \omega_o = \frac{1}{RC} \quad Q = \frac{R_o}{R}$$

State Variable Active RC Filter (Cont.) APP-24

$$\frac{V_{BP}}{V_{IN}} = \frac{-\frac{1}{RC} \cdot S}{S + \frac{1}{R_c \cdot C} \cdot S + \left(\frac{1}{R_c}\right)^2} = \frac{-\omega_o \cdot S}{S + \frac{\omega_o}{Q} \cdot S + \omega_o^2}$$

(Note GAIN is $-Q$ at ω_o instead of 1 as required for a canonical bandpass.)

Highpass :

$$Highpass = 1 - (Lowpass) - (Bandpass)$$


Using a 3RD OP AMP we form the sum,

$$V_{HIGHPASS} = V_{IN} - V_{LP} + \frac{1}{Q} \cdot V_{BP}$$

APP-26

Active RC Filters - Integrator or State Variable Configurations

Basic Element is the OP AMP Integrator :

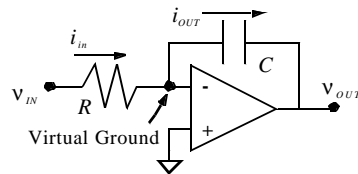

State Variable Active RC Filter (Cont.) APP-25

Bandstop :

$$Bandstop = 1 - (Bandpass)$$

$$V_{BANDSTOP} = V_{IN} + \frac{1}{Q} \cdot V_{BP}$$

All Pass :

$$Allpass = 1 - 2(Bandpass)$$

$$V_{ALLPASS} = V_{IN} + \frac{2}{Q} \cdot V_{BP}$$

APP-27

Active RC Filters - Integrator or State Variable Configurations (Cont.)

$$i_{OUT} = i_{in}$$

$$i_{in} = \frac{v_{in} - 0}{R} = \frac{v_{in}}{R}$$

$$-SC \cdot v_{OUT} = \frac{v_{in}}{R}$$


$$i_{OUT} = \frac{0 - v_{OUT}}{1/SC} = -SC \cdot v_{OUT}$$

$$\frac{v_{OUT}}{v_{in}} = -\frac{1}{RC} \cdot \frac{1}{S} = H(s)$$

$$H(s) |_{s=j\omega} = -\frac{1/RC}{j\omega}$$

Active RC Filters - Integrator or State Variable Configurations (Cont.)

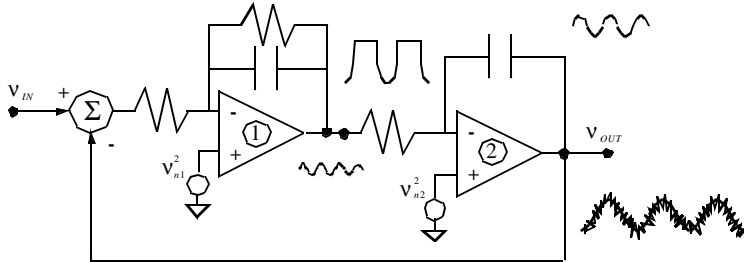Scaling of the internal node voltages for maximum dynamic range.



$$f_o = 3 \text{ kHz}$$

$$\omega_o = \frac{20 \text{ krad}}{\text{sec}} = \frac{1}{RC}$$

$$C = 10 \text{ pF}$$

$$R = \frac{1}{10 \text{ pF} \cdot 20 \cdot 10^3} = \frac{1}{2 \cdot 10^{-7}}$$

$$R = 5 \text{ M}\Omega$$

$$R \pm 10\% \quad C \pm 10\%$$

$$RC \pm 20\%$$


Active RC Filters - Integrator or State Variable Configurations (Cont.)

For maximum dynamic range. (Signal / Noise Ratio) the outputs of both op amps should have the same peak values.

If this is not true;

- If op amp #1 has a peak signal larger than #2, then #1 will saturate early limiting the maximum signal.
- If #1 has a peak amplitude less than #2, then there must be gain from #1 to #2 and the noise of #1 will be amplified.

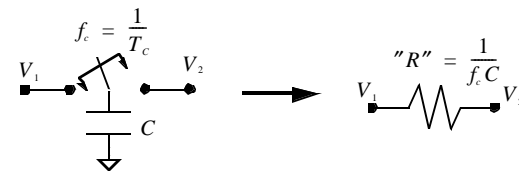Basic Element of Switched - Capacitor Filters





$$\Delta Q = C \cdot (V_2 - V_1)$$


$$"I" = \frac{\Delta Q}{T_c} = f_c \cdot C \cdot (V_2 - V_1)$$

$$"R" = \frac{V_2 - V_1}{I} = \frac{1}{f_c C}$$

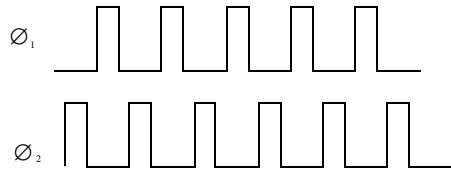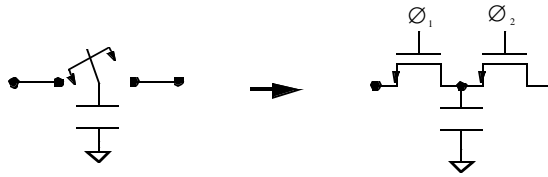Basic Element of Switched - Capacitor Filters (Cont.) APP-32



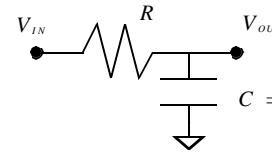Size of Switched - Capacitor, Resistors APP-33



$f_{3dB} = 10kHz$
 $C = 10pF$
 $R = \frac{1}{2\pi \cdot f_{3dB} \cdot C} = \frac{1}{(6.28) \cdot (10^4) \cdot (10^{-11})}$
 $= 1.6M\Omega$

Area of S-C Resistor


$(f_c = 100kHz)$
 $C_R = \frac{1}{f_c \cdot R} = \frac{1}{10^5 \times 1.6 \times 10^6}$
 $= 6.28pF$
 $\approx 31mil^2s (@5mil^2/pF)$

Area of Poly Resistor

$(50\Omega/\square)$
 $= 32 \times 10^3 \square$
 $\approx 3.2 \times 10^3 mil^2s (@1mil^2/\square)$


Equivalent S-C resistor about
 2 orders of magnitude smaller in area.

Simple Filter APP-34

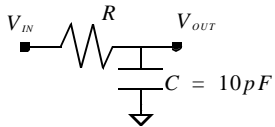

$\omega_{3dB} = \frac{1}{RC}$


Requires absolute
 control of R and C

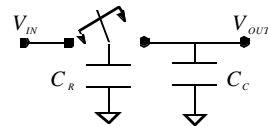

$\omega_{3dB} \approx \frac{1}{\left(\frac{1}{f_c \cdot C_R}\right) \cdot C_C} = f_c \cdot \left(\frac{C_R}{C_C}\right)$


Requires control
 of Ratios of C

S-C Integrator APP-35

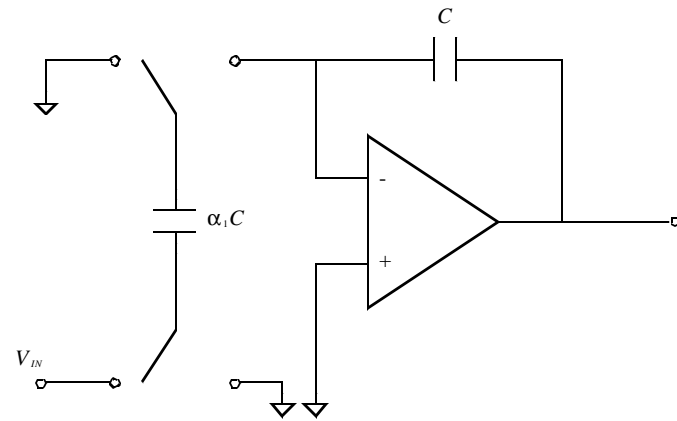


APP-36

Two Integrators Together

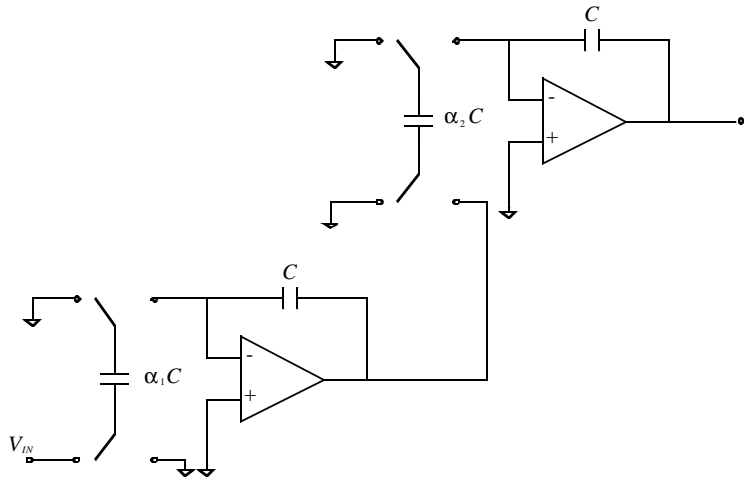

APP-37

Time Switched Equivalent Circuit

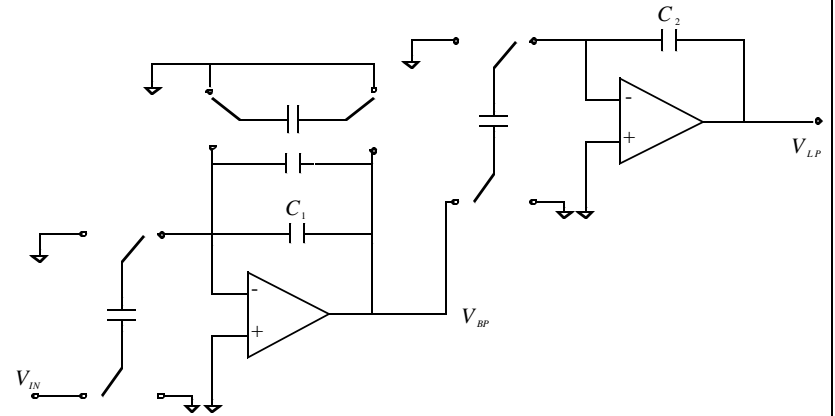


APP-38

$$C_{ox} = \frac{\epsilon_{SiO_2}}{t_{ox}}$$

$$C_c = A_{cap} \cdot C_{ox}$$
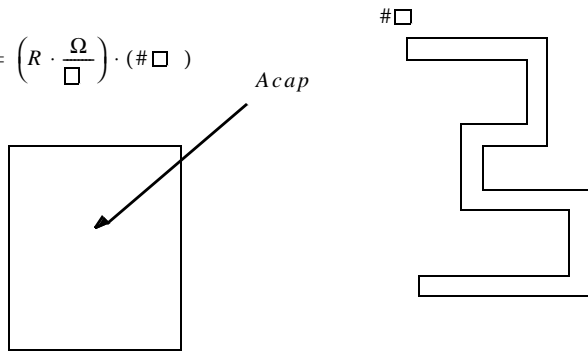
$$R = \left(R \cdot \frac{\Omega}{\square} \right) \cdot (\# \square)$$



APP-39

