

University of California
Berkeley

College of Engineering
Department of Electrical Engineering
and Computer Science



Robert W. Brodersen
EECS140

Analog Circuit Design


Lectures
on
CURRENT SOURCES

CS-1

Current Sources

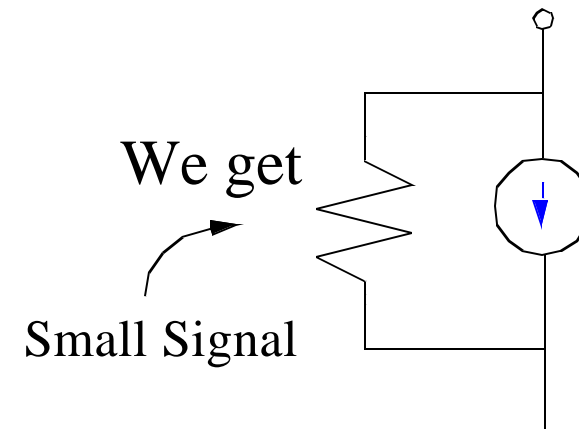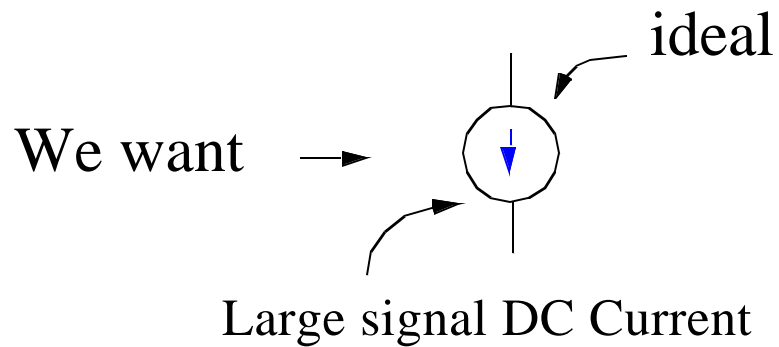

Simple Source

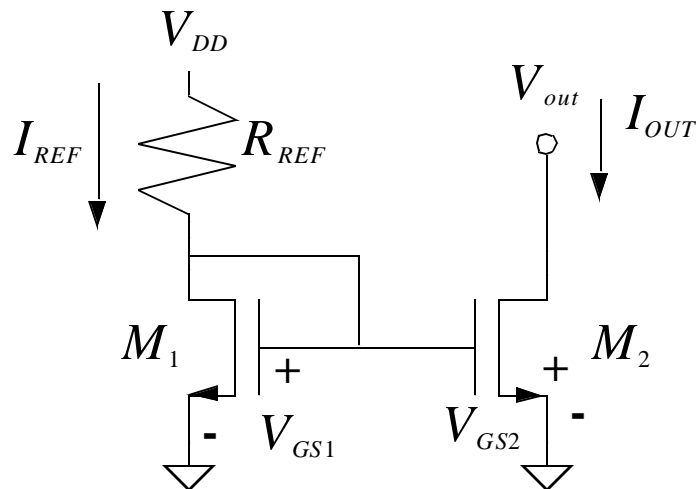


$$V_{OUT} > V_{GS} - V_T$$

$$= V_{DSAT}$$


$$V_{DSAT} = \left(\frac{2 \cdot I_{DS}}{k' \cdot \frac{W}{L}} \right)^{\frac{1}{2}} \approx 0.1$$

CS-1a



Ideal Current Source

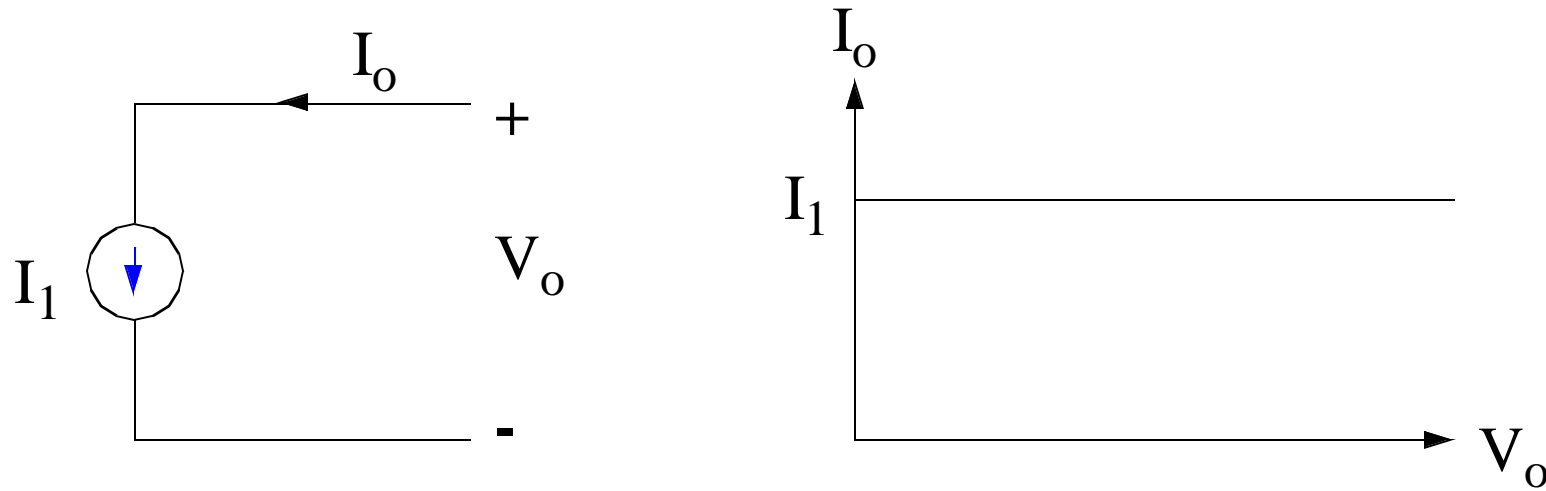

Real Current Source

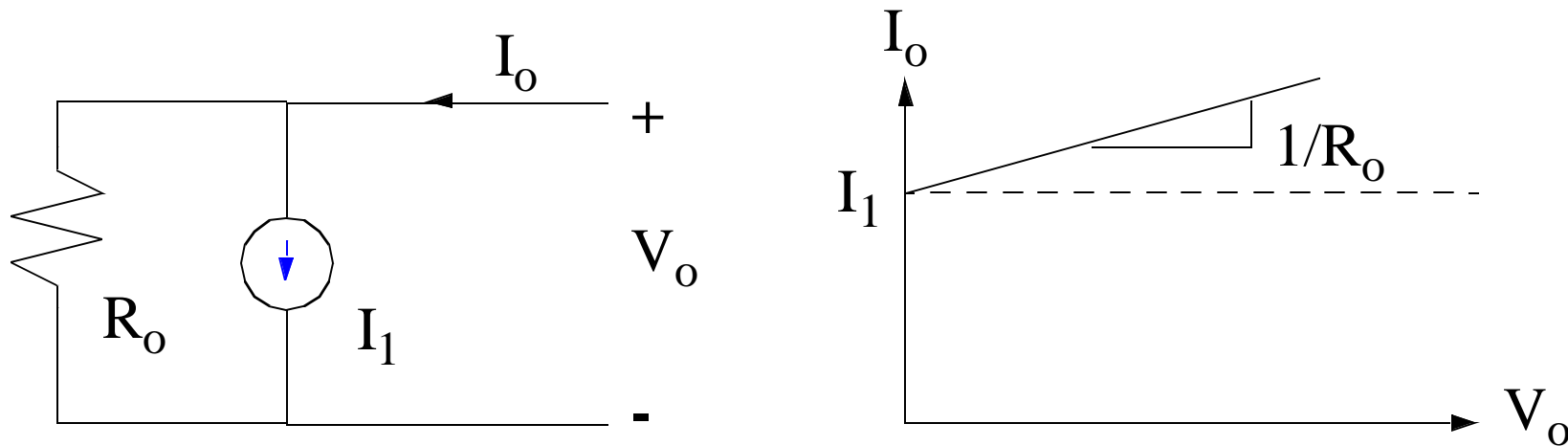

CS-2

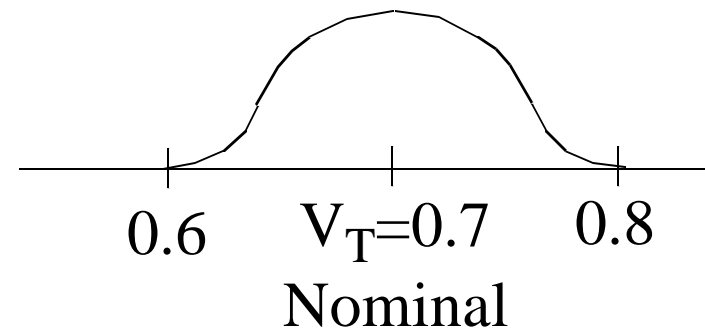
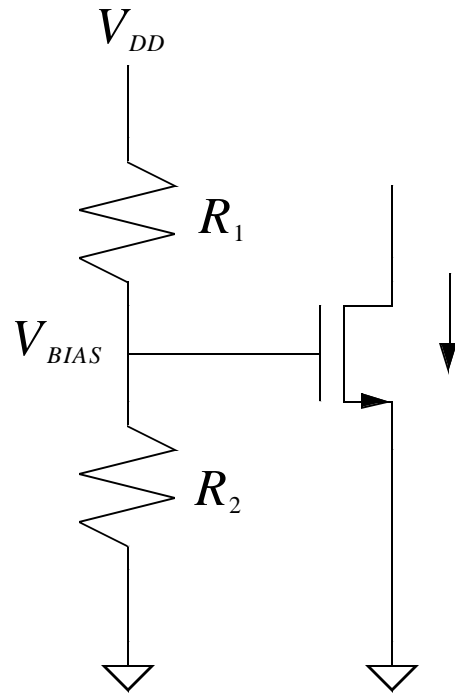


$$I_{DS1} = \frac{W}{L} \cdot \frac{k'}{2} \cdot (V_{BIAS} - V_T)^2$$

Simple Source (Cont.)

CS-3

Diode Connected Transistor :

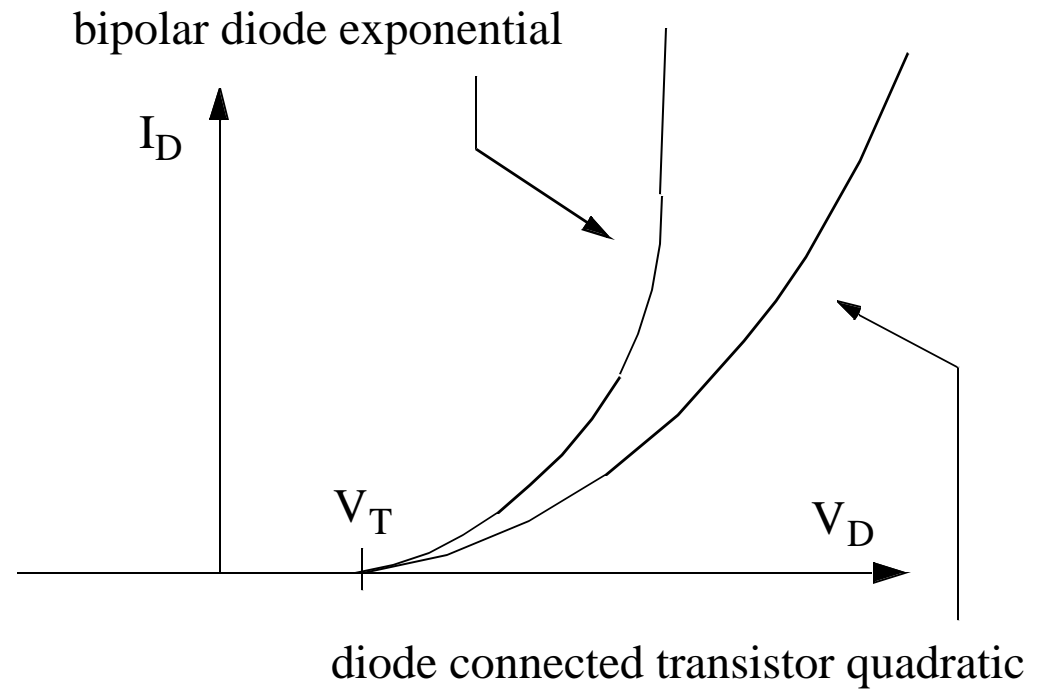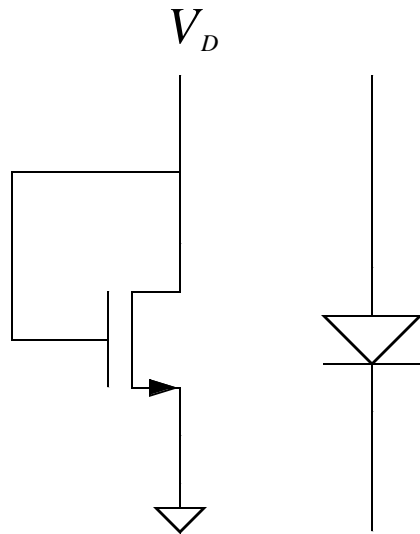

$V_{DS} > V_{GS} - V_T$ } After we reach the point $V_D > V_T$, the transistor will always be in Sat.

Simple Source (Cont.)

CS-4

$$I_{DS1} = \left(\frac{W}{L}\right)_1 \cdot \frac{k'}{2} \cdot (V_{GS1} - V_T)^2$$

$$I_{DS2} = \left(\frac{W}{L}\right)_2 \cdot \frac{k'}{2} \cdot (V_{GS2} - V_T)^2$$

if $\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$, then $I_{DS1} = I_{DS2}$

otherwise $I_{OUT} = I_{REF} \cdot \left[\frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \right]$

$$I_{REF} = I_{DS1} \quad , \quad I_{OUT} = I_{DS2}$$

Simple Source (Cont.)

CS-5

Current Calculation :


Analysis :

$$I_{DS1} = I_{REF} = \frac{V_{DD} - V_{GS1}}{R_{REF}}$$

$$V_{GS1} = V_T + \left(\frac{2 \cdot I_{DS1}}{k' \cdot \frac{W}{L}} \right)^{\frac{1}{2}} = V_T + \Delta V$$

$$I_{REF} = V_{DD} - V_T - \left(\frac{2 \cdot I_{REF}}{k' \cdot \frac{W}{L}} \right)^{\frac{1}{2}}$$

Iterative Solution !

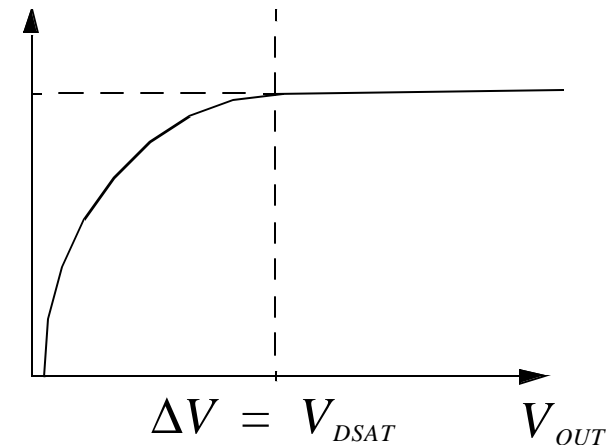

Simple Source (Cont.)

CS-6

Design :

$$R_{REF} = \frac{V_{DD} - V_{GS1}}{I_{REF}} = \frac{V_{DD} - V_T - \left(\frac{2 \cdot I_{REF}}{k' \cdot \frac{W}{L}} \right)^{\frac{1}{2}}}{I_{REF}}$$

$$I_{REF} = 10\mu A, V_{DD} = 5, V_T = 0.7$$


$$k' = 90 \times 10^{-6}$$

$$R_{REF} = 415k\Omega \quad (\text{Pretty Big!})$$

Simple Source (Cont.)

CS-7

Small Signal :

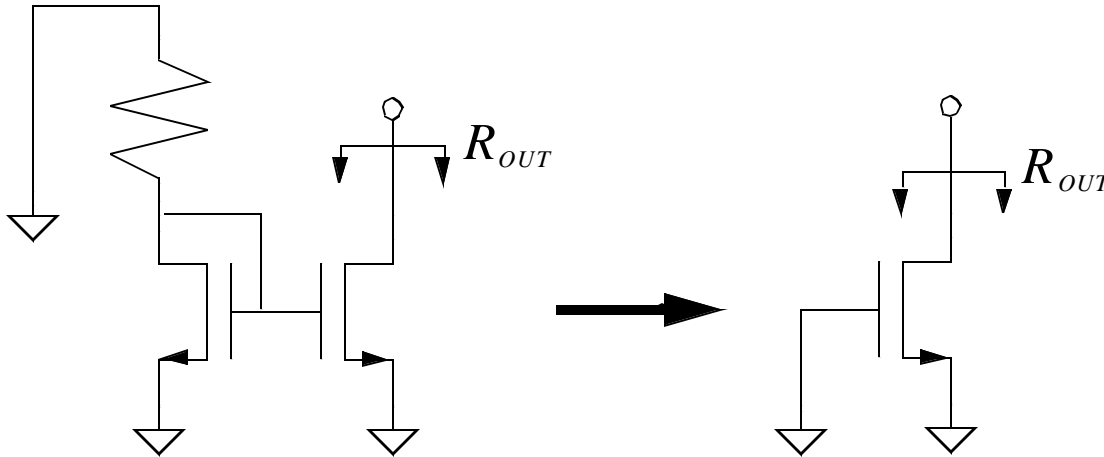


$$R_{OUT} = r_o = \frac{1}{\lambda \cdot I_{OUT}}$$

$$I_{OUT} = 10\mu\text{A}$$

$$\lambda = 0.01$$

$$R_{OUT} = 10\text{M}\Omega$$

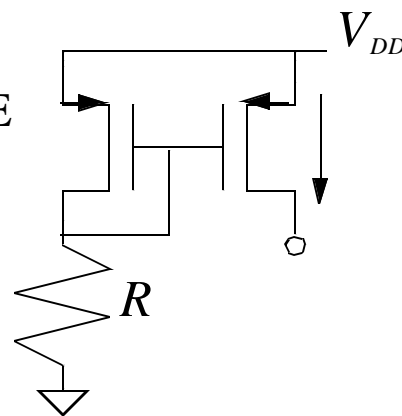
NMOS → current SINK
PMOS → current SOURCE



Simple Source (Cont.)

CS-8

Bipolar :

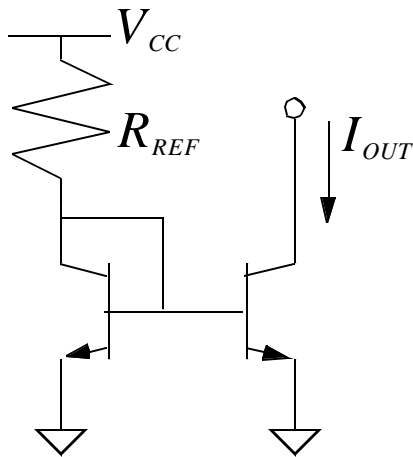


$$I_{OUT} \approx \frac{V_{CC} - V_{BE(ON)}}{R_{REF}}$$

$$V_{BE(ON)} \approx 0.6$$

$$R_{OUT} = \frac{V_A}{I_{OUT}}$$

Simple Source (Cont.)

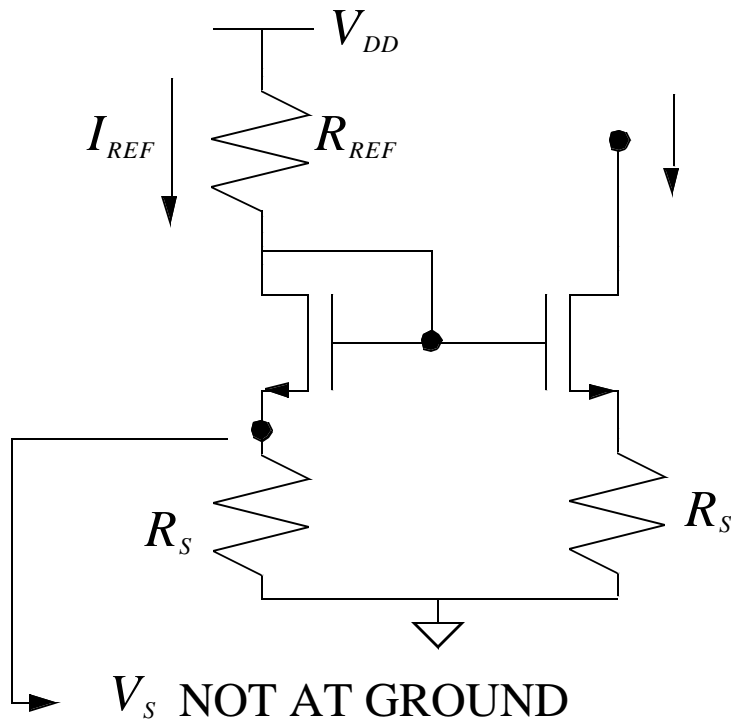How to make R_{OUT} better (ie. larger) ?
Degeneration?



$$V_{OUT} > V_{DSAT} + I_{OUT} \cdot R_S$$


$$R_{OUT} = r_o \cdot [1 + (1 + x) \cdot g_m \cdot R_S]$$

$$V_T = V_{T0} + \gamma \cdot [(V_{SB} + 2 \cdot \phi_f)^{\frac{1}{2}} - (2 \cdot \phi_f)^{\frac{1}{2}}]$$

Not a very efficient way to get high R_{OUT} too much area for resistor.
Better method is to use transistors instead of resistors.

Cascode Source

CS-10

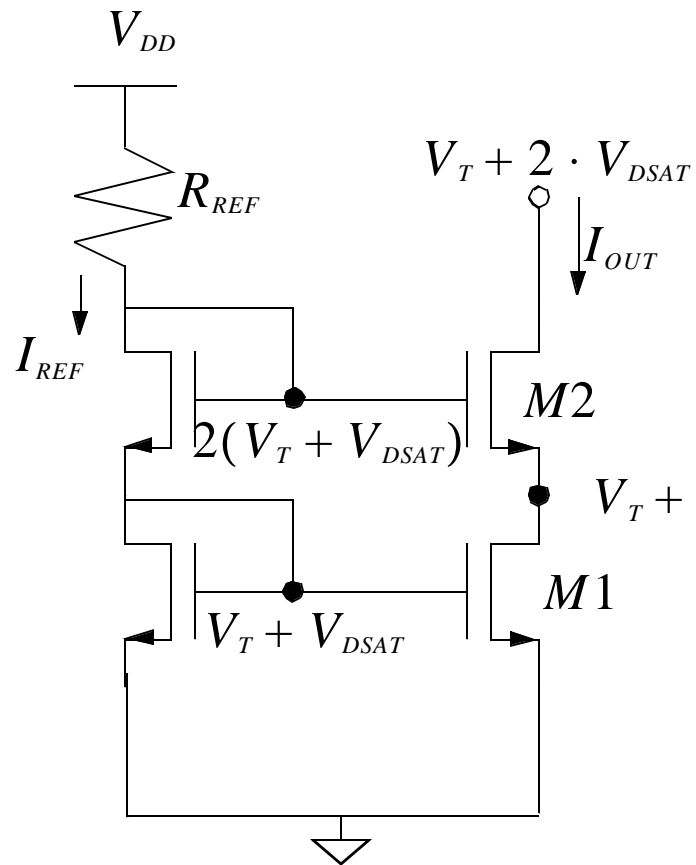

Let $\gamma = 0$ or tie all wells to sources

$V_T + V_{DSAT}$ for EOS


Cascode Source (Cont.)

CS-11

$$V_{GS} = V_T + V_{DSAT}$$

$$\Delta V = \left(\frac{2 \cdot I_{DS}}{k' \cdot \frac{W}{L}} \right)^{\frac{1}{2}}$$

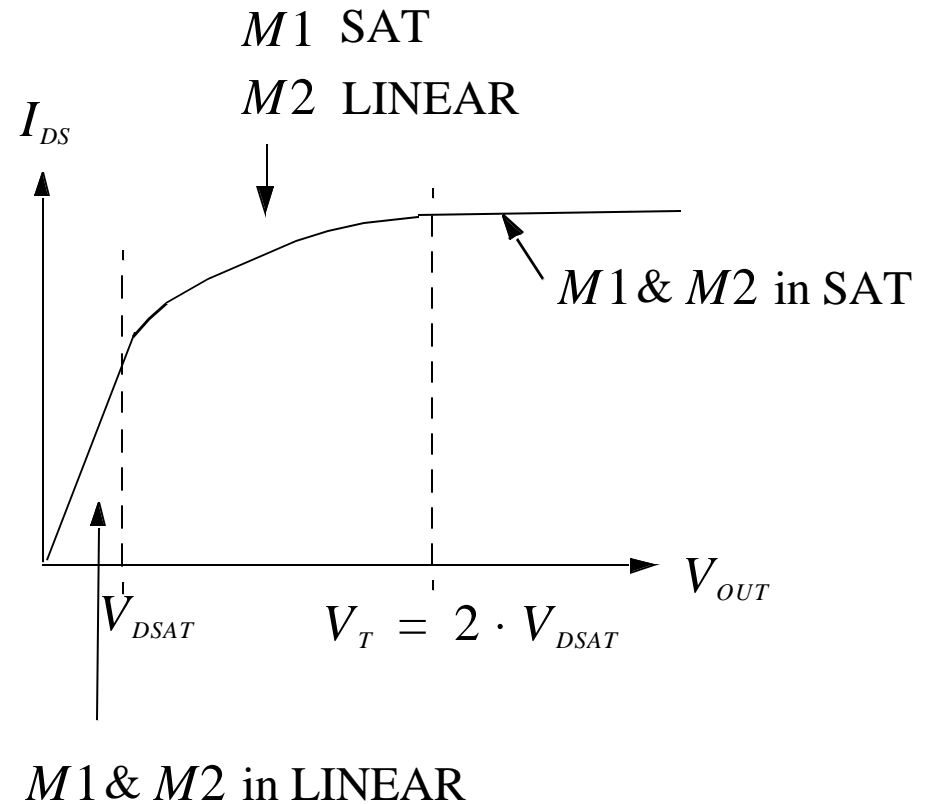
$$I_{REF} = \frac{V_{DD} - 2 \cdot (V_T - V_{DSAT})}{R_{REF}}$$



Cascode Source (Cont.)

CS-12

Rout for Cascode Source :

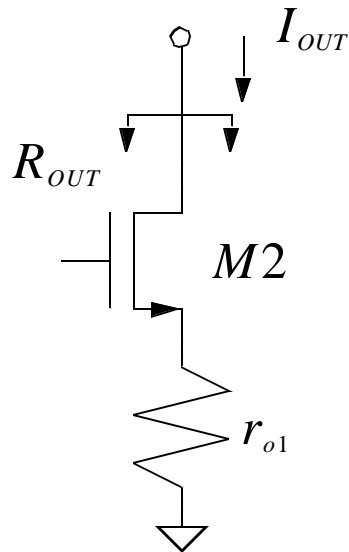

$$\lambda = 0.01$$

$$\gamma = 0$$

$$I_{DS} = 10\mu\text{A}$$

$$\frac{W}{L} = 5$$

$$R_{OUT} = r_{o2} \cdot [1 + (1 + \chi_2) \cdot g_{m2} \cdot r_{o1}]$$

$$\approx (1 + \chi_2) \cdot g_{m2} \cdot r_{o1} \cdot r_{o2}$$

$$r_o = \frac{1}{\lambda \cdot I_{DS}} \quad g_{m2} = \left(2 \cdot k' \cdot \frac{W}{L} \cdot I_{DS}\right)^{\frac{1}{2}} \approx 10^{-4}$$

$$R_{OUT} \approx 10^{-4} \cdot \left(\frac{1}{0.1 \cdot 10^{-5}}\right)^2 \approx 10^{10} \Omega$$


$$g_{m2} = \frac{2 \cdot I_{OUT}}{V_{DSAT}} \quad V_{DSAT} \approx 0.2V$$

$$R_{OUT} = \frac{(1 + \chi_2)}{\lambda^2} \cdot \frac{2}{(V_{DSAT}) \cdot (I_{OUT})}$$

Cascode Source (Cont.)

CS-13

Triple Cascode :

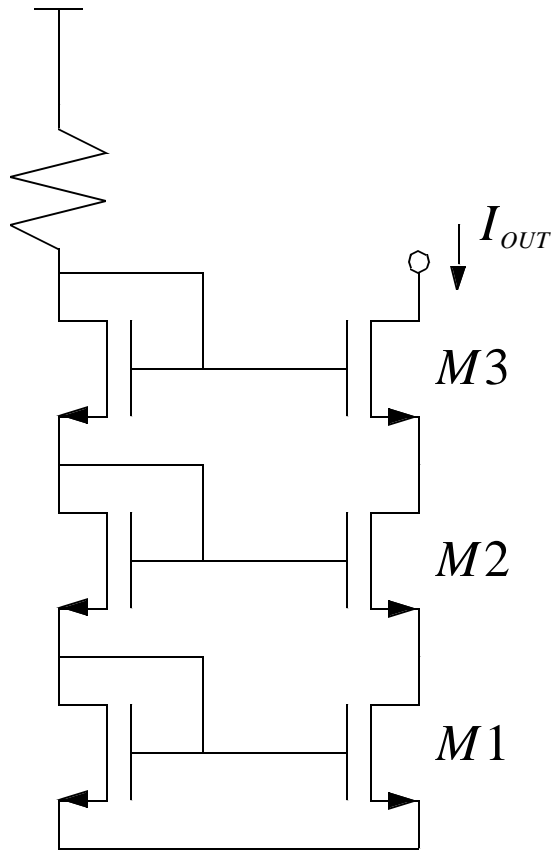

$$R_{OUT} = (1 + \chi_2) \cdot (1 + \chi_3) \cdot g_{m2} \cdot g_{m3} \cdot r_{o1} \cdot r_{o2} \cdot r_{o3}$$



HUGE!!

Cascode Source (Cont.)

CS-14

Problem with Cascode is the $V_T + 2 \cdot V_{DSAT}$ drop required for saturation.


High Swing Cascode is the solution

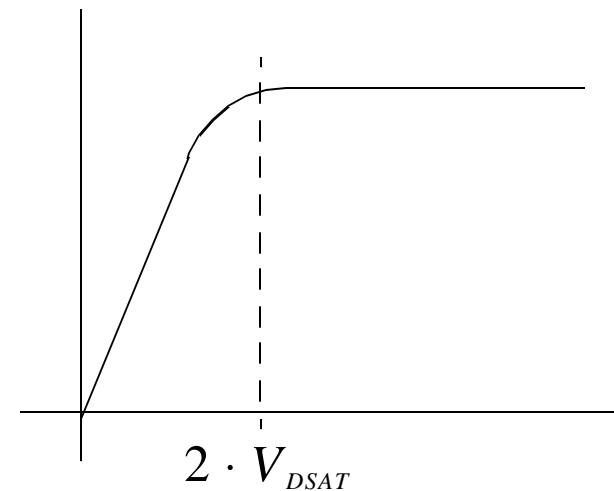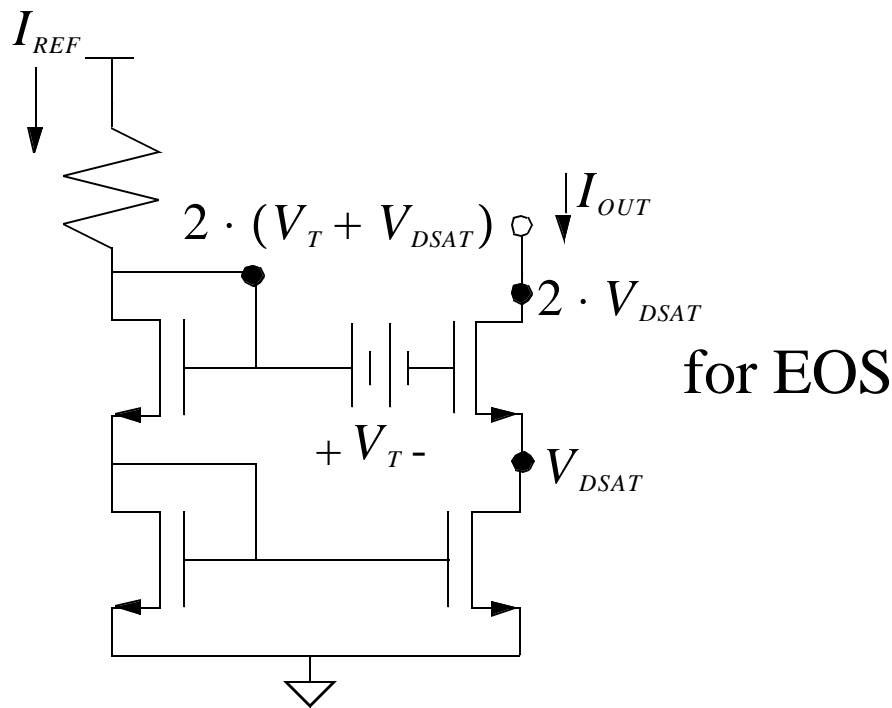

Cascode Source (Cont.)


CS-15

How to implement Battery?

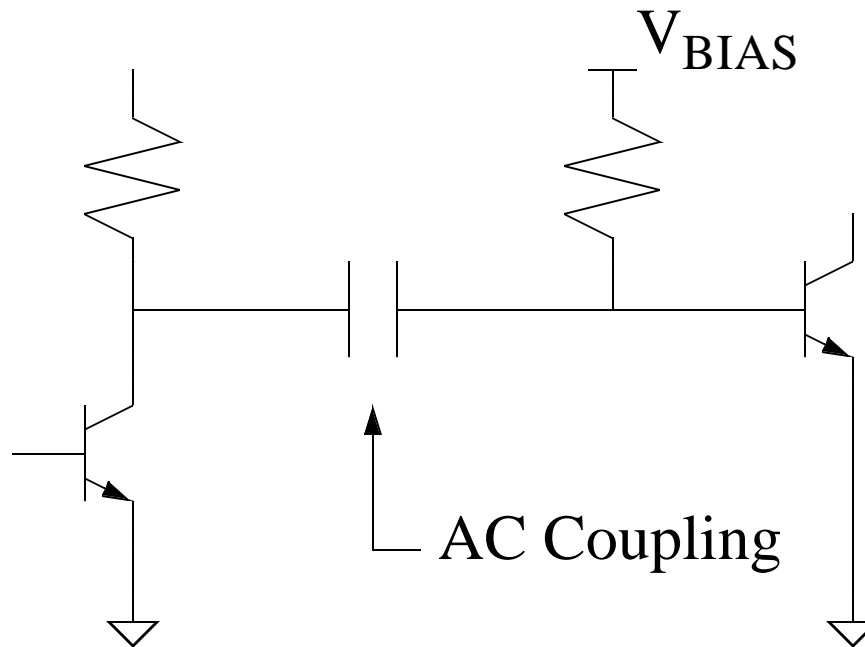

Cascode Source (Cont.)

CS-16

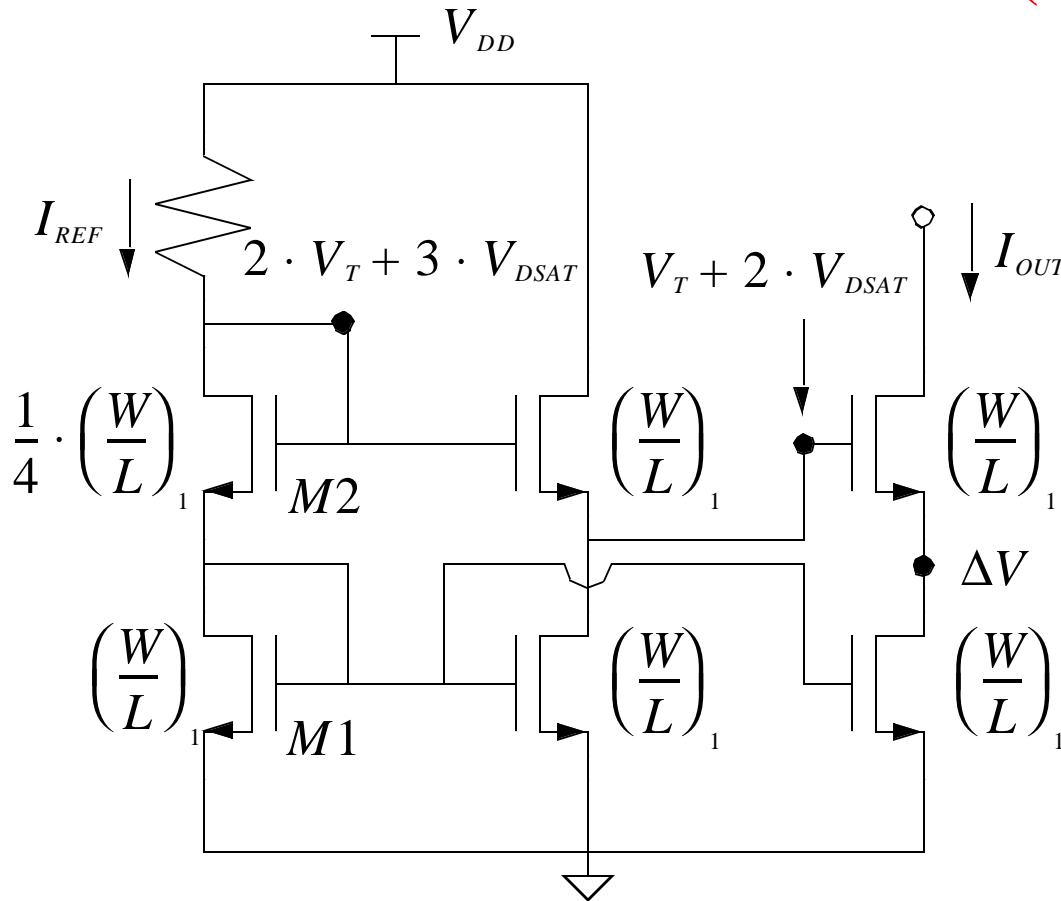

$$V_{DSAT1} = \left(\frac{2 \cdot I_{REF}}{k' \cdot \left(\frac{W}{L}\right)_1} \right)^{\frac{1}{2}}$$


$$V_{DSAT2} = \left(\frac{2 \cdot I_{REF}}{k' \cdot \frac{\left(\frac{W}{L}\right)_1}{4}} \right)^{\frac{1}{2}}$$

$$= 2 \cdot V_{DSAT1}$$

$$\approx 2 \cdot V_{DSAT}$$

Cascode Source (Cont.)

Power Reduction :

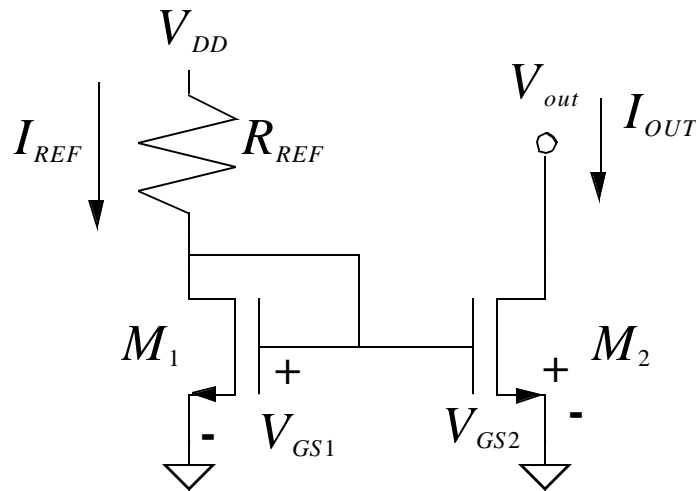


If we want $I_{out} = 1\text{mA}$,

then we can either:

- Set $(W/L)_1 = (W/L)_2$
and $I_{REF} = I_{out}$
- Ratio $(W/L)_1$ and $(W/L)_2$
so that $I_{REF} < I_{out}$, e.g. set
 $(W/L)_2 = 100(W/L)_1$ so that
 $I_{REF} = 10\mu\text{A}$

The tradeoff is between power and area.

Wilson Source

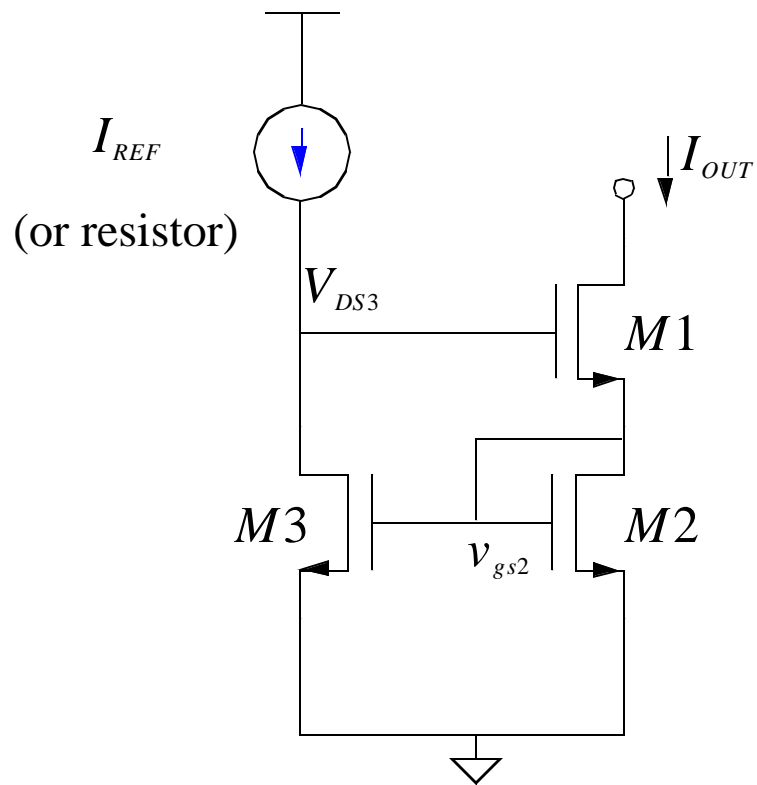

Assume $\gamma = 0$


$$I_{OUT} = I_{REF}$$

$$V_{DS3} = 2 \cdot (V_T + V_{DSAT})$$

Equivalent to Cascode

Wilson Source (Cont)

Small Signal Analysis :

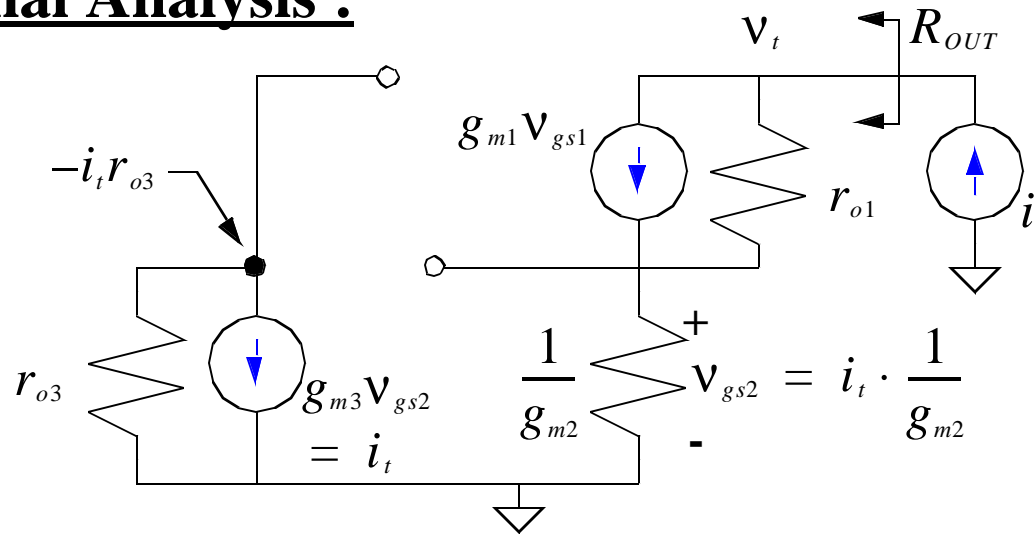

$$g_{m1} = g_{m2} = g_{m3} = g_m$$


$$v_t = i_t \cdot r_o - g_{m1} \cdot v_{gs1} \cdot r_{o1} + i_t \cdot \frac{1}{g_{m2}}$$

$$v_{gs1} = -i_t \cdot r_{o3} - i_t \cdot \frac{1}{g_{m2}}$$

$$v_t = i_t \cdot (r_{o1} + g_m \cdot r_{o1} \cdot r_{o3}) \quad ; \quad R_{OUT} = r_{o1} \cdot (1 + g_m \cdot r_{o3})$$

Wilson Current Source

CS-21

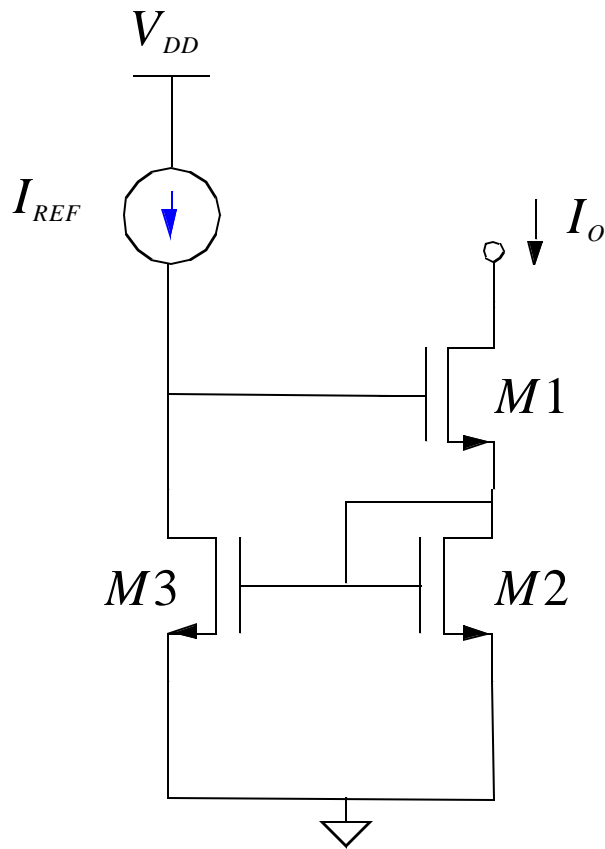

$$I_{DS1} = \frac{1}{2} \cdot \mu \cdot C_{ox} \cdot \frac{W}{L} \cdot (V_{GS} - V_T)^2 \cdot (1 + \lambda \cdot V_{DS})$$

with $\lambda = 0$

$$I_O = I_{REF}$$

assuming same W/L and


$$V_{GS3} = V_{GS2}$$

Wilson Current Source (Cont)

CS-22

R_{out} :

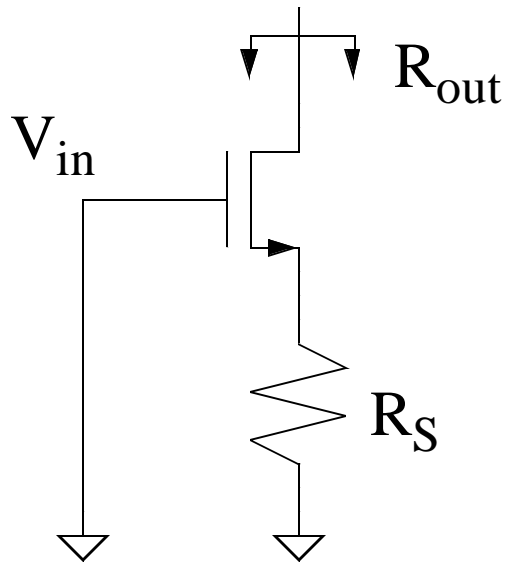For this we must apply the small signal analysis,
it is not correct to calculate R_{out} as for a common source
with degeneration :




NO!

$$R_{OUT} = r_o \cdot (1 + g_m \cdot R_S)$$


Wilson Current Source (Cont)

CS-23

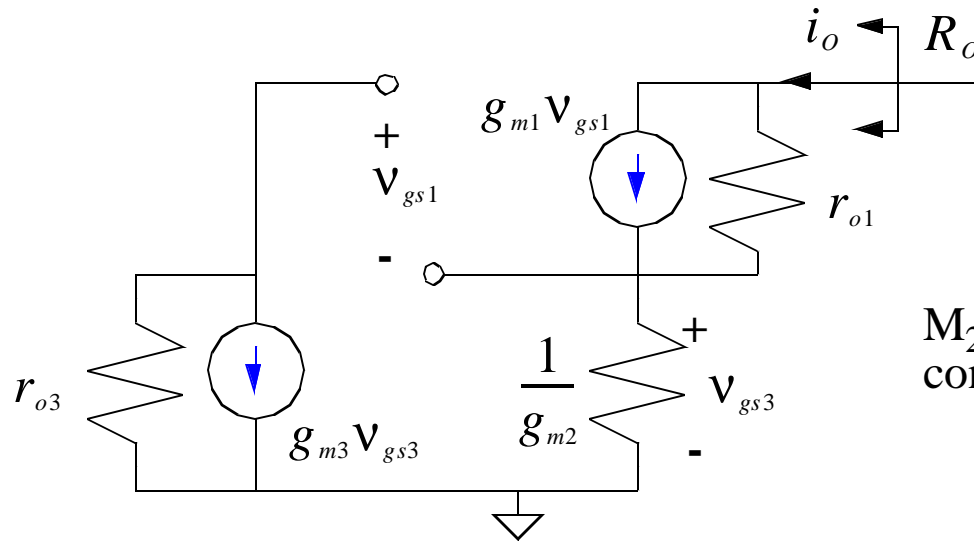


assume $g_{m1} = g_{m2} = g_{m3} = g_m$

M_2 diode connected :

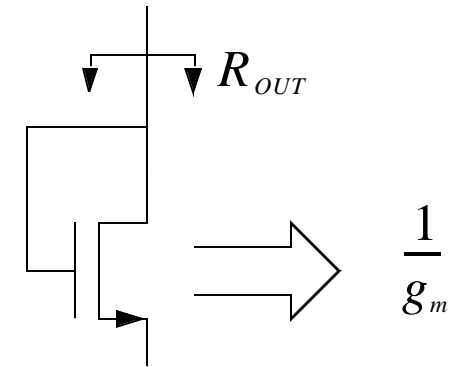

$$i_o = g_m \cdot v_{gs1} + \frac{v_o - v_{gs3}}{r_{o1}}$$
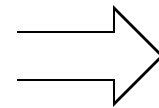
$$g_m \cdot v_{gs1} + \frac{v_o - v_{gs3}}{r_{o1}} = v_{gs3} \cdot g_{m2}$$




$$\frac{v_o}{i_o} = r_{o1} \cdot (2 + g_m \cdot r_{o3})$$

$$\frac{v_{gs1} + v_{gs3}}{r_{o3}} + g_m \cdot v_{gs3} = 0$$

Wilson Current Source (Cont)

CS-24

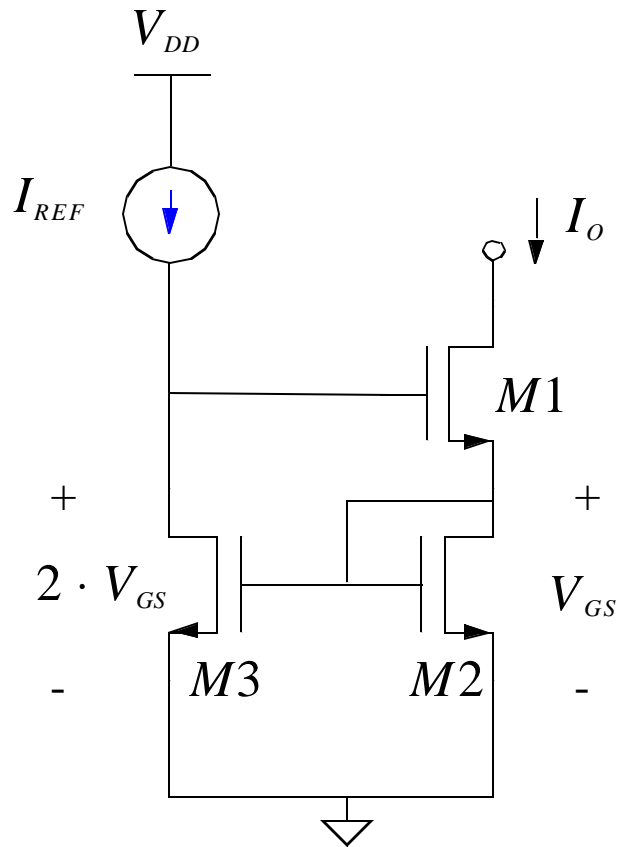

$$I_{DS1} = \frac{1}{2} \cdot \mu \cdot C_{ox} \cdot \frac{W}{L} \cdot (V_{GS} - V_T)^2 \cdot (1 + \lambda \cdot V_{DS})$$

with $\lambda \neq 0$

$$V_{DS2} = V_{GS2} = V_{GS}$$

$$V_{DS3} = 2 \cdot V_{GS}$$


$$\frac{I_{DS2}}{I_{DS3}} = \frac{1 + \lambda \cdot V_{DS2}}{1 + \lambda \cdot V_{DS3}} = \frac{1 + \lambda \cdot V_{GS}}{1 + 2 \cdot \lambda \cdot V_{GS}}$$

$$I_O \neq I_{REF}$$

Wilson Current Source (Cont)

CS-25

To solve the matching problem,

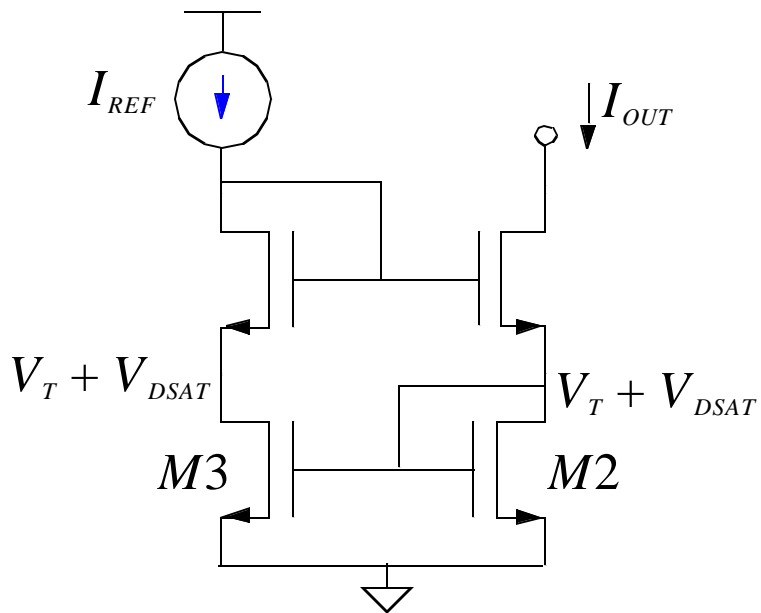


$$I_O = I_{REF}$$

$$R_o = \text{same as before}$$

Widlar Current Source

CS-26

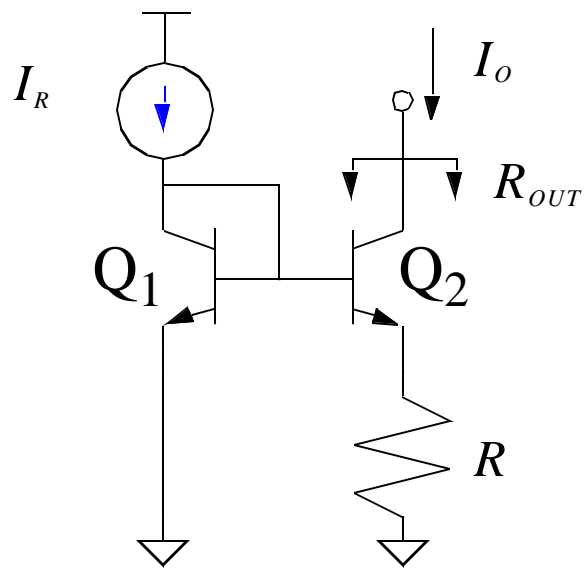

$$R_{OUT} =$$

for emitter degenerated BJT

$$R_{OUT} = r_o \cdot [1 + g_m \cdot (R \parallel r_\pi)]$$

$$I_O =$$

$$V_{BE1} = V_{BE2} + I_O \cdot R$$

for BJT

$$V_{BE} = V_T \cdot \ln \frac{I_C}{I_S} \quad \text{so,}$$


$$V_T \cdot \ln \frac{I_R}{I_{S1}} = V_T \cdot \ln \frac{I_O}{I_{S2}} + I_O \cdot R$$

$$I_O \cdot R = V_T \cdot \ln \left(\frac{I_R}{I_O} \cdot \frac{I_{S2}}{I_{S1}} \right)$$

$$I_O = \frac{V_T}{R} \cdot \ln \frac{I_R}{I_O} \quad \text{solve iteratively}$$

Low Current Bias Circuit (bipolar)

CS-27

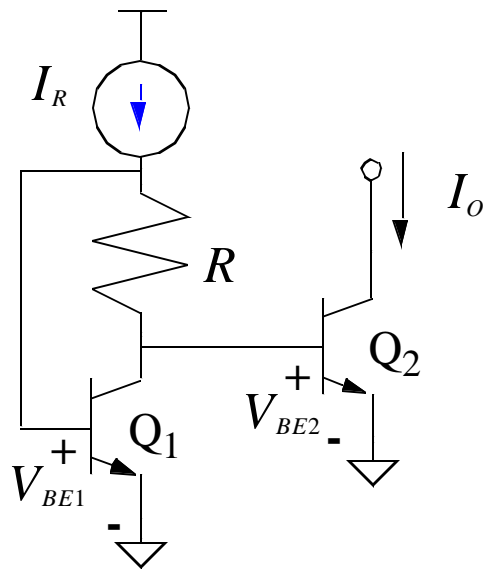

Very low $I_o \sim$ nanoamps

$$V_{BE1} = V_{BE2} + I_R \cdot R$$

$$V_T \cdot \ln \frac{I_R}{I_{S1}} = V_T \cdot \ln \frac{I_o}{I_{S2}} + I_R R$$

$$\text{let } I_{S1} = I_{S2}$$

$$I_o = I_R \cdot \exp\left(-\frac{I_R \cdot R}{V_T}\right)$$


$$\text{for } I_R = 10\mu\text{A} \quad R = 12\text{k}\Omega$$

$$I_o = 100\text{nA}$$

allows low I_o with reasonable values of R

$$R_{OUT} = r_{o2}$$

Supply Independent Biasing

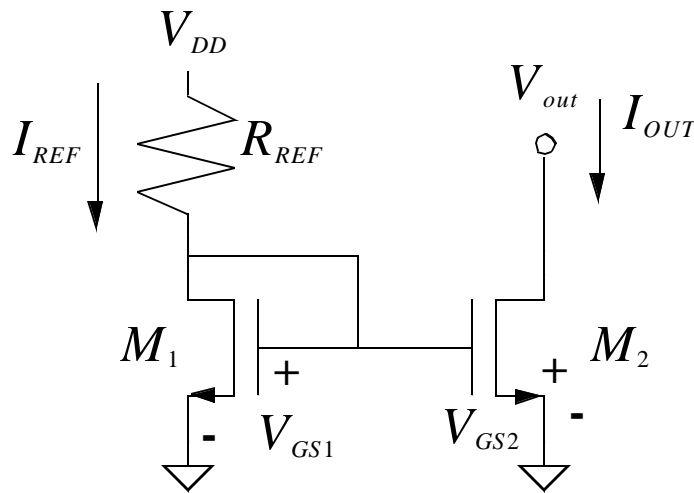

$$I_{OUT} = I_{REF}$$


$$I_{REF} = \frac{V_{DD} - V_{GS}}{R}$$

Hence, I_{REF} depends on the supply voltage V_{DD} . If the supply is a battery or similar device, then this will change over time, causing the reference current to also vary with time

Supply Independent Biasing (Cont.)

CS-29

V_t - Referenced Self-Biased Circuit :

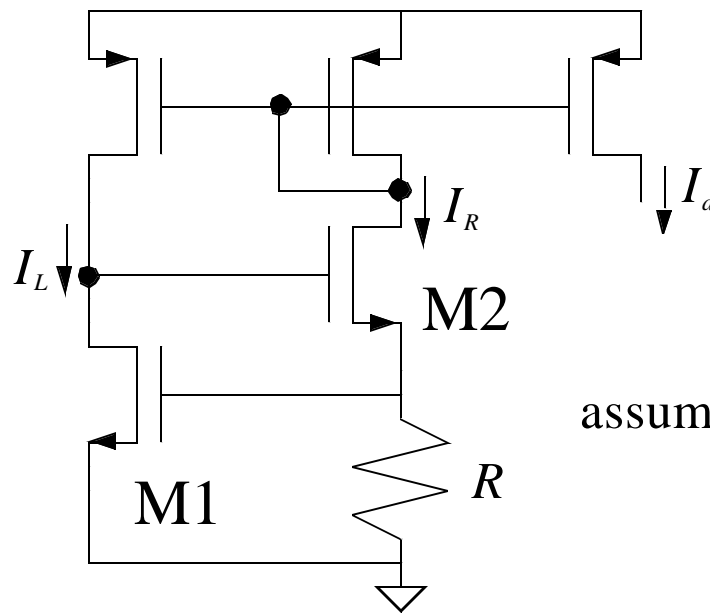

$$V_{GS1} = I_R \cdot R = V_{DSAT}$$

$$= \sqrt{\frac{2 \cdot I_L}{\mu \cdot C_{ox} \cdot \left(\frac{W}{L}\right)_1}} + V_{T1}$$

assume $\left(\frac{W}{L}\right)_1 \gg 1$, V_{dsat} is then negligible


$$I_L = I_R$$

$$I_R \approx \frac{V_{T1}}{R}$$


$$I_O = I_R = \frac{V_{T1}}{R}$$

Supply Independent Biasing (Cont.)

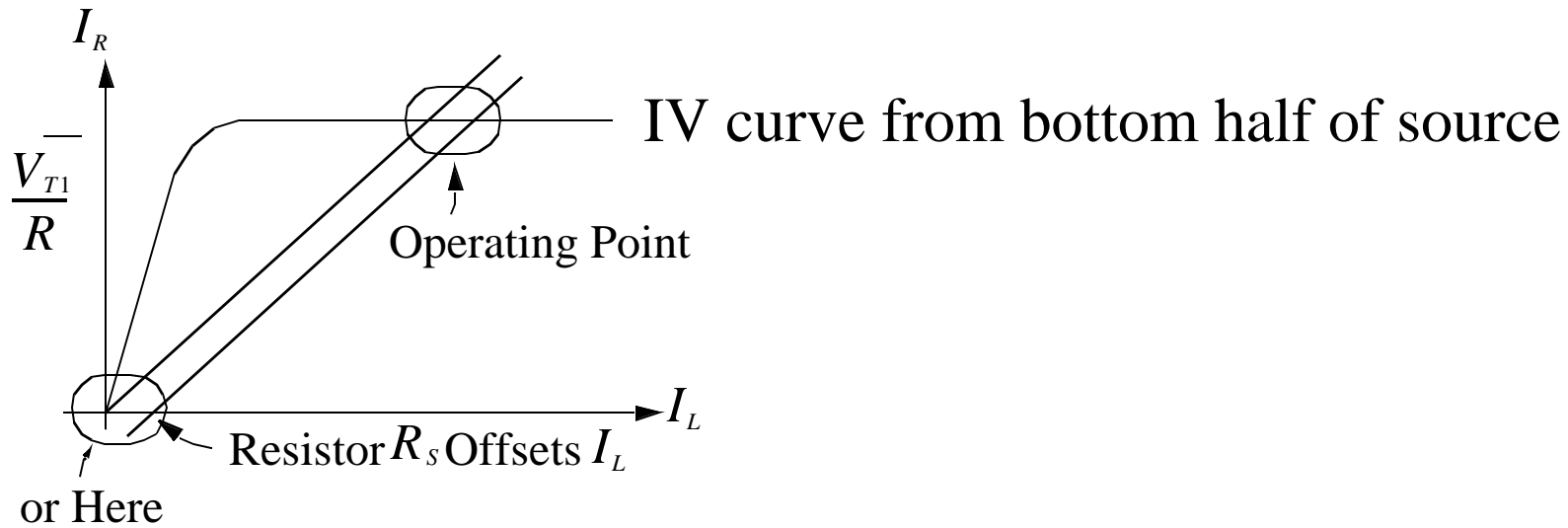For most self-biased circuits, there is a startup problem:



Soln : add R_S to top mirror

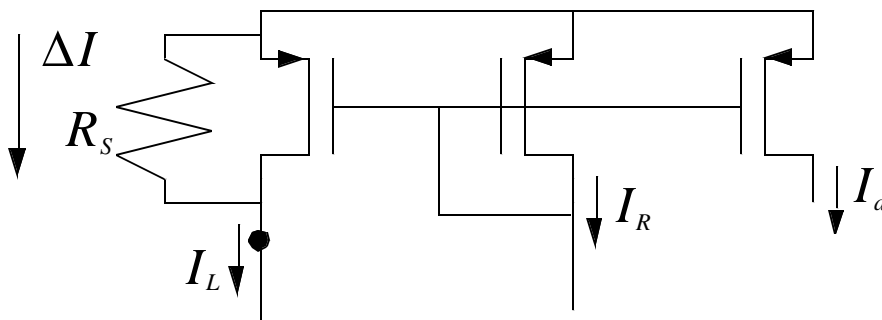

$$I_L = I_R + \Delta I$$

Supply Independent Biasing (Cont.)

CS-32

With Temperature Fluctuation

$$TC = \text{parts per million/degree C} = \text{ppm}/^{\circ}\text{C} = \frac{\left(\frac{\Delta I}{I}\right)}{\Delta T} = \left(\frac{1}{I_{OUT}} \cdot \frac{\partial I_{OUT}}{\partial T}\right)$$


$$I_{OUT} = \frac{V_{EB1}}{R}$$

$$\frac{\partial I_{OUT}}{\partial T} = \frac{1}{R} \cdot \frac{\partial V_{EB}}{\partial T} - \frac{V_{EB}}{R^2} \cdot \frac{\partial R}{\partial T}$$

$$TC = \frac{1}{V_{EB}} \cdot \frac{\partial V_{EB}}{\partial T} - \frac{1}{R} \cdot \frac{\partial R}{\partial T}$$

Supply Independent Biasing (Cont.)

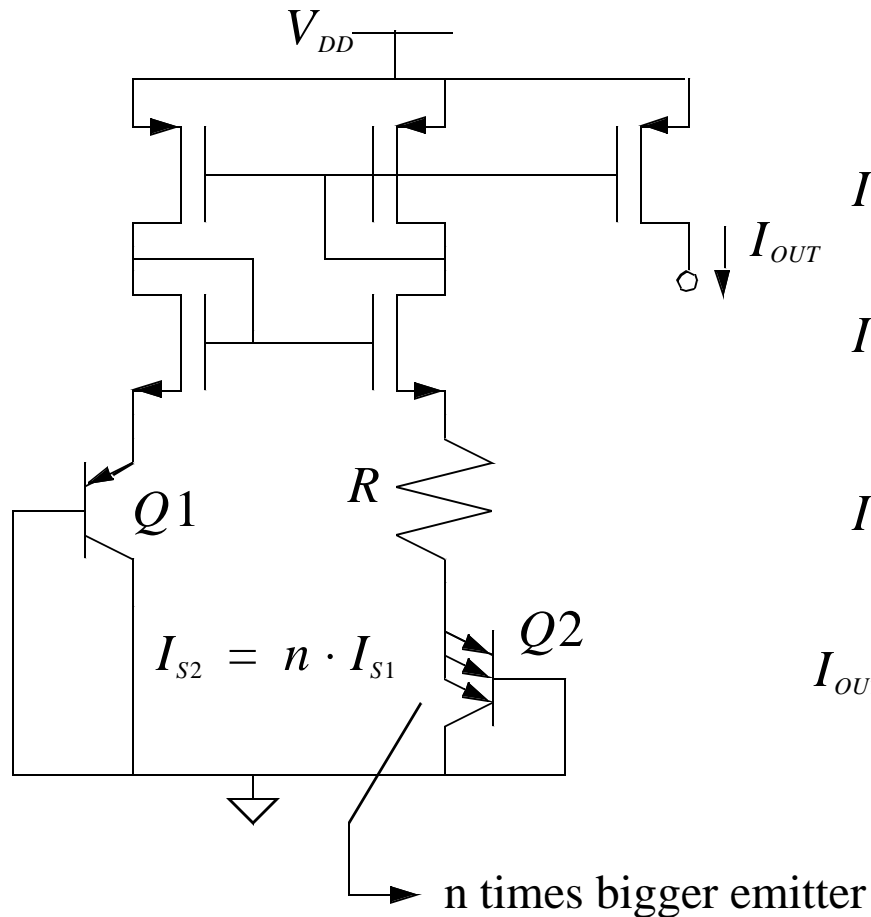V_{thermal} referenced Self-Biased Circuit :



$$I_{OUT} \cdot R + V_{EB2} = V_{EB1}$$


$$I_{OUT} \cdot R + V_T \cdot \ln\left(\frac{I_{OUT}}{n \cdot I_{S1}}\right) = V_T \cdot \ln\left(\frac{I_{OUT}}{I_{S1}}\right)$$

$$I_{OUT} = \frac{V_T}{R} \cdot \ln(n)$$

$$I_{OUT} \cdot R = V_{Thermal} \cdot \ln(n)$$

Cascode - Self-Biased Source

CS-34

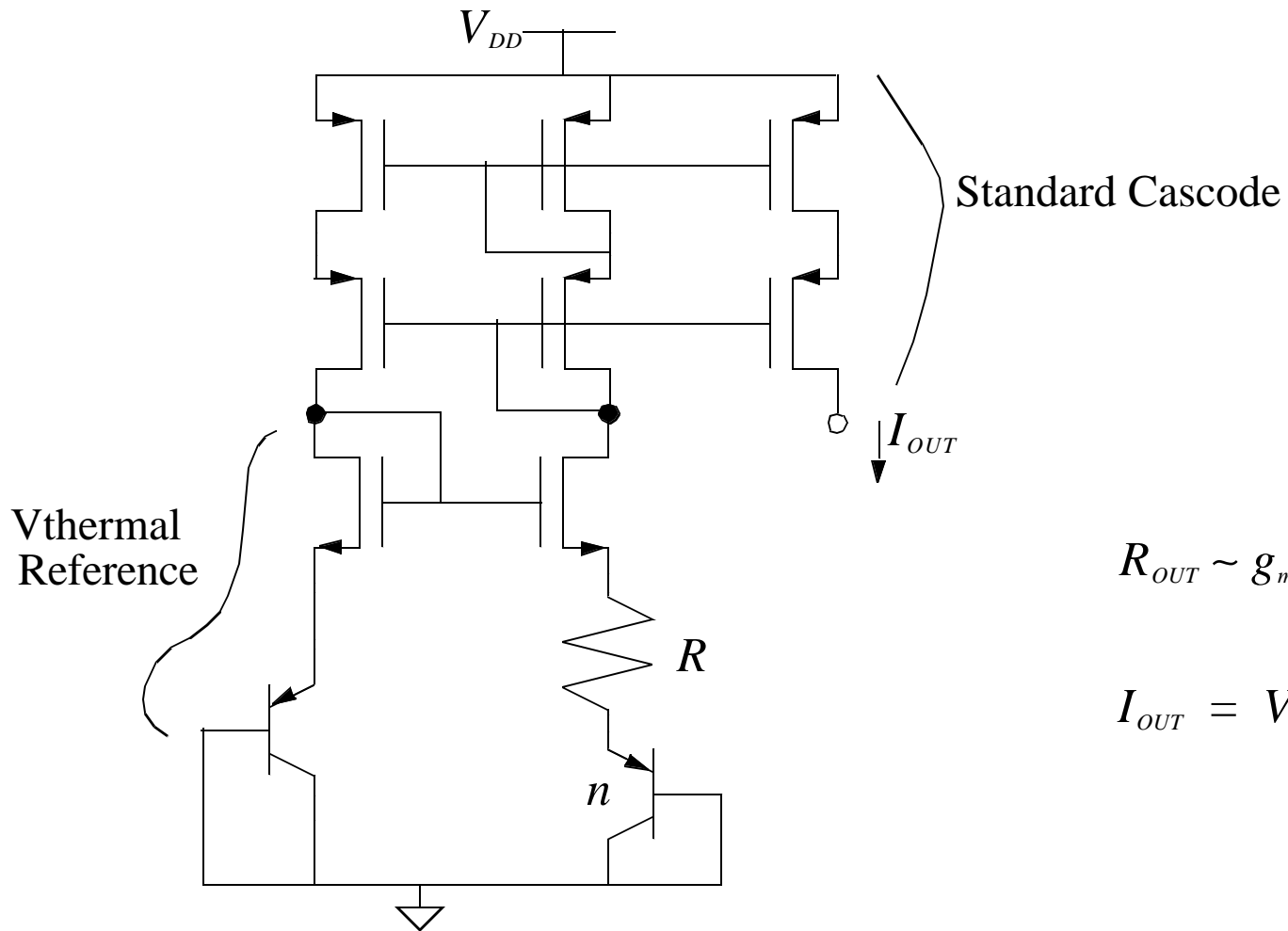


$$R_{OUT} \sim g_m \cdot r_o^2$$

$$I_{OUT} = V_T \cdot \frac{\ln(n)}{R}$$

Current Source Load

CS-35

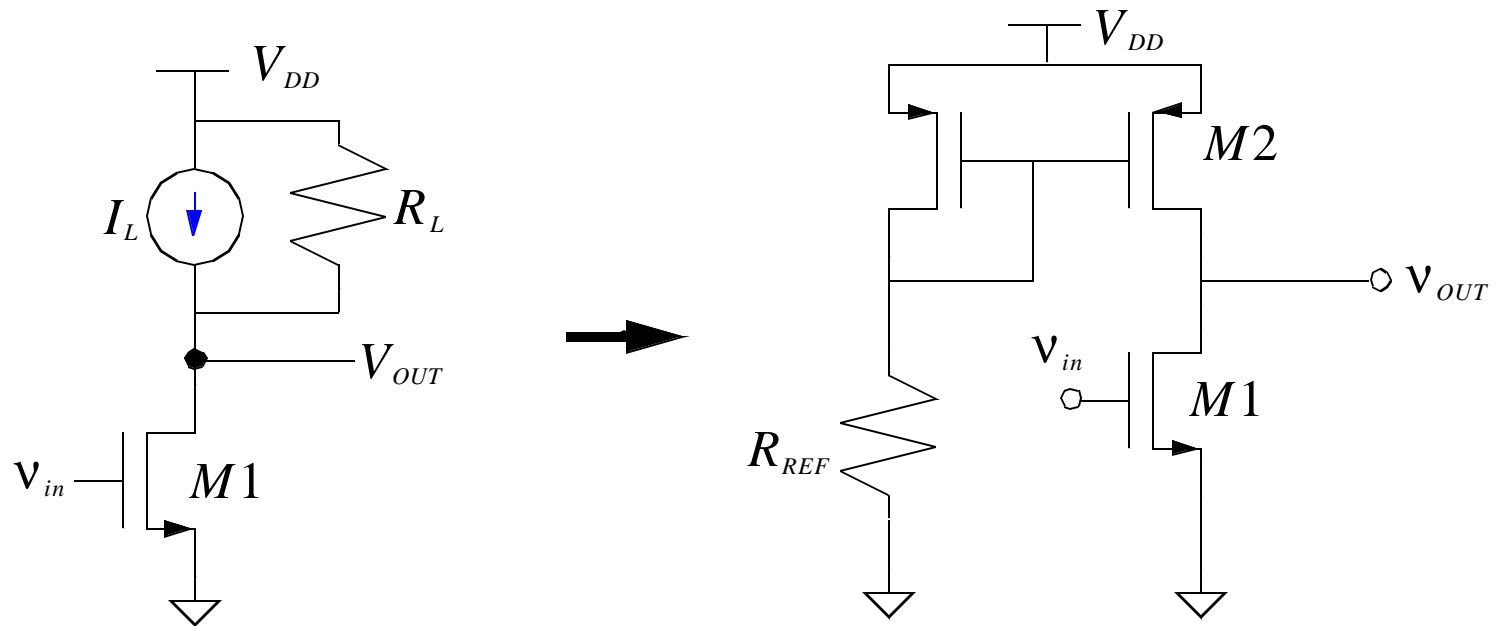

or any other current source

Current Source Load (Cont.)

CS-36

$$R_L = r_{o2} = \frac{1}{\lambda_p \cdot I_L} \quad r_{o1} = \frac{1}{\lambda_n \cdot I_L}$$

$$R_{OUT} = R_L \parallel r_{o1} = r_{o2} \parallel r_{o1}$$

$$A_v = -g_m \cdot (r_{o1} \parallel r_{o2}) \quad \text{If } \lambda_n = \lambda_p$$


$$g_m = \frac{2 \cdot I_{DS}}{V_{DSAT}} \quad \longleftarrow \quad \text{Handy Formula}$$

$$A_v = -\frac{2 \cdot I_L}{V_{DSAT}} - \frac{1}{2 \cdot \lambda \cdot I_L} = -\frac{1}{\lambda \cdot V_{DSAT}} \propto \frac{1}{I_L^{\frac{1}{2}}}$$

Differential Pair with Current Source Load

CS-37

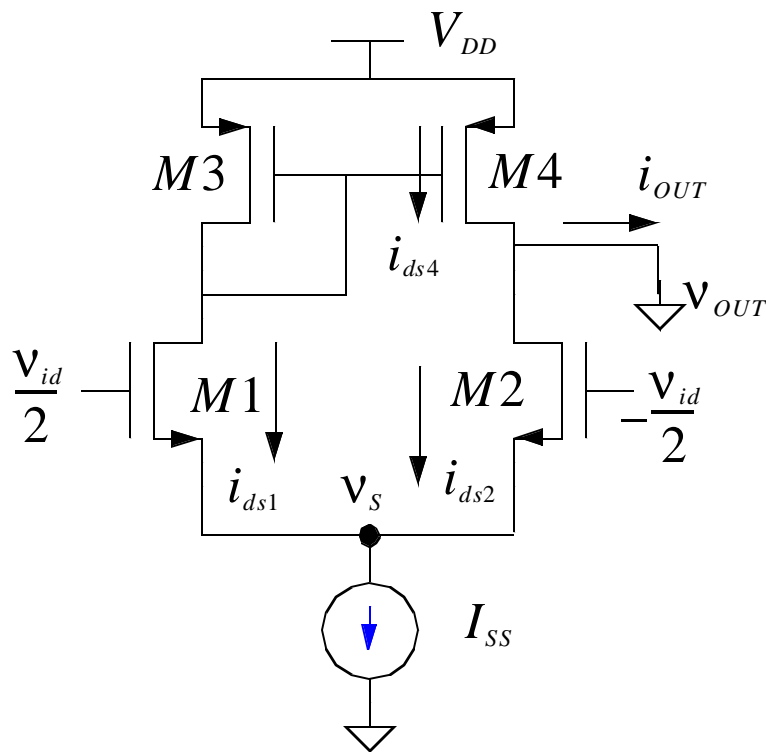Double to single ended conversion without loss :



Calculate GM

$$\left(\frac{v_{id}}{2} - v_s\right) \cdot g_m = i_{ds1} = i_{ds3} = i_{ds4}$$

$$i_{ds2} = \left(-\frac{v_{id}}{2} - v_s\right) \cdot g_m$$

$$i_{OUT} = i_{ds4} - i_{ds2} = \left(\frac{v_{id}}{2} - v_s\right) \cdot g_m - \left(-\frac{v_{id}}{2} - v_s\right) \cdot g_m$$

$$i_{OUT} = g_m \cdot v_{id}$$


$$GM = \frac{i_{OUT}}{v_{id}} = g_m$$

by current
source connection




Differential Pair with Current Source Load (Cont.) CS-38

ROUT for Differential Pair :

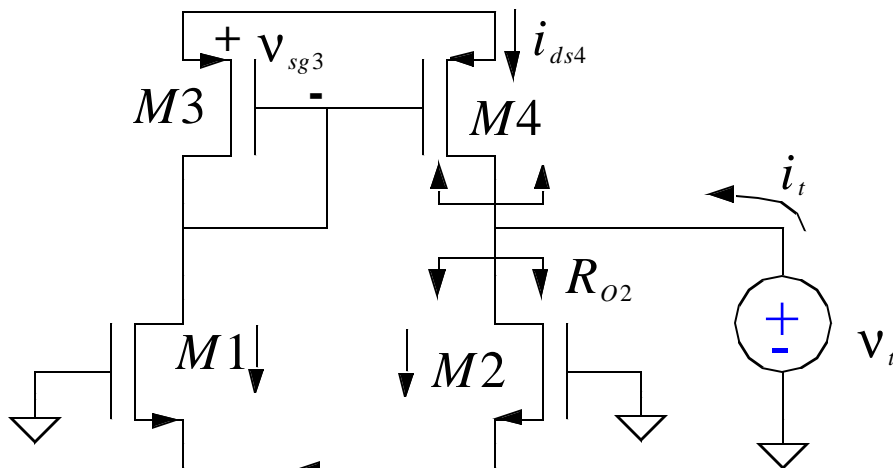

$$R_{s2} = \frac{1}{g_m(1 + \chi)}$$
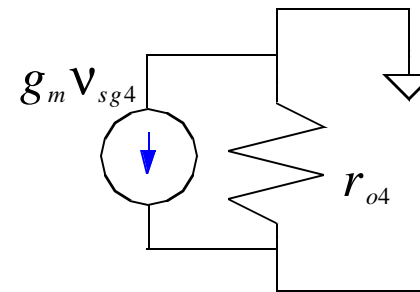
$$R_{o2} = r_{o2} \cdot [1 + (1 + \chi) \cdot g_m \cdot R_{s2}] = r_{o2} \cdot [2]$$



Differential Pair with Current Source Load (Cont.)

CS-39

$$i_t = i_{ds2} - i_{ds4}$$

$$i_{ds4} = g_m \cdot v_{sg4} - \frac{v_t}{r_{o4}}$$

$$v_{sg4} = v_{sg3} = \left(\frac{1}{g_m}\right) \cdot i_{ds1} = -i_{ds2} \cdot \left(\frac{1}{g_m}\right)$$

$$-g_m \cdot v_{sg4} = \cancel{g_m} \cdot \frac{v_t}{2 \cdot r_{o2}} \cdot \frac{1}{\cancel{g_m}} = -\frac{v_t}{2 \cdot r_{o2}}$$

$$i_{ds4} = -\frac{v_t}{2 \cdot r_{o2}} - \frac{v_t}{r_{o4}}$$

$$i_t = i_{ds2} - i_{ds4} = \frac{v_t}{2 \cdot r_{o2}} + \frac{v_t}{2 \cdot r_{o2}} + \frac{v_t}{r_{o4}}$$

$$R_{OUT} = \frac{v_t}{i_t} = r_{o2} \parallel r_{o4}$$