

University of California  
Berkeley

College of Engineering  
Department of Electrical Engineering  
and Computer Science

Robert W. Brodersen  
EECS140


Analog Circuit Design

**Lectures**  
**on**  
**OP AMPS**



# Miller Op Amp (Cont.)

OP-2

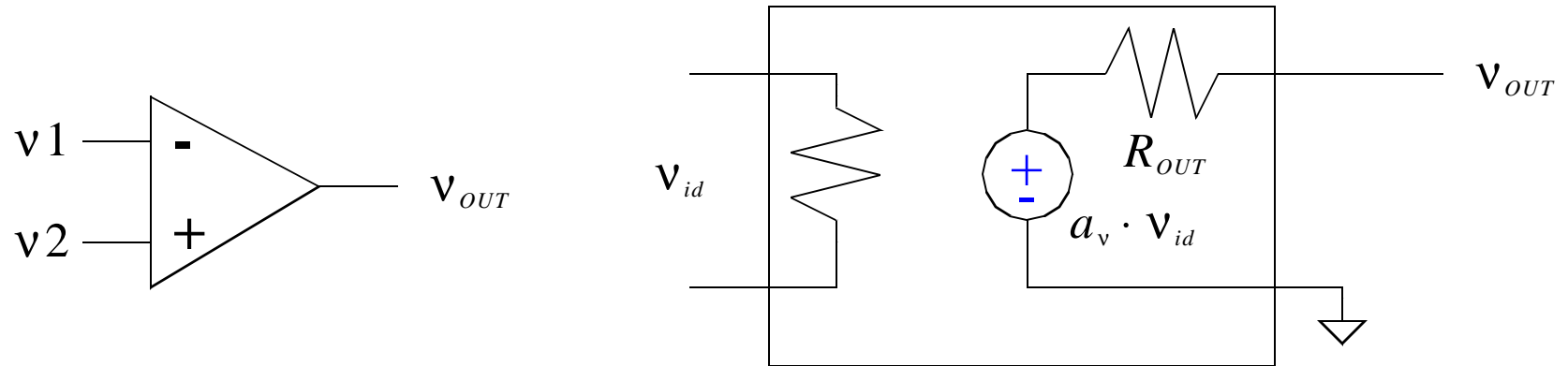

$$R_{id} = \infty$$

$$R_{OUT} = r_{o5} \parallel r_{o6}$$

$$\frac{v_{d2}}{v_{id}} \cdot \frac{v_{OUT}}{v_{d2}} = \frac{v_{OUT}}{v_{id}}$$

$\nearrow$   $g_{m2} \cdot (r_{o2} \parallel r_{o4})$        $\nearrow$   $g_{m5} \cdot R_{OUT}$

## Miller Op Amp (Cont.)

## OP-3

What is the DC voltage at  $V_{d2}$ ?

$$I_{DS1} = I_{DS2} = I_{DS3} = I_{DS4}$$

$$I_{DS3} = \frac{k'}{2} \cdot \frac{W}{L} \cdot (V_{SG3} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD3})$$

$$I_{DS4} = \frac{k'}{2} \cdot \frac{W}{L} \cdot (V_{SG4} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD4})$$

$$I_{DS3} = I_{DS4}$$

$$(V_{SG3} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD3}) = (V_{SG4} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD4})$$

$$V_{SG3} = V_{SG4}$$


~~$$(V_{SG3} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD3}) = (V_{SG3} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD4})$$~~

$$V_{SD3} = V_{SD4} = V_{SG3} = V_T + V_{DSAT3}$$

$$V_{D1} = V_{DD} - V_{SG3} = V_{DD} - V_T - V_{DSAT3} = V_{D2}$$
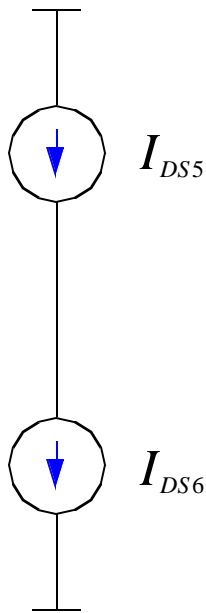
## Miller Op Amp (Cont.)

To set offset at output or 2<sup>nd</sup> stage M5, M6 to near zero,  
set  $I_{DS5} = I_{DS6}$



$$I_{SD5} = \frac{k'}{2} \cdot \left(\frac{W}{L}\right)_5 \cdot (V_{SG5} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD5})$$

$$I_{SD6} = \frac{k'}{2} \cdot \left(\frac{W}{L}\right)_6 \cdot (V_{GS6} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{DS6})$$

Since  $V_{SD4} = V_{SG3} = V_{SG5}$

$$I_{SD5} = I_{DS3} \quad \text{if} \quad \left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_3$$

$$I_{SD6} = \frac{1}{2} \cdot I_{SD13} \quad \text{if} \quad \left(\frac{W}{L}\right)_{13} = 2 \cdot \left(\frac{W}{L}\right)_6$$


then  $I_{DS6} = I_{DS5}$  or,

$$\frac{I_{DS5}}{I_{DS3}} = \frac{\left(\frac{W}{L}\right)_5}{\left(\frac{W}{L}\right)_3} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_{13} / 2} = \frac{2 \cdot \left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_{13}}$$

## Miller Op Amp (Cont.)
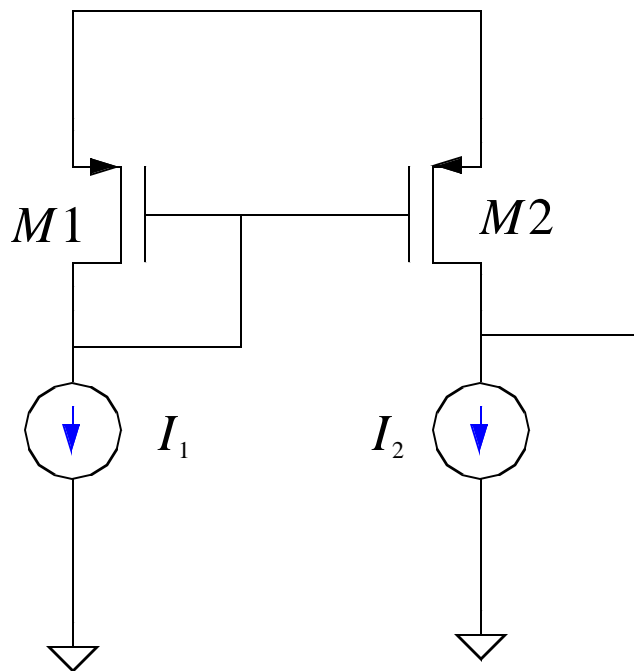
## OP-5

What happens if  $I_1 = \alpha \cdot I_2$



$$\frac{k'}{2} \cdot \left(\frac{W}{L}\right)_1 \cdot (V_{SG1} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD1})$$

$$= \alpha \cdot \frac{k'}{2} \cdot \left(\frac{W}{L}\right)_2 \cdot (V_{SG2} - |V_T|)^2 \cdot (1 + \lambda \cdot V_{SD2})$$

$$1 + \lambda \cdot V_{SD1} = \alpha \cdot (1 + \lambda \cdot V_{SD2})$$

$$V_{SD2} = \frac{\frac{1}{\lambda} + V_{SD1}}{\alpha} - \frac{1}{\lambda}$$

$$\alpha = 1 \quad V_{SD2} = V_{SD1}$$

$$\alpha = \frac{1}{2} \quad V_{SD2} = \frac{100 + V_{SD1}}{1/2} - 100$$

$$\lambda = 0.01 \quad = 100 + 2 \cdot V_{SD1} \quad \text{Big Offset}$$

## Miller Op Amp (Cont.)

OP-6

### Gain :

#### First Stage

$$\frac{V_{ds}}{V_{id}} = -g_{m1} \cdot (r_{o4} \parallel r_{o2})$$

#### Second Stage

$$\frac{V_{OUT}}{V_{d2}} = -g_{m5} \cdot (r_{o6} \parallel r_{o5})$$

#### Overall

$$A_v = g_{m1} \cdot g_{m5} \cdot (r_{o4} \parallel r_{o2}) \cdot (r_{o5} \parallel r_{o6})$$

## Miller Op Amp (Cont.)

$$A_v = \frac{2 \cdot I_{DS1}}{V_{DSAT1}} \cdot \left( \frac{2 \cdot I_{DS5}}{V_{DSAT5}} \right) \cdot \frac{1}{(\lambda_n + \lambda_p) \cdot I_{DS1}} \cdot \frac{1}{(\lambda_n + \lambda_p) \cdot I_{DS5}}$$

$$= \frac{4}{(V_{DSAT1}) \cdot (V_{DSAT5}) \cdot (\lambda_n + \lambda_p)^2}$$

$$A_v = \frac{4}{\left( \frac{2 \cdot I_{SD1}}{k'_n \cdot (W/L)_1} \right)^{\frac{1}{2}} \cdot \left( \frac{2 \cdot I_{DS5}}{k'_p \cdot (W/L)_5} \right)^{\frac{1}{2}} \cdot (\lambda_n + \lambda_p)^2}$$


$$= \frac{2 \cdot (k'_n \cdot k'_p)^{\frac{1}{2}} \cdot \left( \frac{W}{L} \right)_1^{\frac{1}{2}} \cdot \left( \frac{W}{L} \right)_5^{\frac{1}{2}}}{(\lambda_n + \lambda_p)^2 \cdot (I_{SD1} \cdot I_{DS5})^{\frac{1}{2}}}$$

## Miller Op Amp (Cont.)

OP-8

$$R_{OUT} = r_{o5} \parallel r_{o6} = \frac{1}{(\lambda_p + \lambda_n) \cdot I_{DS5}}$$

Add output stage if this is too high.

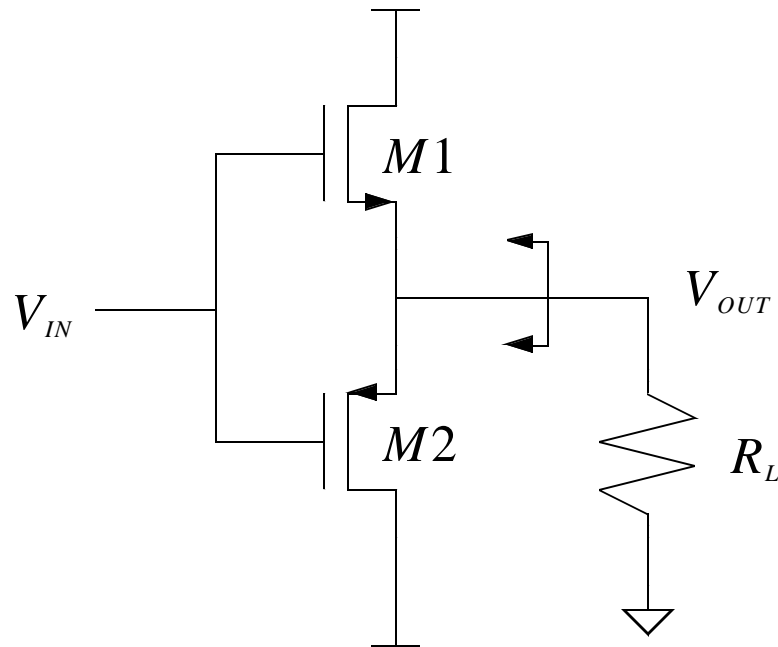

What is the output resistance of this ?

## Miller Op Amp (Cont.)

OP-9

You need to choose an operating point since the  $R_{out}$  is very non-linear.

$$R_{OUT} = \frac{1}{g_{m1}} \Big|_{V_{IN} > V_{Tn}}$$

$$= \frac{1}{g_{m2}} \Big|_{V_{IN} < -|V_{Tp}|}$$

$$g_m = \left( 2 \cdot \frac{W}{L} \cdot k' \cdot I_{DS} \right)^{\frac{1}{2}} = \left( 2 \cdot \frac{W}{L} \cdot k' \cdot I_{OUT} \right)^{\frac{1}{2}}$$


$$= \left( 2 \cdot \frac{W}{L} \cdot k' \cdot \frac{V_{OUT}}{R_L} \right)^{\frac{1}{2}}$$


b

**OP-10**  
**Empty Slide**


OP-11

You could use a level shifter

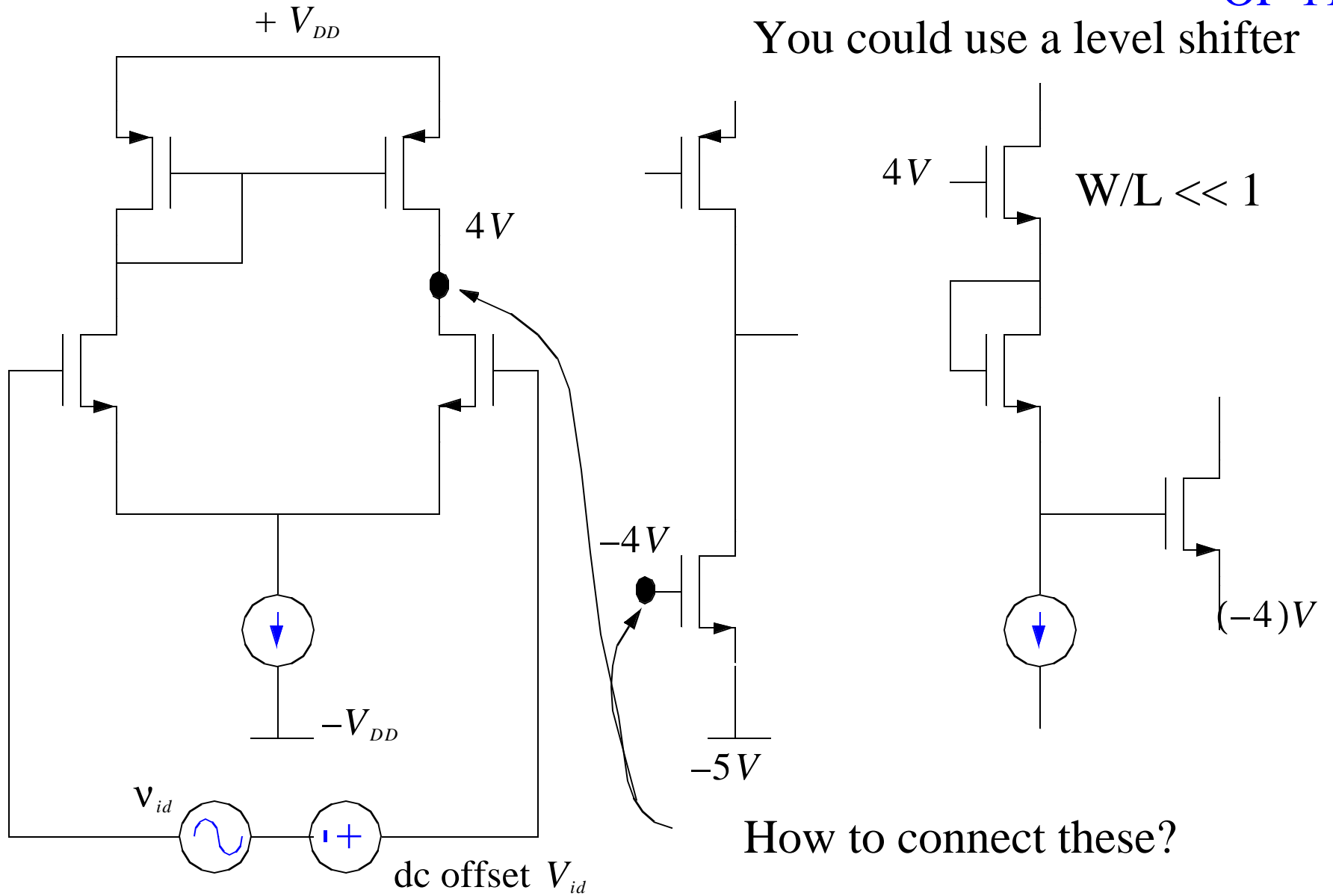

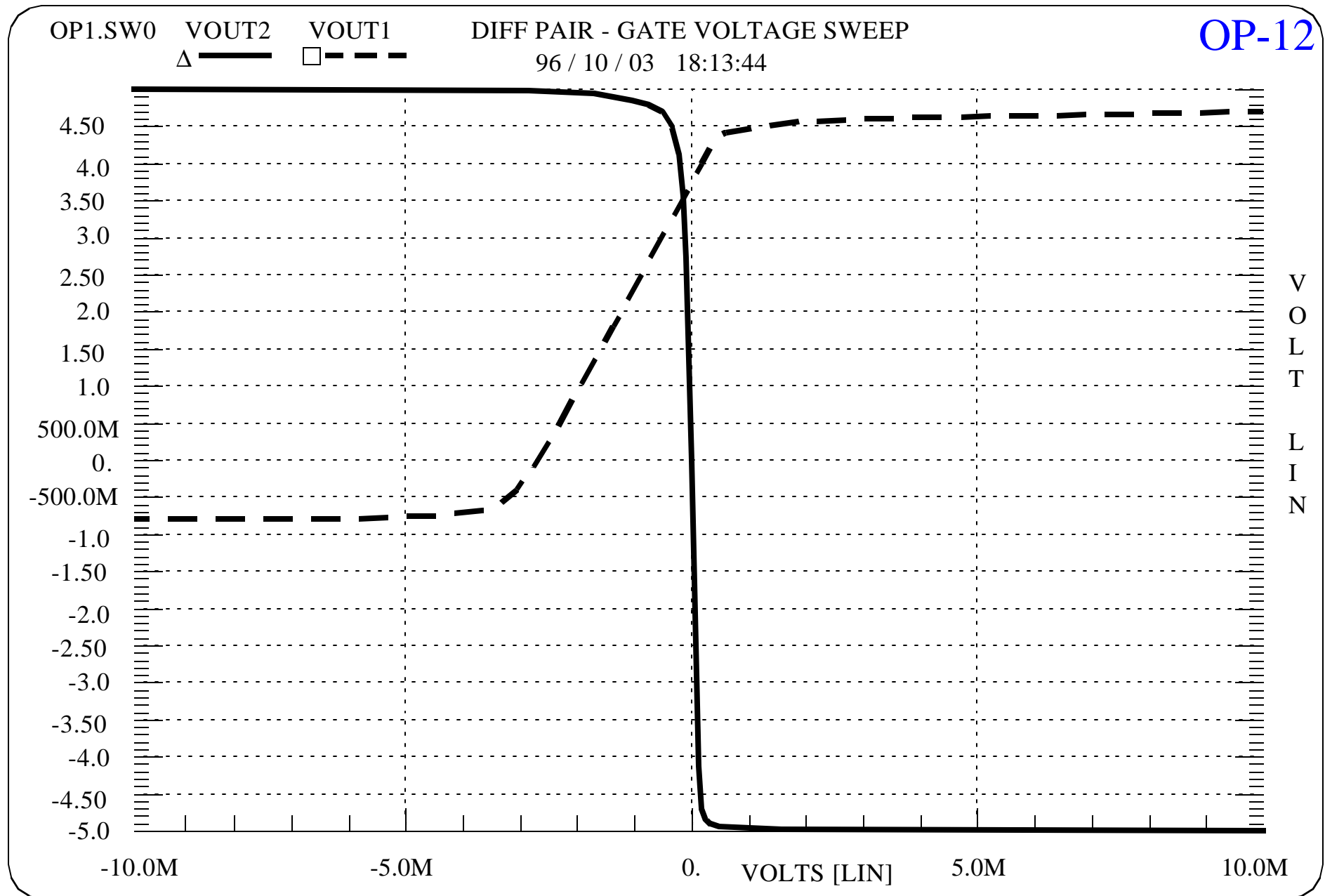

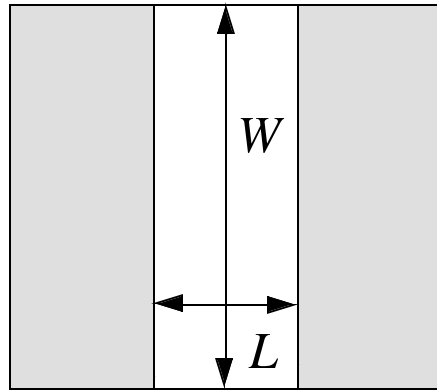
# Area Calculation (L=.5 micron minimum channel Length) OP-13




$$W/L=3$$
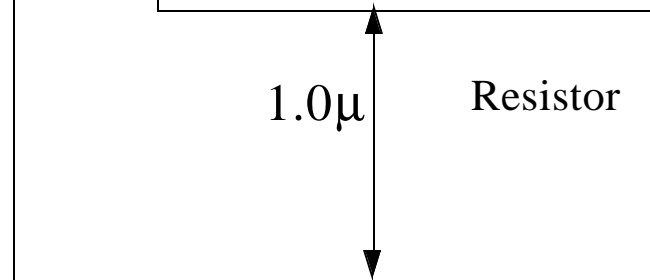
$$\text{Resistor Area} = \# \text{ of squares} * 1.0 \mu^2$$




$$W \times \langle L + 1\mu^2 \rangle \approx \text{TransistorArea}$$

$$1.5\mu \times (0.5 + 1) = 2.25\mu^2$$

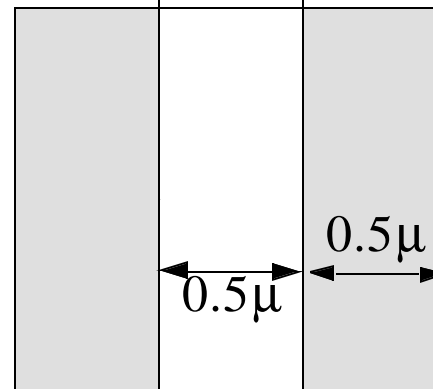

## Sheet Resistance

OP-14

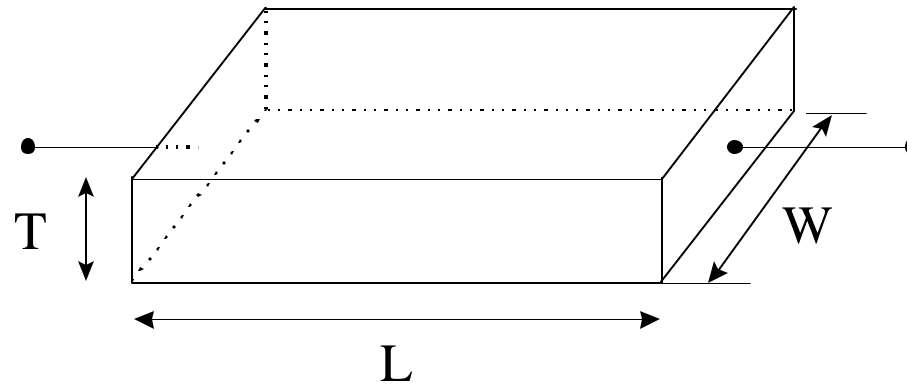


$$\text{Conductance} = \frac{1}{\text{Resistance}} = \frac{W \cdot T}{L} \cdot \sigma \quad \left[ \frac{\text{mhos}}{\text{cm}^3} \right]$$

$$R = \frac{L}{W} \cdot \underbrace{\rho_{\square}}_{\text{ohms}/\square} \quad \rho_{\square} = \sigma \cdot T$$

## Sheet Resistance (Cont.)

## OP-15

### TOP VIEW

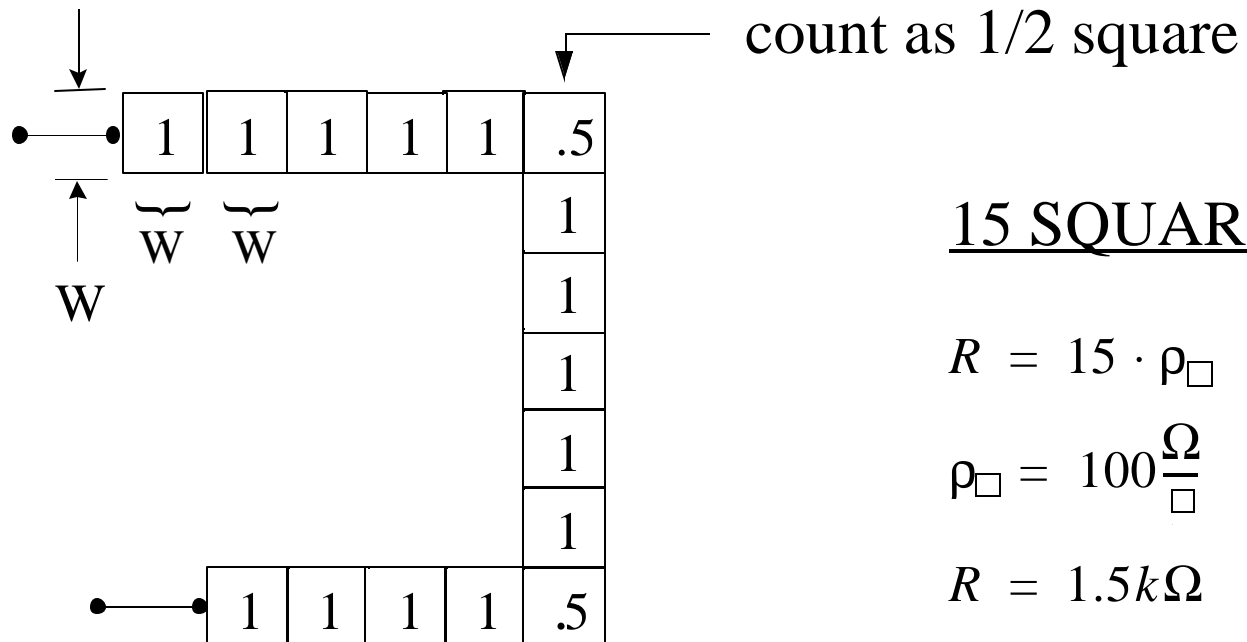

15 SQUARES

$$R = 15 \cdot \rho_{\square}$$

$$\rho_{\square} = 100 \frac{\Omega}{\square}$$

$$R = 1.5k\Omega$$