

University of California  
Berkeley  
College of Engineering  
Department of Electrical Engineering  
and Computer Science


Robert W. Brodersen  
EECS140

Analog Circuit Design

**Lectures  
on  
FEEDBACK**

**Feedback**

FB-1

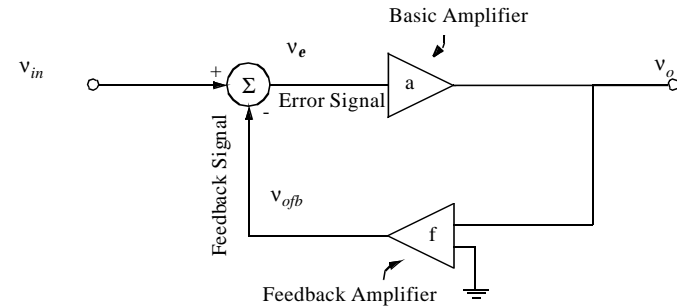

f = gain of feedback amplifier  
a = gain of basic amplifier

**Feedback (Cont.)**

FB-2

$$v_e = v_{in} - v_{ofb}$$

$$v_{ofb} = f \cdot v_o$$

$$v_e = v_{in} - f \cdot v_o$$

$$v_o = a \cdot v_e$$

$$A_v = v_o / v_{in} = \frac{a}{(1 + a \cdot f)} = \frac{1}{f} \cdot \left( \frac{T}{1 + T} \right) \leftarrow \text{Closed loop gain}$$

$$T \equiv \text{Loop Gain} = a \cdot f$$

a = Open Loop Gain

f = Feedback Factor

$$A_v |_{a \rightarrow \infty} = \frac{1}{f} \quad T \gg 1$$

**Feedback (Cont.)**

FB-5


There are 4 basic kinds of Feedback Circuits :

(Type of Feedback)		(Type of Sensing)
1) Series (Voltage)	-	Shunt (Voltage)
2) Shunt (Current)	-	Shunt (Voltage)
3) Shunt (Current)	-	Series (Current)
4) Series (Voltage)	-	Series (Current)

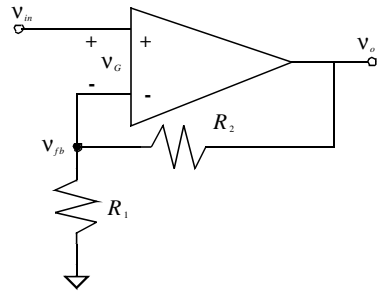**Series-Shunt ( $v_{out}/v_{in}$ )**


FB-6

This is a voltage amplifier, a typical example is the well known configuration shown below :



**Series-Shunt (Cont.)**

FB-7

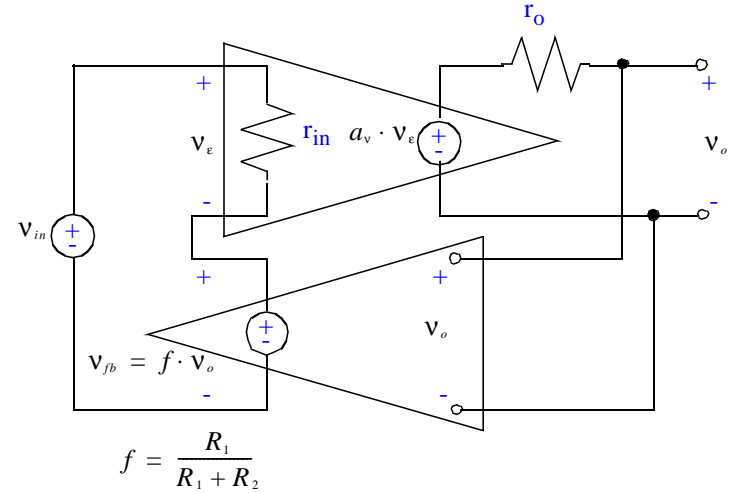

**Series-Shunt (Cont.)**

FB-8

**Gain Calculation :**

$$v_o = a_v \cdot v_\epsilon$$

$$v_{fb} = f_v \cdot v_o$$

$$v_{in} = v_\epsilon + v_{fb} = \frac{v_o}{a_v} + f_v \cdot v_o$$

$$\frac{v_o}{v_{in}} = \frac{1}{f_v} \cdot \left( \frac{T}{1+T} \right) = A_v \quad \text{Closed Loop Gain}$$

$$v_o = \frac{v_{in} \cdot a_v}{1 + a_v \cdot f_v}$$

$$v_{in} = v_\epsilon \cdot (1 + a_v \cdot f_v)$$

**Series-Shunt (Cont.)**

FB-9

**Rout Calculation (Closed Loop Output Resistance) :**

$$R_{out}|_{v_o=0} = \frac{v_t}{i_t}$$

Drive output with  $v_t$ , measure  $i_t$


$$i_t = \frac{v_t - a_v \cdot v_\epsilon}{r_o}$$

$$v_\epsilon + f_v \cdot v_t = v_{in} = 0 ; v_\epsilon = -f_v \cdot v_t$$

$$v_{in} = 0$$

$$i_t = \frac{v_t + a_v \cdot f_v \cdot v_t}{r_o}$$
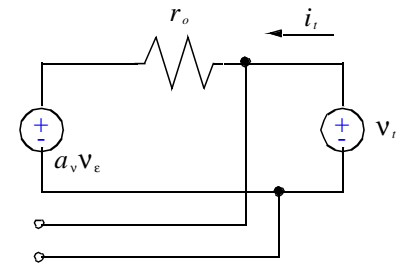
$$\frac{v_t}{i_t} = R_{out} = \frac{r_o}{1 + a_v \cdot f_v} = \frac{r_o}{1 + T}$$



$$A_v = 10 \quad f_v = 0.1 \quad a_v = 50,000$$

$$T = 0.1 \cdot 50,000 = 5000 \quad r_o = 100\Omega$$

$$R_{out} = \frac{r_o}{1 + T} = 0.02\Omega$$

**Series-Shunt (Cont.)**

FB-10

**R<sub>in</sub> Calculation :**

$$R_{in} = \frac{V_{in}}{i_{in}}$$


$$V_{in} = (1 + T) \cdot v_{\epsilon}$$

$$i_{in} = \frac{v_{\epsilon}}{r_{in}} = \frac{V_{in}}{(1 + T) \cdot r_{in}}$$

$$R_{in} = \frac{V_{in}}{i_{in}} = (1 + T) \cdot r_{in}$$

**Shunt-Shunt (Transresistance  $v_{out}/i_{in}$ )**

FB-11

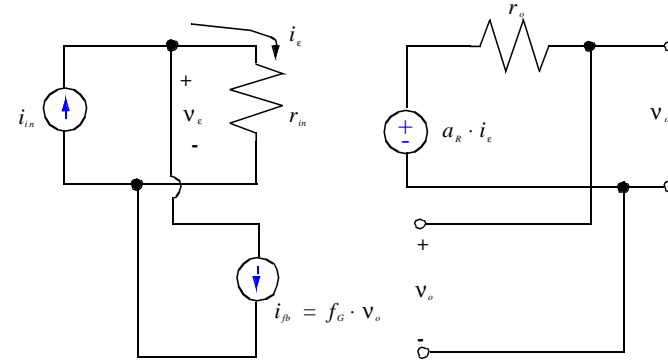

**Shunt-Shunt (Cont.)**

FB-13

**Gain Calculation :**

$$i_{fb} = f_G \cdot v_o$$

$$f_G = \frac{i_{fb}}{v_o}$$

$$i_{\epsilon} = i_{in} - i_{fb}$$

$$v_o = a_R \cdot i_{\epsilon}$$


$a_R$  has units of resistance

$$v_o = a_R \cdot (i_{in} - \underbrace{f_G \cdot v_o}_{i_{fb}})$$

$$\frac{v_o}{i_{in}} = \frac{1}{f_G} \cdot \left( \frac{T}{1 + T} \right)$$

**Shunt-Shunt (Cont.)**

FB-14

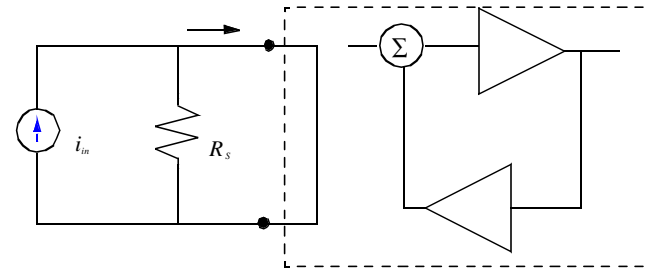

**Shunt-Shunt (Cont.)**

FB-15

**Rin Calculation :**

$$R_{IN} = \frac{V_\epsilon}{i_{in}}$$

$$i_\epsilon = i_{in} - f_G \cdot V_o = i_{in} - a_R \cdot f_G \cdot i_\epsilon$$

$$\therefore i_\epsilon = \frac{i_{in}}{1 + a_R \cdot f}$$

$$R_{IN} = \frac{V_\epsilon}{i_{in}} = \frac{r_{in}}{1 + T}$$

**Shunt-Shunt (Cont.)**

FB-16

**Rout Calculation (Closed Loop Output Resistance) :**

$$R_{OUT} = \left. \frac{V_o}{i_i} \right|_{i_{in}=0}$$

$$(V_o = V_i)$$

$$i_{in} = 0 = i_i + i_{fb}$$


$$i_\epsilon = -i_{fb} = -f_G \cdot V_o$$

$$V_o = i_i \cdot r_o + a_R \cdot i_\epsilon = i_i \cdot r_o - a_R \cdot f_G \cdot V_o$$

$$\frac{V_o}{i_i} = \frac{r_o}{1 + T} = R_{OUT}$$

**Shunt-Series (Current Amp  $i_{out}/i_{in}$ )**

FB-17

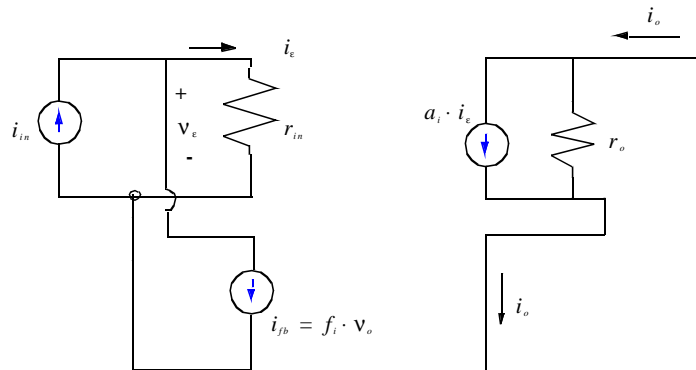

**Shunt-Series (Cont.)**

FB-18

$$T = a_i \cdot f_i$$

$$f_i = \frac{i_{fb}}{i_o}$$

**Gain Calculation :**

$$\frac{i_o}{i_{in}} = \frac{1}{f_i} \cdot \left( \frac{T}{1 + T} \right)$$

**Rin Calculation :**

$$R_{IN} = \frac{r_{in}}{1 + T}$$

**Rout Calculation (Closed Loop Output Resistance) :**

$$R_{OUT} = r_o \cdot (1 + T)$$

### Series-Series (Transconductance $i_{out}/v_{in}$ ) FB-19

### Series-Series (Cont.) FB-20

$$T = a_G \cdot f_R$$

$$f_R = \frac{v_{fb}}{i_o}$$

**Gain Calculation :**

$$A_G = \frac{i_o}{v_{in}} = \frac{1}{f_R} \cdot \left( \frac{T}{1+T} \right)$$

**Rin Calculation :**

$$R_{in} = r_{in} \cdot (1+T)$$

**Rout Calculation (Closed Loop Output Resistance) :**

$$R_{out} = r_o \cdot (1+T)$$

### Series-Shunt Example (Without Loading) FB-21

$a_v = 10^5$   
 $R_1 = 1k\Omega$   
 $R_2 = 9k\Omega$   
 $r_o = 10 \cdot k\Omega$   
 $r_{in} = \infty$

$f_v = \frac{v_{fb}}{v_o}$   
 $\frac{v_{fb}}{v_o} = \frac{R_1}{R_1 + R_2} = f_v = 0.1$

### Series-Shunt Example (Cont.) FB-22

$$A_v = \frac{v_o}{v_{in}} = \frac{1}{f_v} \cdot \frac{T}{1+T} \qquad T = a_v \cdot f_v = a_v \cdot \left( \frac{R_1}{R_1 + R_2} \right)$$

$$T = 10^5 \cdot \left( \frac{1k}{1k + 9k} \right) = 10^4$$


(No loading means we don't taken into account the drop across  $r_o$  due to  $R_1$  &  $R_2$ )

$$A_v = \frac{1}{0.1} \cdot \left( \frac{10^4}{1 + 10^4} \right) = 10.000 \quad \text{precisely 10 to 4 decimal places}$$


$$R_{in} = r_{in} \cdot (1+T) = \infty \cdot (1 + 10^4) \rightarrow \infty$$

$$R_{out} = \frac{r_o}{1+T} = \frac{10^4}{1 + 10^4} = 1\Omega$$

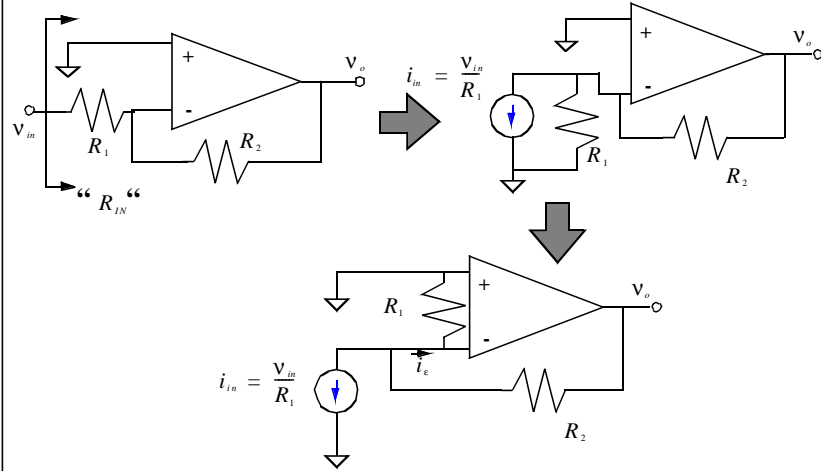
**Shunt-Shunt Example (Without Loading)** FB-24



**Shunt-Shunt Example (Cont.)** FB-25

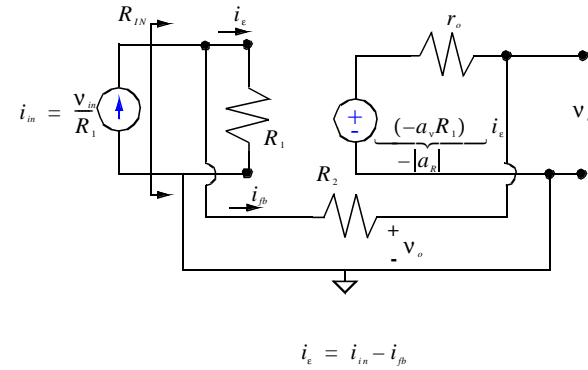

**Shunt-Shunt Example (Cont.)** FB-26

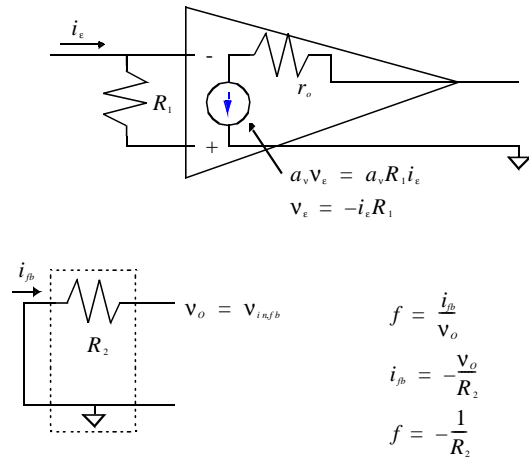

**Shunt-Shunt Example (Cont.)** FB-27

$$T = (-a_v) \cdot \left(-\frac{1}{R_2}\right) = a_v \cdot \left(\frac{R_1}{R_2}\right) = 10^5 \cdot \left(\frac{1}{9}\right) = 1.1 \times 10^4$$

$$A_R = \frac{v_o}{i_{in}} = \frac{1}{f} \cdot \frac{T}{1+T} = -R_2 \cdot \left(\frac{1.1 \times 10^4}{1 + 1.1 \times 10^4}\right) = -R_2 = \underline{\underline{-9k\Omega}}$$

But we want  $\frac{v_o}{v_{in}}$

$$i_{in} = \frac{v_{in}}{R_1}$$


$$\frac{v_o}{v_{in}} = \frac{v_o}{i_{in}} \cdot \frac{1}{R_1} = -\frac{R_2}{R_1} = -9 = \frac{v_o}{v_{in}}$$

**Shunt-Shunt Example (Cont.)**

FB-28

$$R_{OUT} = \frac{r_o}{1+T} = \frac{10k}{1.1 \times 10^4} \approx 0.9\Omega$$

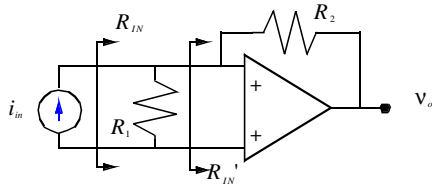
$$R_{IN} = \frac{R_1}{1+T} = \frac{R_1}{1+a_v \cdot \frac{R_1}{R_2}}$$



But  $R_{IN}$  is not what we want.

**Shunt-Shunt Example (Cont.)**

FB-30

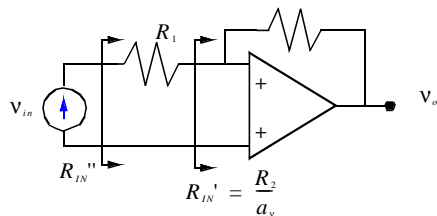


$$R_{IN}'' = R_1 + R_{IN}' = R_1 + \frac{R_2}{a_v}$$

$R_{IN}''$  is the real input resistance we want, but it doesn't come out directly since we used the Norton equivalent circuit at the input

**Shunt-Shunt Example (Cont.)**

FB-29

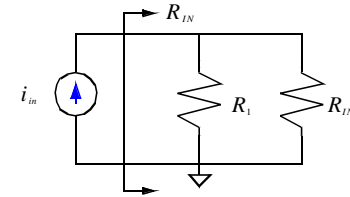

$$R_{IN}' = \frac{R_2}{a_v}$$

$$R_{IN} = \frac{R_1 \cdot R_{IN}'}{R_1 + R_{IN}'} = \frac{R_1 \cdot R_2}{R_2 + a_v \cdot R_1}$$

$$(\cancel{R_1} \cdot R_{IN}') \cdot (R_2 + a_v \cdot R_1) = (\cancel{R_1} \cdot R_2) \cdot (R_1 \cdot \cancel{R_{IN}'})$$


$$R_{IN}' \cdot (\cancel{R_2} - \cancel{R_2} + a_v \cdot R_1) = R_2 \cdot R_1$$

$$R_{IN}' = \frac{R_2}{a_v}$$

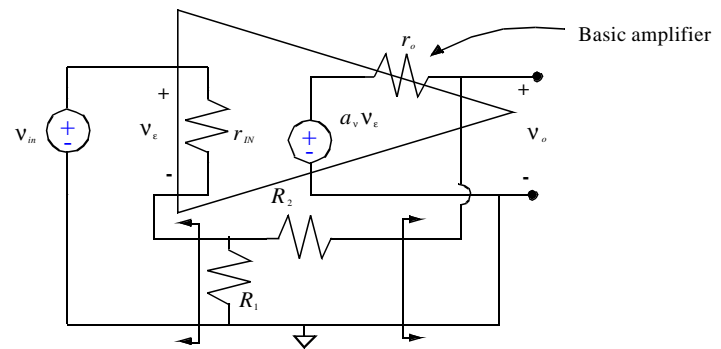**Series-Shunt Example (With Loading)**

FB-31

Series - Shunt with loading effects of feedback circuit on the basic amplifier.




For loading at OUTPUT assume open

For loading at INPUT assume short

**Series-Shunt Example (Cont.)**


FB-32

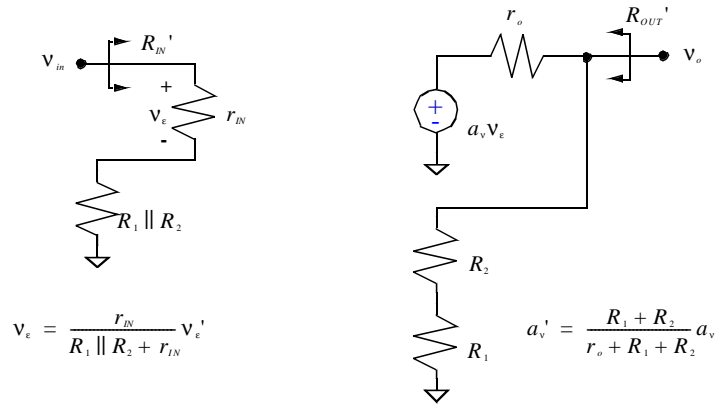

**Series-Shunt Example (Cont.)**


FB-33

**Basic amp with loading :**

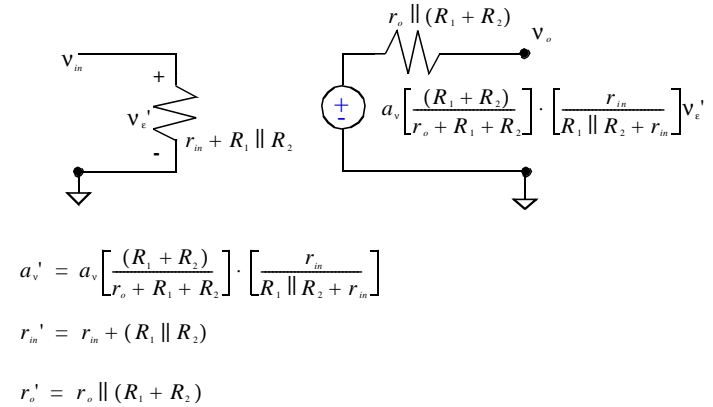

**Series-Shunt Example (Cont.)**

FB-34

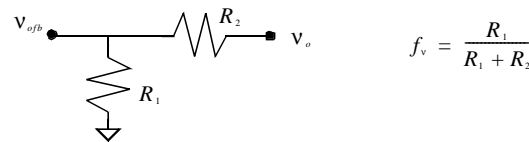

$$T' = a_v' \cdot f = a_v \cdot \left( \frac{R_1}{R_1 + R_2} \right) \cdot \left( \frac{r_{in}}{r_{in} + R_1 \parallel R_2} \right) \cdot \left( \frac{R_1 + R_2}{r_o + R_1 + R_2} \right)$$

$T' < T$  Because of Loading

$$T' = 10^4 \quad T' = (10^4) \cdot (0.1) \cdot \left( \frac{\infty}{\infty + 1k \parallel 9k} \right) \cdot \left( \frac{10k}{10k + 10k} \right)$$

$\uparrow$  without loading       $= \frac{1}{2} \times 10^4$  ← with loading

**Series-Shunt Example (Cont.)**

FB-35

$$R_{IN} = (r_{in} + R_1 \parallel R_2) \cdot (1 + T')$$

$$T' \gg 1$$

$$R_{IN} = (r_{in} + R_1 \parallel R_2) \cdot \left( \frac{r_{in} \cdot a_v}{r_{in} + R_1 \parallel R_2} \right) \cdot \left( \frac{R_1 + R_2}{r_o + R_1 + R_2} \right) \cdot \left( \frac{R_1}{R_1 + R_2} \right)$$


$$R_{IN} = r_{in} \cdot T \cdot \left( \frac{R_1 + R_2}{r_o + R_1 + R_2} \right)$$

$$R_{OUT} = \frac{r_o'}{1 + T'} = \frac{r_o \cdot (R_1 + R_2)}{r_o + R_1 + R_2} \cdot \frac{1}{a_v \cdot \left( \frac{r_{in}}{r_{in} + R_1 \parallel R_2} \right) \cdot \left( \frac{R_1}{r_o + R_1 + R_2} \right)}$$

$$R_{OUT} = \frac{r_o}{T \cdot \left( \frac{r_{in}}{r_{in} + R_1 \parallel R_2} \right)}$$

**Shunt-Shunt Example (With Loading)**


FB-36

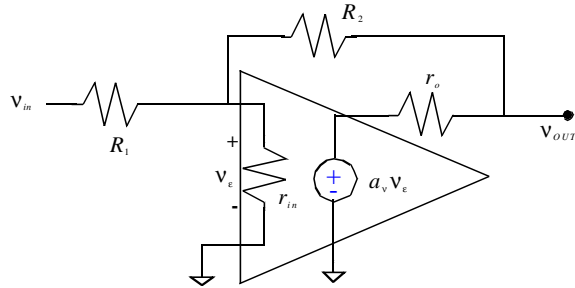

**Shunt-Shunt Example (Cont.)**

FB-37


Transforming to current source input :

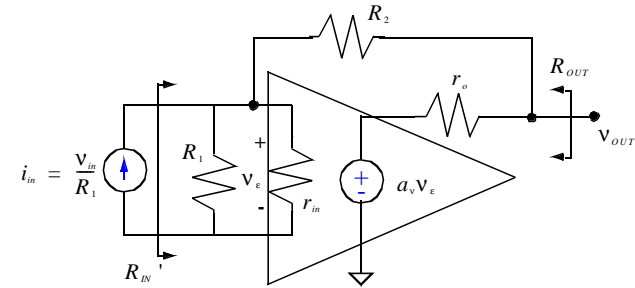

**Shunt-Shunt Example (Cont.)**

FB-38


Redrawing :

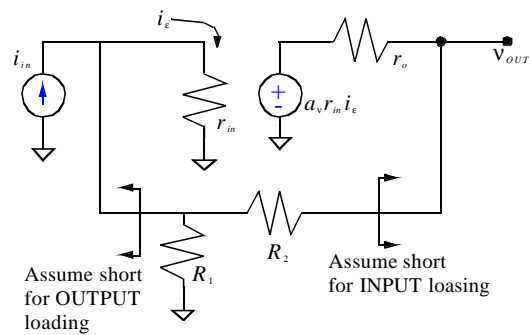

**Shunt-Shunt Example (Cont.)**

FB-39

**Basic amplifier with loading :**

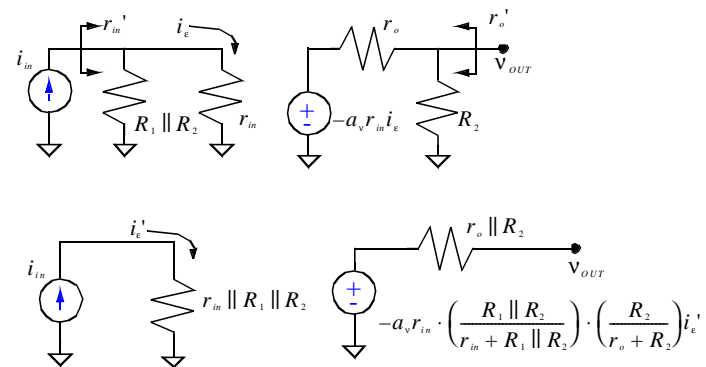


**Shunt-Shunt Example (Cont.)**

FB-40

$$a_k' = -a_v \cdot r_{in} \cdot \left( \frac{R_1 \parallel R_2}{r_{in} + R_1 \parallel R_2} \right) \cdot \left( \frac{R_2}{r_o + R_2} \right) = -a_v \cdot (r_{in} \parallel R_1 \parallel R_2) \cdot \left( \frac{R_2}{r_o + R_2} \right)$$

$$r_{in}' = r_{in} \parallel R_1 \parallel R_2$$

$$r_{out}' = R_2 \parallel r_o$$

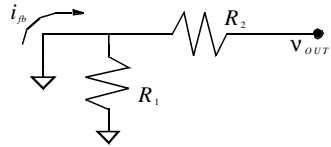

$$f_G = \frac{i_{\beta}}{v_{OUT}} = -\frac{1}{R_2}$$

**Shunt-Shunt Example (Cont.)**

FB-42

$$T' \gg 1$$

$$R_{IN}' = \frac{r_{in}'}{1 + T'} = \frac{r_{in} \parallel R_1 \parallel R_2}{a_v \cdot \frac{r_{in}}{R_2} \cdot \left( \frac{R_1 \parallel R_2}{r_{in} + R_1 \parallel R_2} \right) \cdot \left( \frac{R_2}{r_o + R_2} \right)}$$

$$R_{IN}' = \frac{r_o + R_2}{a_v} \quad \text{independent of } R_1$$

$$R_{IN}'' = R_1 + R_{IN}' \quad \text{at } v_{in}$$

$$R_{OUT} = \frac{r_{out}'}{1 + T'} = \frac{R_2 \parallel r_o}{1 + T'} = \frac{r_o}{a_v \cdot f_G \cdot (r_{in} \parallel R_1 \parallel R_2)} = R_{OUT}'$$

**Shunt-Shunt Example (Cont.)**

FB-41

Finally we get :


$$\frac{v_{OUT}}{i_{in}} = \frac{1}{f_G} \cdot \left( \frac{T'}{1 + T'} \right)$$

$$T' = a_k' \cdot f_G = a_v \cdot \frac{r_{in}}{R_2} \cdot \left( \frac{R_1 \parallel R_2}{r_{in} + R_1 \parallel R_2} \right) \cdot \left( \frac{R_2}{r_o + R_2} \right)$$

$$\frac{v_{OUT}}{v_{in}} = \frac{1}{R_1} \cdot \left( \frac{v_{OUT}}{i_{in}} \right)$$

$$\frac{v_{OUT}}{v_{in}} = \left( \frac{R_2}{R_1} \right) \cdot \left( \frac{T'}{1 + T'} \right)$$

FB-43

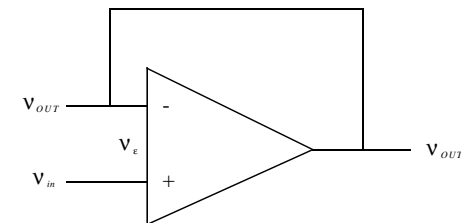

$$v_{\epsilon} = v_{in} - v_{OUT}$$


$$= v_{in} - v_{\beta} = v_{in} - f \cdot v_{OUT}$$

$$f = 1$$

Series - Shunt

FB-44

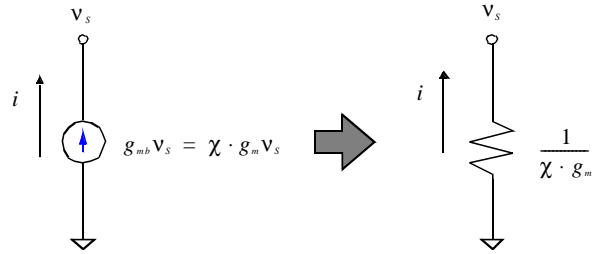**Replacing current sources with resistances :**




$$i = g_{mb} v_s$$

$$\frac{v_s}{i} = \frac{1}{g_{mb}} = \frac{1}{\chi \cdot g_m}$$

FB-45

**Single Transistor : Series - Shunt**

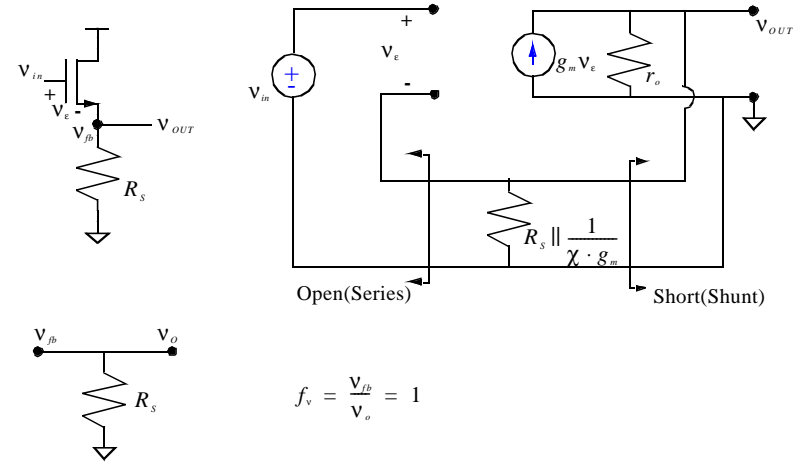


$$f_v = \frac{v_{fb}}{v_o} = 1$$

FB-46

**Single Transistor : Series - Shunt (Cont.)**

**With Loading :**

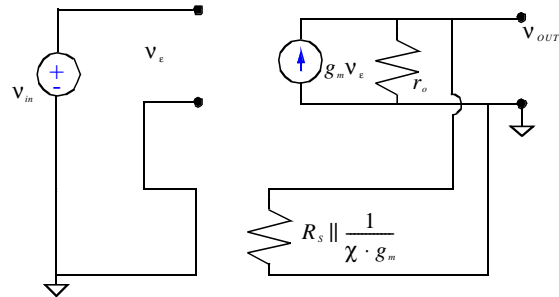

FB-47

**Single Transistor : Series - Shunt (Cont.)**

$$a_v' = g_m \cdot \left( r_o \parallel R_s \parallel \frac{1}{\chi \cdot g_m} \right) = T' \quad \text{since } f_v = 1$$

$$r_o \gg R_s$$

$$A_v = \frac{1}{f_v} \cdot \frac{T'}{1 + T'} \approx \frac{g_m \cdot \left( R_s \parallel \frac{1}{\chi \cdot g_m} \right)}{1 + g_m \cdot \left( R_s \parallel \frac{1}{\chi \cdot g_m} \right)} = \frac{g_m \cdot R_s}{1 + g_m \cdot R_s \cdot (1 + \chi)} = A_v'$$

$$r_{out}' = r_o \parallel R_s \parallel \frac{1}{\chi \cdot g_m} \approx R_s \parallel \frac{1}{\chi \cdot g_m}$$


$$r_{in}' = \infty$$

$$R_{out} = \frac{r_{out}'}{1 + T'} = \frac{R_s \parallel \frac{1}{\chi \cdot g_m}}{1 + g_m \cdot \left( R_s \parallel \frac{1}{\chi \cdot g_m} \right)} = \frac{R_s}{1 + g_m \cdot (1 + \chi) \cdot R_s}$$

$$= R_s \parallel \frac{1}{g_m \cdot (1 + \chi)} = R_{out}$$


**Series - Series with Degeneration**

FB-48

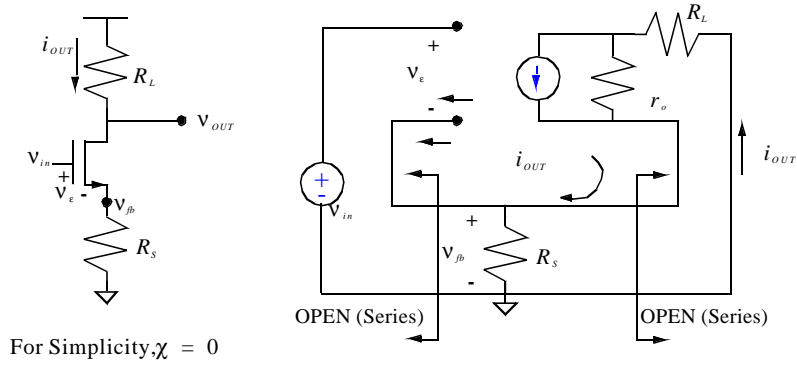

**Series - Series Degeneration (Cont.)**


FB-49

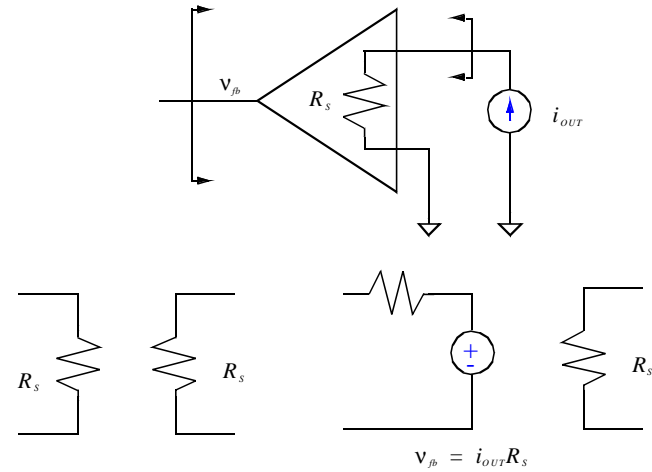

**Series - Series Degeneration (Cont.)**

FB-50


**Basic amplifier with loading :**

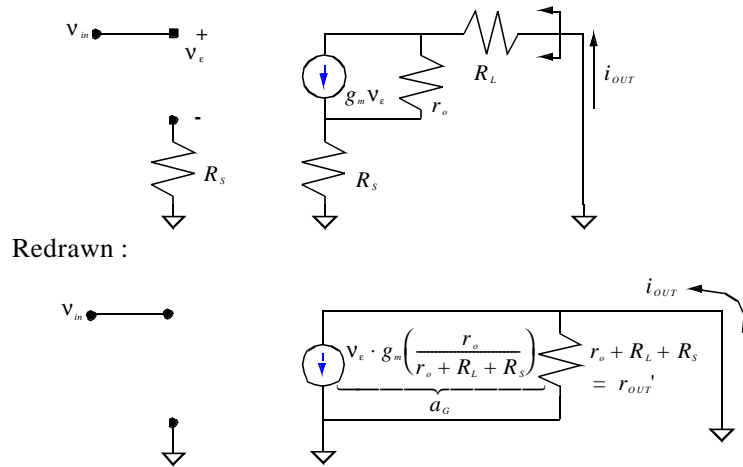

**Series - Series Degeneration (Cont.)**

FB-51

**Feedback Network :**

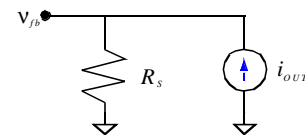

$$f_k = \frac{v_{fb}}{i_{OUT}} = R_S$$

$$T' = a_G \cdot f_G = g_m \cdot \left( \frac{r_o}{r_o + R_L + R_S} \right) \cdot R_S$$

$$R_{OUT}' = r_{OUT}' \cdot (1 + T') = (r_o + R_L + R_S) \cdot \left( 1 + g_m \cdot \frac{r_o \cdot R_S}{r_o + R_L + R_S} \right)$$

$$= r_o + R_L + R_S + g_m \cdot r_o \cdot R_S = R_L + R_S + (1 + g_m \cdot R_S) \cdot r_o$$

**Series - Series Degeneration (Cont.)**

FB-52

$$G_M = \frac{i_{OUT}}{V_{in}} = \frac{1}{f_r} \cdot \frac{T'}{1 + T'}$$


$$= \left( \frac{1}{R_s} \cdot \frac{g_m \cdot \frac{r_o \cdot R_s}{r_o + R_L + R_s}}{1 + \frac{g_m \cdot r_o \cdot R_s}{r_o + R_L + R_s}} = \frac{g_m \cdot r_o}{r_o + R_L + R_s + g_m \cdot r_o \cdot R_s} \right)$$

$$G_M = \frac{g_m \cdot r_o}{R_L + R_s + r_o \cdot (1 + g_m \cdot R_s)} \approx \frac{g_m}{(1 + g_m \cdot R_s)}$$

$$r_o \gg R_L, R_s$$

**Shunt - Shunt**


FB-53

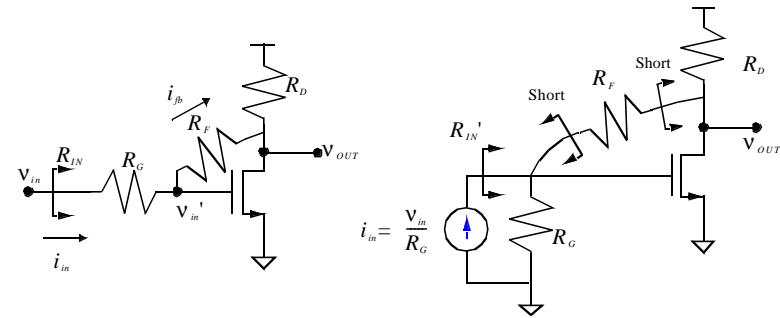

**Shunt - Shunt (Cont.)**

FB-54

**Basic amp with loading :**

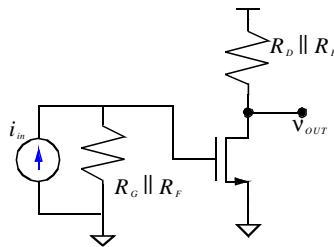


$$v_{OUT} = -i_{in} \cdot (R_G \parallel R_F) \cdot g_m \cdot (R_D \parallel R_F \parallel r_o)$$

$$a_R' = \frac{v_{OUT}}{i_{in}} = -(R_G \parallel R_F) \cdot g_m \cdot (R_D \parallel R_F \parallel r_o)$$

$$r_{in}' = R_G \parallel R_F \quad r_{out}' = R_D \parallel R_F$$

**Shunt - Shunt (Cont.)**

FB-55

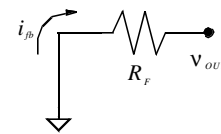

$$f_G = \frac{v_{OUT}}{i_{fb}} = -\frac{1}{R_F}$$

$$T' = a_R \cdot f_G = \frac{1}{R_F} \cdot (R_G \parallel R_F) \cdot g_m \cdot (R_D \parallel R_F \parallel r_o)$$

$$T' \gg 1$$

$$R_{IN}' = \frac{r_{in}'}{1 + T'} = \frac{R_G \parallel R_F}{\frac{1}{R_F} \cdot (R_G \parallel R_F) \cdot g_m \cdot (R_D \parallel R_F \parallel r_o)}$$

$$= \frac{R_F}{g_m \cdot (R_D \parallel R_F \parallel r_o)} \approx \frac{R_F}{a_v}$$

**Shunt - Shunt (Cont.)**

FB-56

$$\text{At } v_{in} \quad a_v = \frac{v_{out}}{v_{in}'}$$

$$R_{IN} = R_G + R_{IN}' = R_G + \frac{R_f}{a_v} \approx R_G$$

$$T' \gg 1$$

$$R_{OUT} = \frac{r_{out}'}{1 + T'} = \frac{(R_D \parallel R_f \parallel r_o)}{\frac{1}{R_f} \cdot (R_G \parallel R_f) \cdot g_m \cdot (R_D \parallel R_f \parallel r_o)}$$

$$= \frac{1}{g_m \cdot \left( \frac{R_G}{R_f + R_G} \right)}$$