

University of California
Berkeley

College of Engineering
Department of Electrical Engineering
and Computer Science


Robert W. Brodersen
EECS140

Analog Circuit Design

Lectures
on
FEEDBACK

Feedback

FB-1

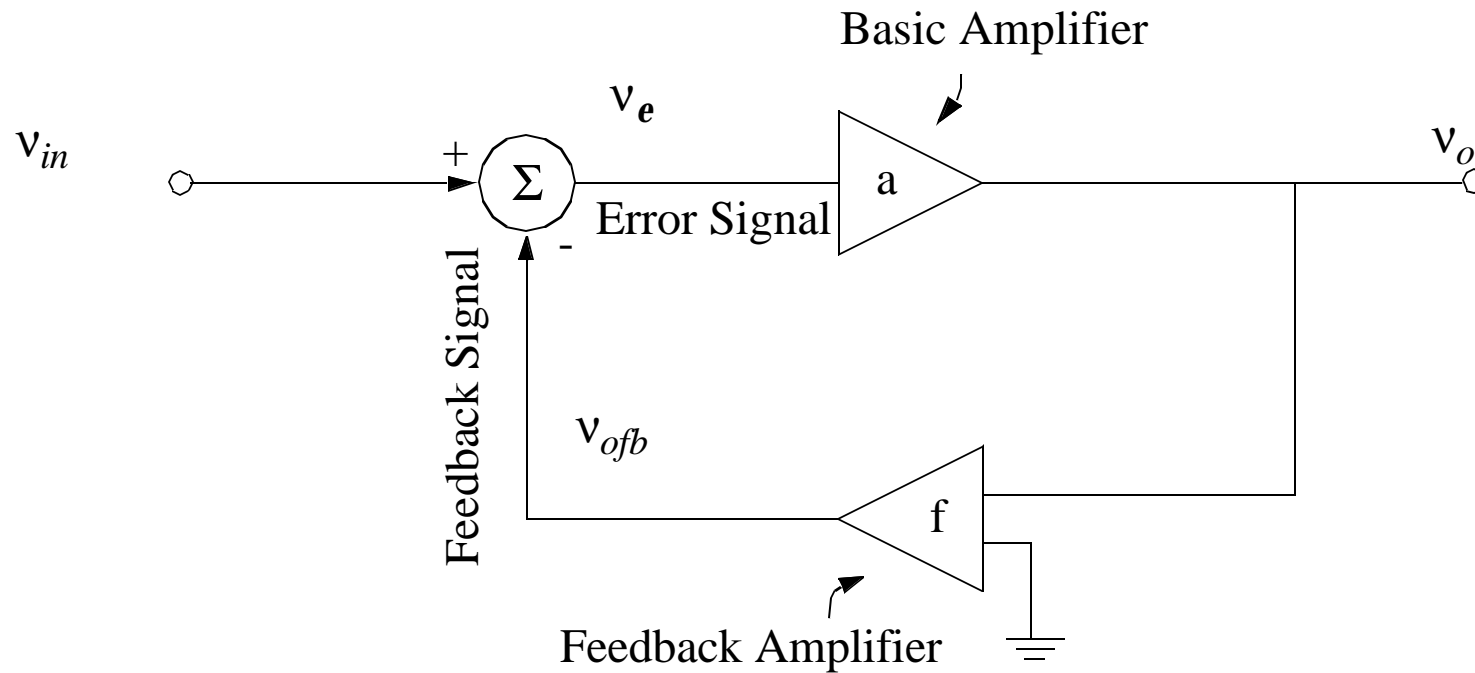

f = gain of feedback amplifier

a = gain of basic amplifier

Feedback (Cont.)

FB-2

$$V_{\varepsilon} = V_{in} - V_{ofb}$$

$$V_{ofb} = f \cdot V_o$$

$$V_{\varepsilon} = V_{in} - f \cdot V_o$$

$$V_o = a \cdot V_{\varepsilon}$$

$$A_v = V_o / V_{in} = \frac{a}{(1 + a \cdot f)} = \frac{1}{f} \cdot \left(\frac{T}{1 + T} \right) \leftarrow \text{Closed loop gain}$$

$$T \equiv \text{Loop Gain} = a \cdot f$$

a = Open Loop Gain

f = Feedback Factor

$$A_v|_{a \rightarrow \infty} = \frac{1}{f} \quad T \gg 1$$

Feedback (Cont.)

FB-5


There are 4 basic kinds of Feedback Circuits :

(Type of Feedback)		(Type of Sensing)
1) Series (Voltage)	-	Shunt (Voltage)
2) Shunt (Current)	-	Shunt (Voltage)
3) Shunt (Current)	-	Series (Current)
4) Series (Voltage)	-	Series (Current)

Series-Shunt (v_{out}/v_{in})


FB-6

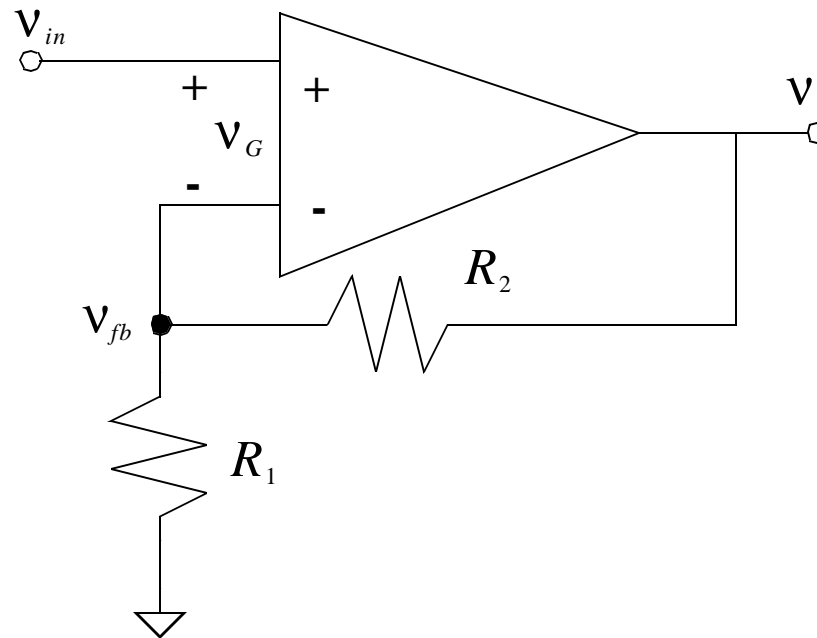This is a voltage amplifier, a typical example is the well known configuration shown below :



Series-Shunt (Cont.)

FB-7

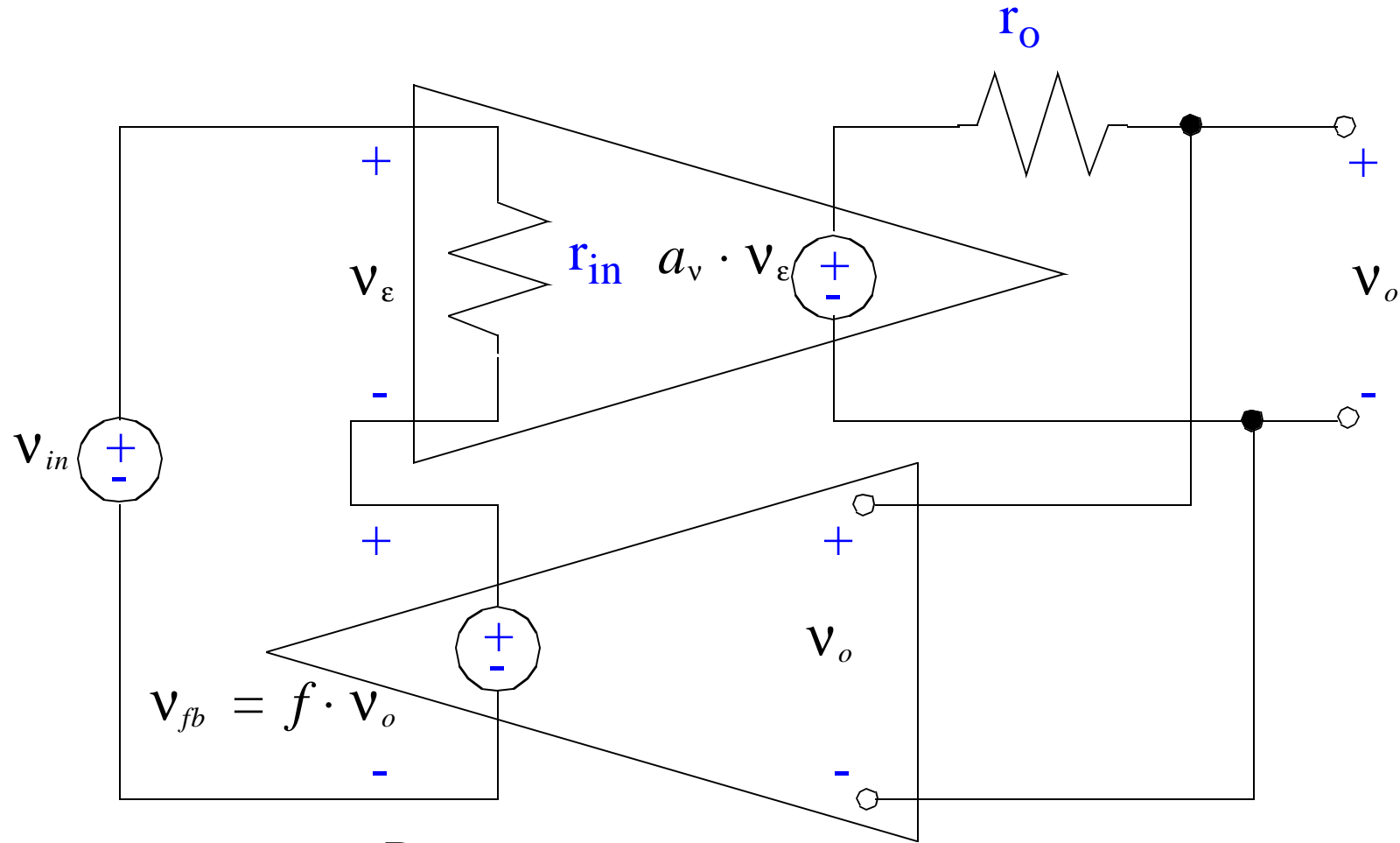

$$f = \frac{R_1}{R_1 + R_2}$$

Series-Shunt (Cont.)

FB-8

Gain Calculation :

$$V_o = a_v \cdot V_\varepsilon$$

$$V_{fb} = f_v \cdot V_o$$

$$V_{in} = V_\varepsilon + V_{fb} = \frac{V_o}{a_v} + f_v \cdot V_o$$

$$\frac{V_o}{V_{in}} = \frac{1}{f_v} \cdot \left(\frac{T}{1+T} \right) = A_v \quad \text{Closed Loop Gain}$$

$$V_o = \frac{V_{in} \cdot a_v}{1 + a_v \cdot f_v}$$

$$V_{in} = V_\varepsilon \cdot (1 + a_v \cdot f_v)$$

Series-Shunt (Cont.)

FB-9

Rout Calculation (Closed Loop Output Resistance) :

$$R_{out} |_{v_{in}=0} = \frac{v_t}{i_t}$$

Drive output with v_t , measure i_t


$$i_t = \frac{v_t - a_v \cdot v_\epsilon}{r_o}$$

$$v_\epsilon + f_v \cdot v_t = v_{in} = 0 ; v_\epsilon = -f_v \cdot v_t$$

$$v_{in} = 0$$

$$i_t = \frac{v_t + a_v \cdot f_v \cdot v_t}{r_o}$$
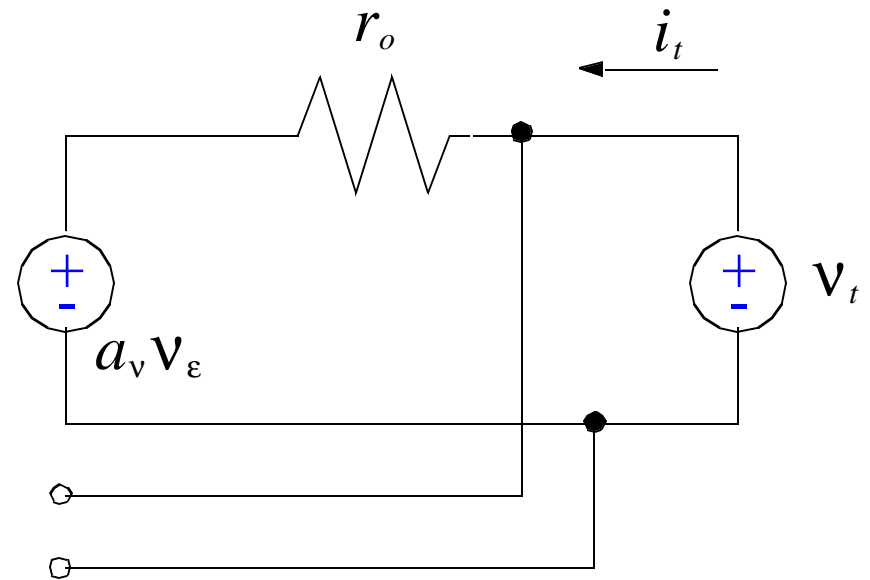
$$\frac{v_t}{i_t} = R_{out} = \frac{r_o}{1 + a_v \cdot f_v} = \frac{r_o}{1 + T}$$



$$A_v = 10 \quad f_v = 0.1 \quad a_v = 50,000$$

$$T = 0.1 \cdot 50,000 = 5000 \quad r_o = 100\Omega$$

$$R_{OUT} = \frac{r_o}{1 + T} = 0.02\Omega$$

Series-Shunt (Cont.)

FB-10

Rin Calculation :


$$R_{in} = \frac{V_{in}}{i_{in}}$$

$$V_{in} = (1 + T) \cdot v_{\epsilon}$$

$$i_{in} = \frac{v_{\epsilon}}{r_{in}} = \frac{V_{in}}{(1 + T) \cdot r_{in}}$$

$$R_{in} = \frac{V_{in}}{i_{in}} = (1 + T) \cdot r_{in}$$

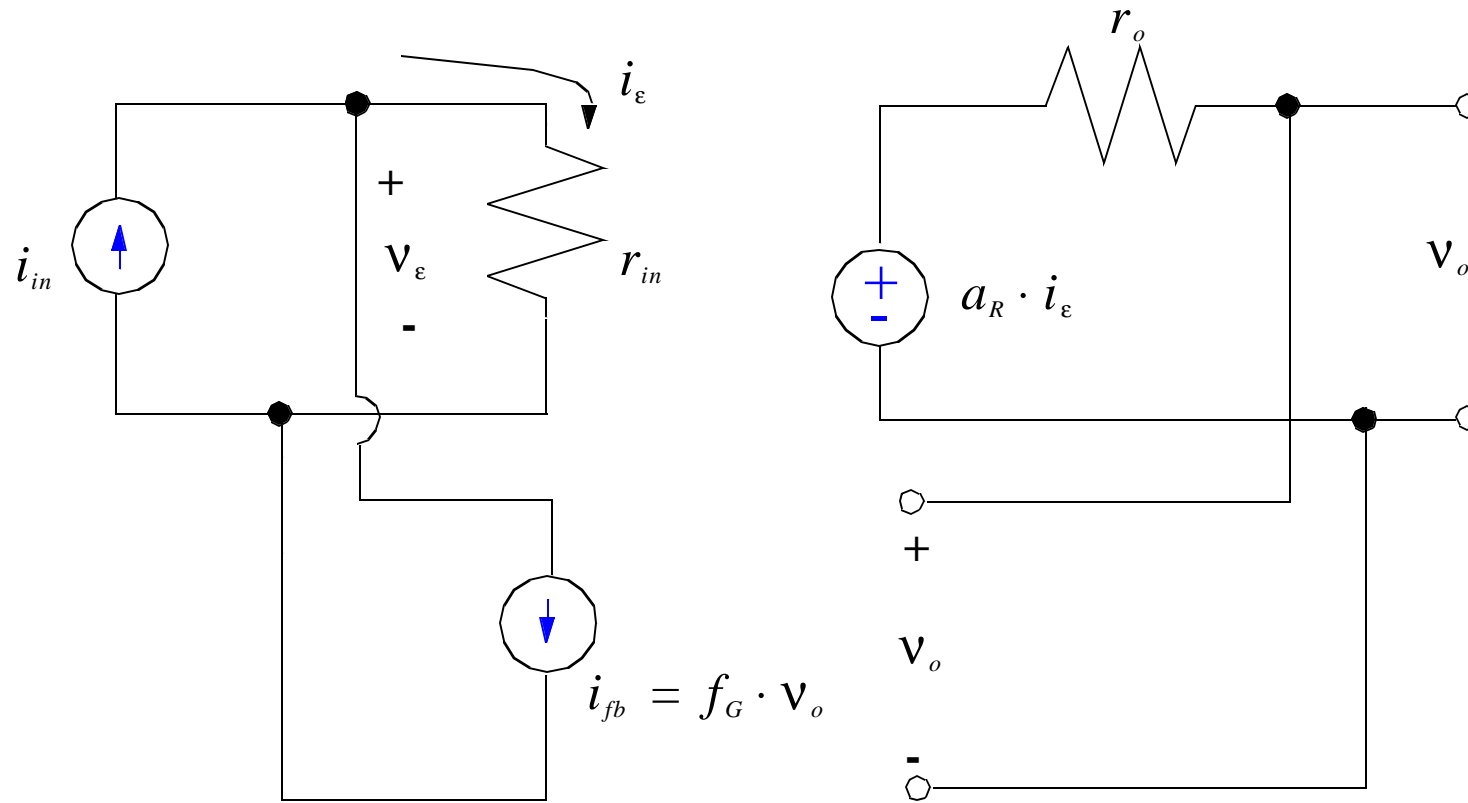Shunt-Shunt (Transresistance v_{out}/i_{in}) FB-11



Shunt-Shunt (Cont.)**Gain Calculation :**

$$i_{fb} = f_G \cdot v_o$$

$$f_G = \frac{i_{fb}}{v_o}$$

$$i_\epsilon = i_{in} - i_{fb}$$

$$v_o = a_R \cdot i_\epsilon$$


a_R has units of resistance

$$v_o = a_R \cdot (i_{in} - \underbrace{f_G \cdot v_o}_{i_{fb}})$$

$$\frac{v_o}{i_{in}} = \frac{1}{f_G} \cdot \left(\frac{T}{1 + T} \right)$$

Shunt-Shunt (Cont.)

FB-14

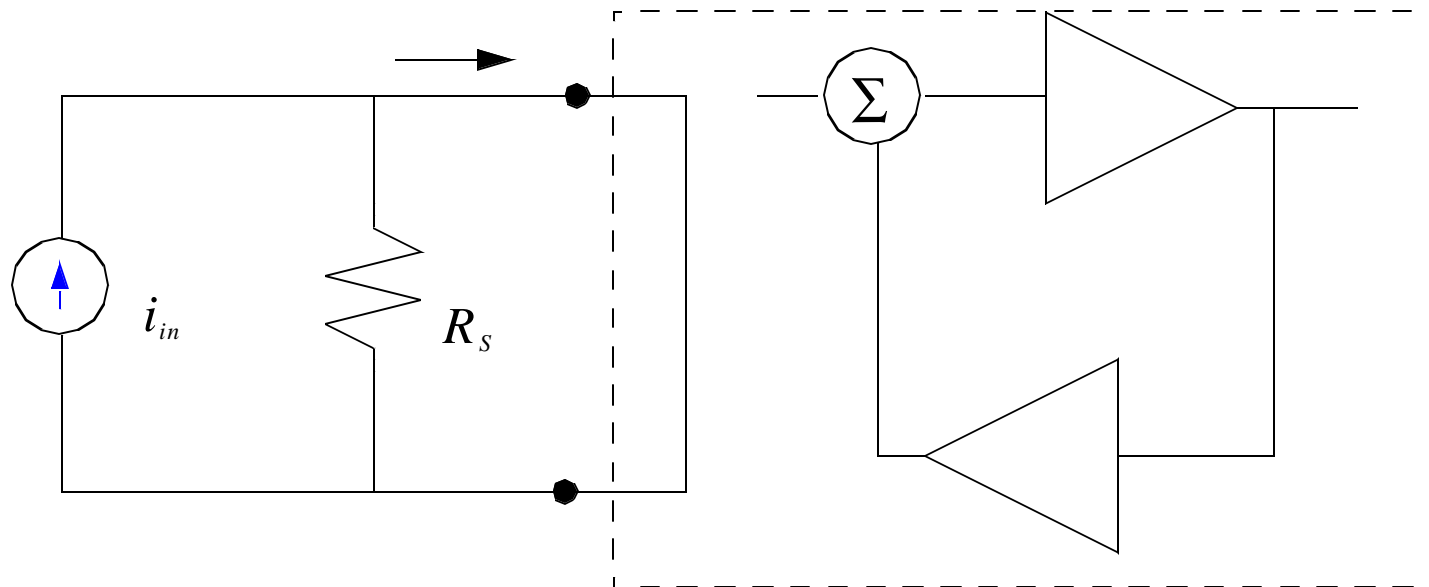

Shunt-Shunt (Cont.)

Rin Calculation :

$$R_{IN} = \frac{V_\varepsilon}{i_{in}}$$

$$i_\varepsilon = i_{in} - f_G \cdot V_o = i_{in} - a_R \cdot f_G \cdot i_\varepsilon$$

$$\therefore i_\varepsilon = \frac{i_{in}}{1 + a_R \cdot f}$$

$$R_{IN} = \frac{V_\varepsilon}{i_{in}} = \frac{r_{in}}{1 + T}$$

Shunt-Shunt (Cont.)

FB-16

Rout Calculation (Closed Loop Output Resistance) :

$$R_{OUT} = \left. \frac{v_t}{i_t} \right|_{i_{in}=0}$$

$$(v_o = v_t)$$

$$i_{in} = 0 = i_t + i_{fb}$$


$$i_{\epsilon} = -i_{fb} = -f_G \cdot v_o$$

$$v_o = i_t \cdot r_o + a_R \cdot i_{\epsilon} = i_t \cdot r_o - a_R \cdot f_G \cdot v_o$$

$$\frac{v_o}{i_t} = \frac{r_o}{1 + T} = R_{OUT}$$

Shunt-Series (Current Amp i_{out}/i_{in})

FB-17

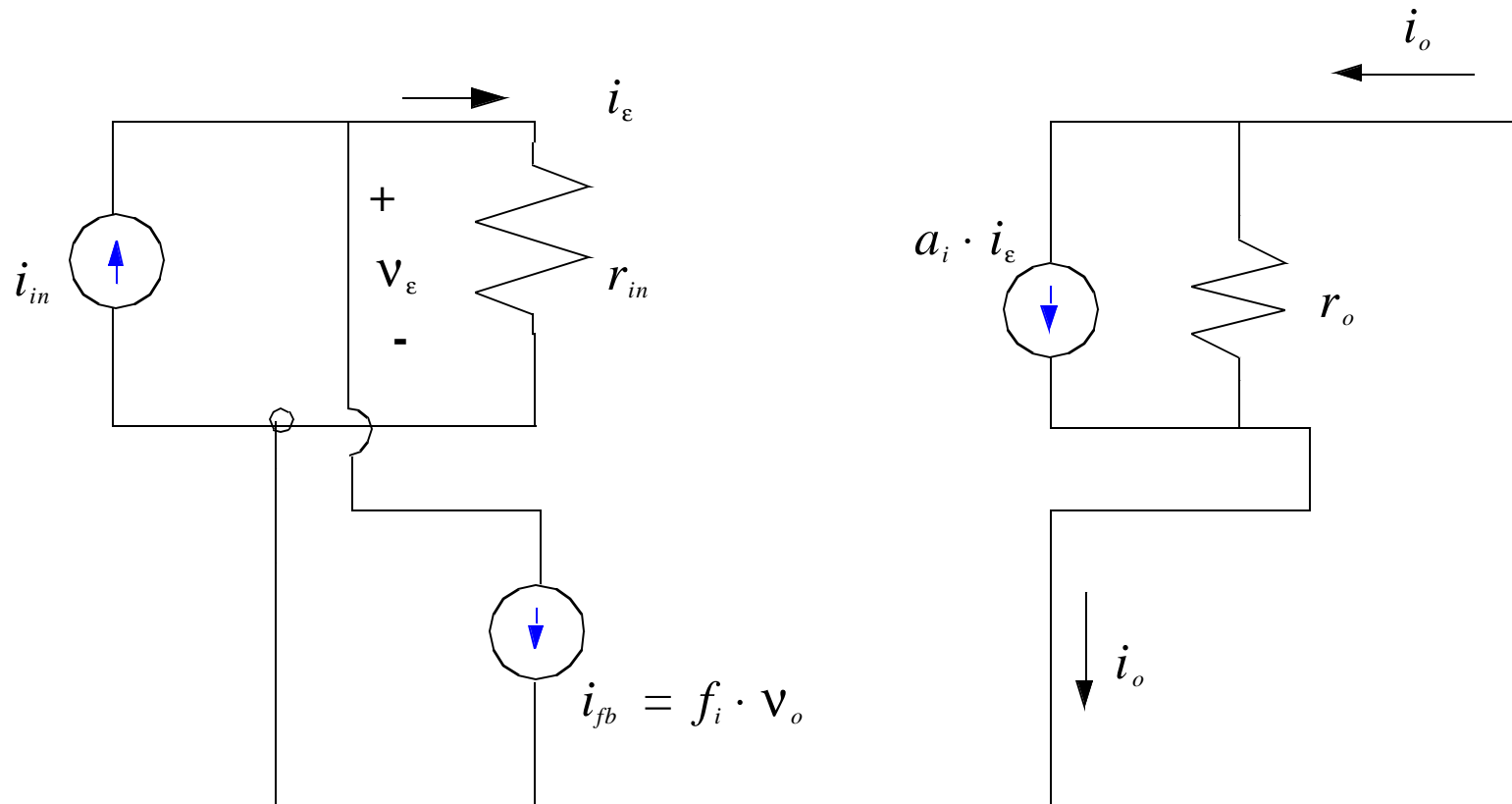

Shunt-Series (Cont.)

FB-18

$$T = a_i \cdot f_i$$

$$f_i = \frac{i_{fb}}{i_o}$$

Gain Calculation :

$$\frac{i_o}{i_{in}} = \frac{1}{f_i} \cdot \left(\frac{T}{1 + T} \right)$$

Rin Calculation :


$$R_{IN} = \frac{r_{in}}{1 + T}$$

Rout Calculation (Closed Loop Output Resistance) :

$$R_{OUT} = r_o \cdot (1 + T)$$

FB-19

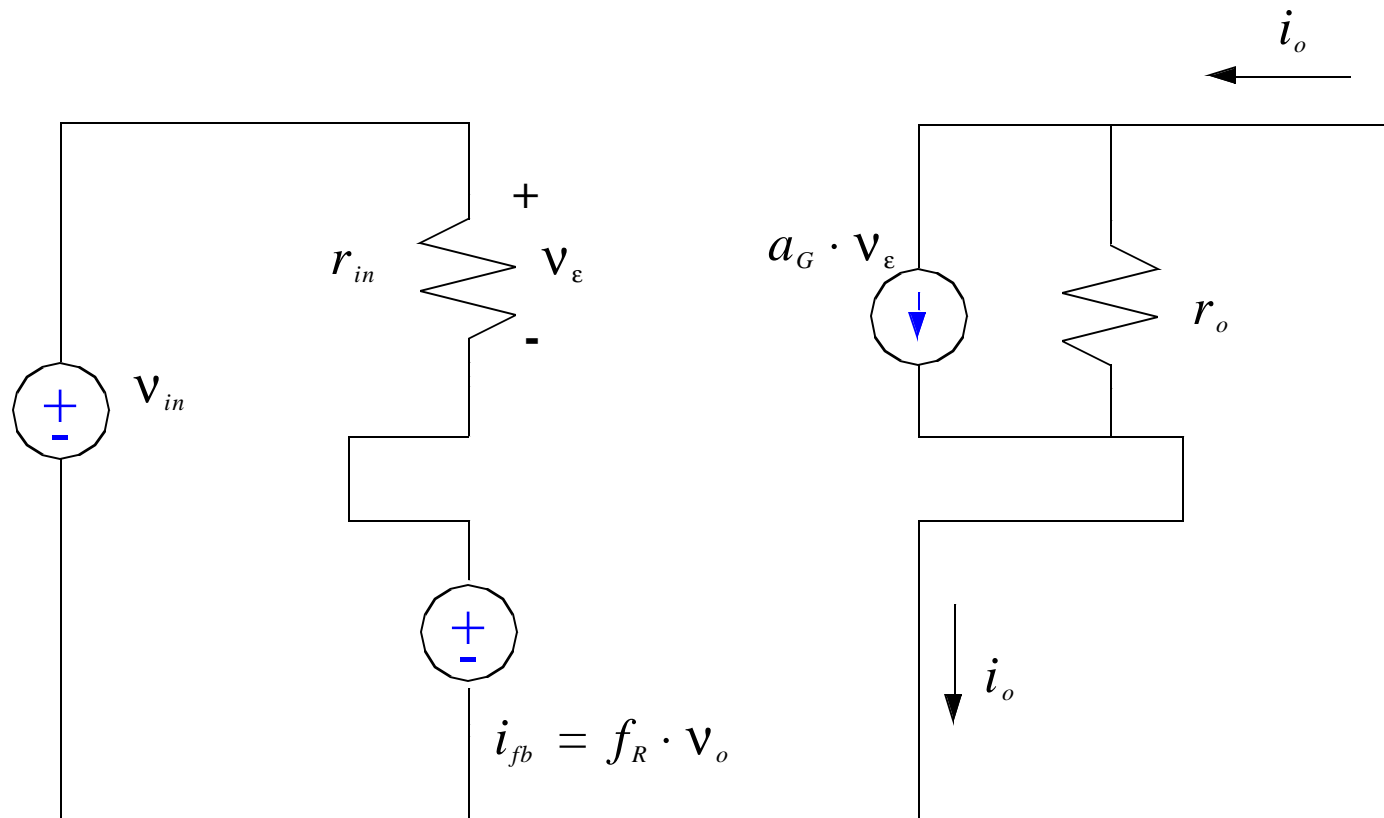Series-Series (Transconductance i_{out}/v_{in})



Series-Series (Cont.)

FB-20

$$T = a_G \cdot f_R$$

$$f_R = \frac{v_{fb}}{i_o}$$

Gain Calculation :

$$A_G = \frac{i_o}{v_{in}} = \frac{1}{f_R} \cdot \left(\frac{T}{1 + T} \right)$$

Rin Calculation :



$$R_{IN} = r_{in} \cdot (1 + T)$$

Rout Calculation (Closed Loop Output Resistance) :


$$R_{OUT} = r_o \cdot (1 + T)$$

Series-Shunt Example (Without Loading)

FB-21

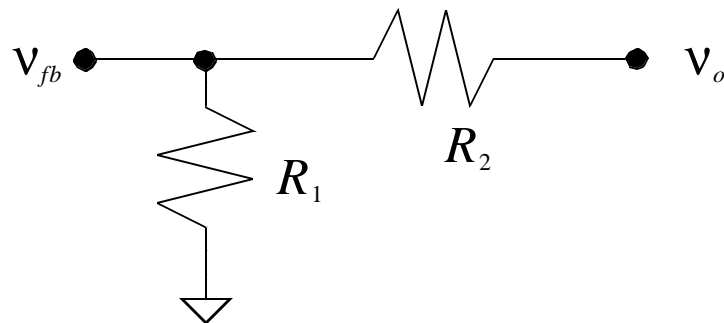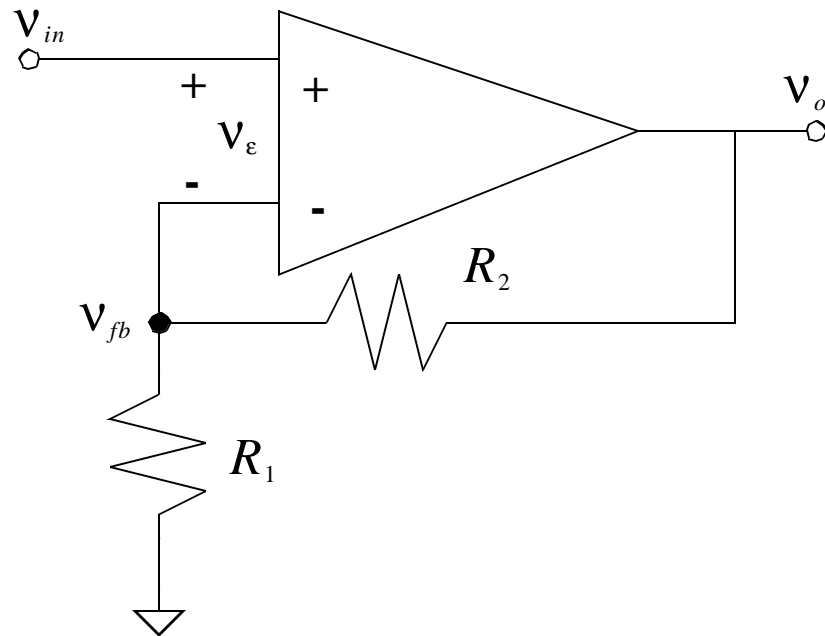

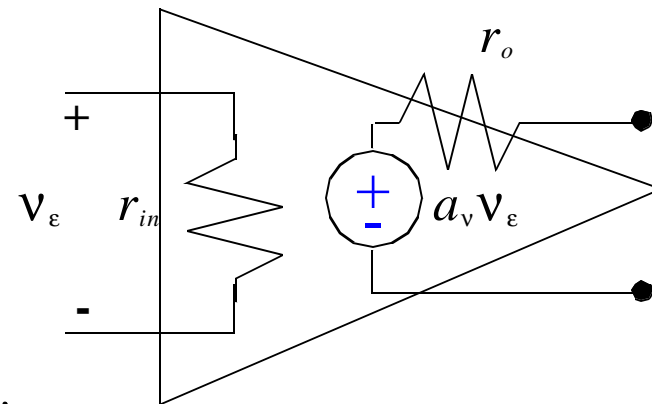- $a_v = 10^5$
- $R_1 = 1k\Omega$
- $R_2 = 9k\Omega$
- $r_o = 10 \cdot k\Omega$
- $r_{in} = \infty$



$$f_v = \frac{v_{fb}}{v_o}$$

$$\frac{v_{fb}}{v_o} = \frac{R_1}{R_1 + R_2} = f_v = 0.1$$

Series-Shunt Example (Cont.)

FB-22

$$A_v = \frac{v_o}{v_{in}} = \frac{1}{f_v} \cdot \frac{T}{1+T} \qquad T = a_v \cdot f_v = a_v \cdot \left(\frac{R_1}{R_1 + R_2} \right)$$

$$T = 10^5 \cdot \left(\frac{1k}{1k + 9k} \right) = 10^4$$

(No loading means we don't taken into account the drop across r_o due to R_1 & R_2)


$$A_v = \frac{1}{0.1} \cdot \left(\frac{10^4}{1 + 10^4} \right) = 10.000 \quad \text{precisely 10 to 4 decimal places}$$

$$R_{in} = r_{in} \cdot (1 + T) = \infty \cdot (1 + 10^4) \rightarrow \infty$$


$$R_{OUT} = \frac{r_o}{1 + T} = \frac{10^4}{1 + 10^4} = 1\Omega$$

Shunt-Shunt Example (Without Loading)

FB-24

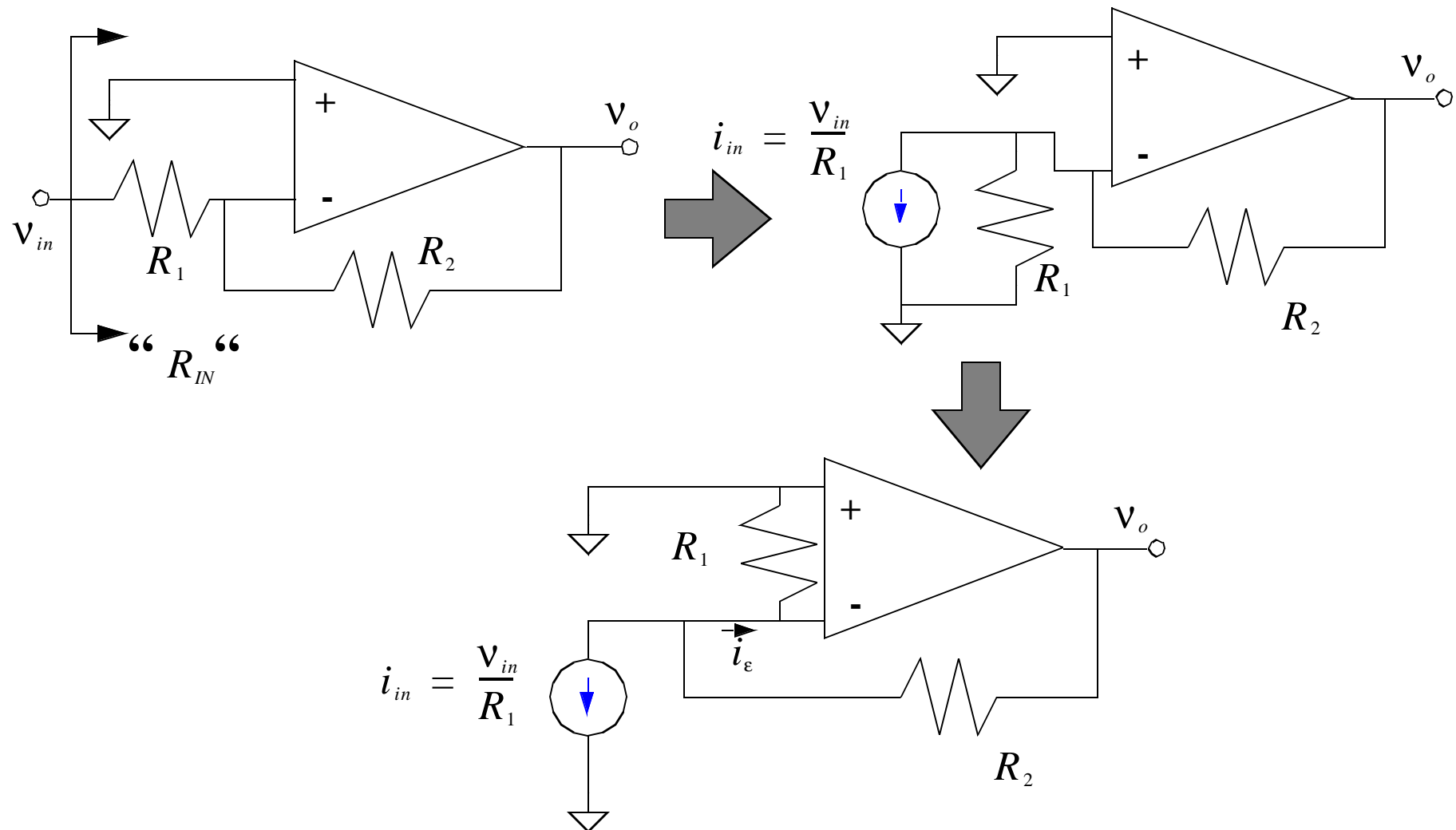



Shunt-Shunt Example (Cont.)

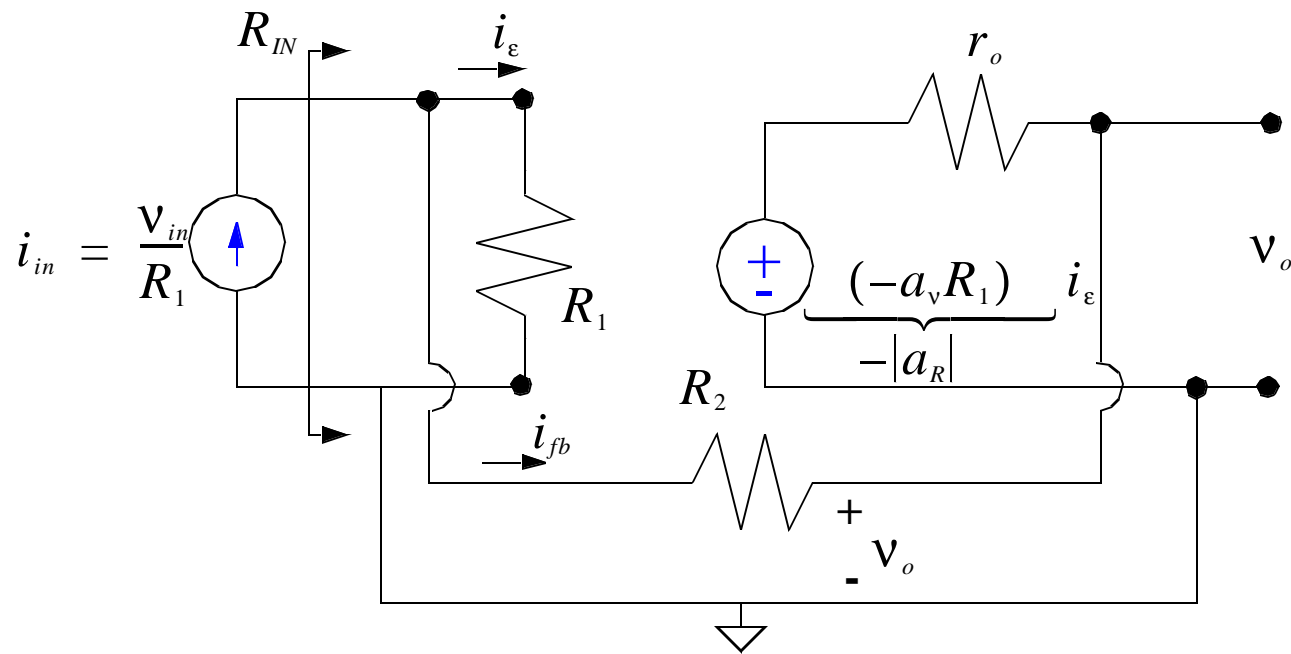

$$i_\epsilon = i_{in} - i_{fb}$$

Shunt-Shunt Example (Cont.)

FB-26

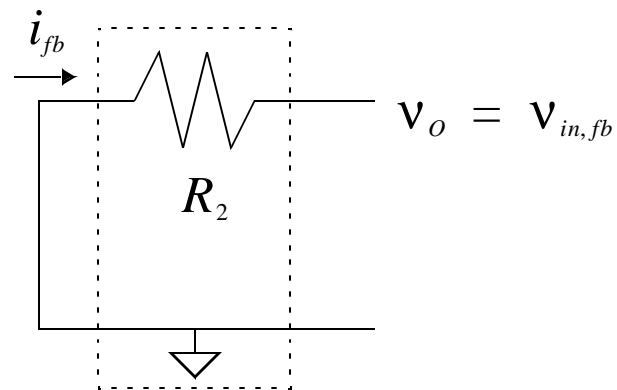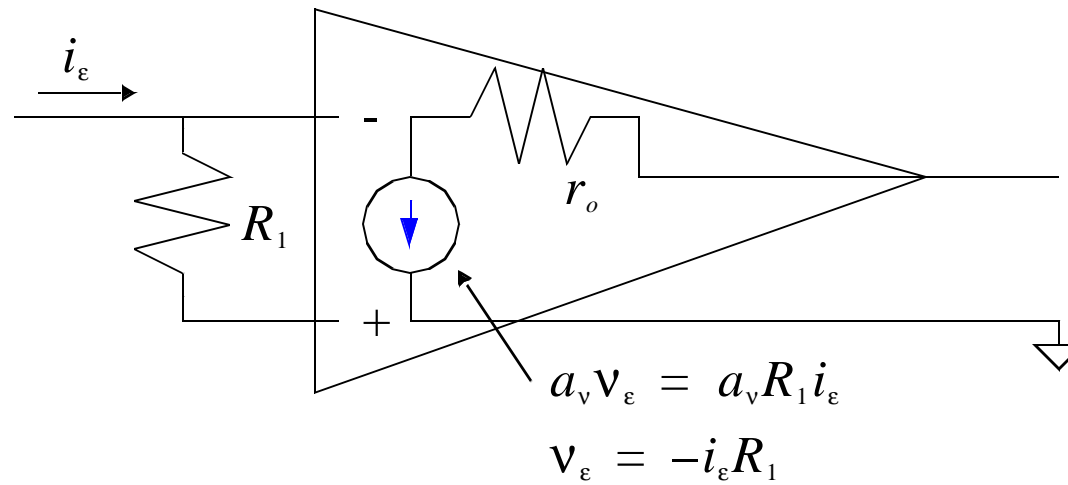

$$f = \frac{i_{fb}}{v_o}$$

$$i_{fb} = -\frac{v_o}{R_2}$$

$$f = -\frac{1}{R_2}$$

Shunt-Shunt Example (Cont.)

FB-27

$$T = (-a_R) \cdot \left(-\frac{1}{R_2}\right) = a_v \cdot \left(\frac{R_1}{R_2}\right) = 10^5 \cdot \left(\frac{1}{9}\right) = 1.1 \times 10^4$$

$$A_R = \frac{v_o}{i_{in}} = \frac{1}{f} \cdot \frac{T}{1+T} = -R_2 \cdot \left(\frac{1.1 \times 10^4}{1 + 1.1 \times 10^4}\right) = -R_2 = \underline{\underline{-9k\Omega}}$$

But we want $\frac{v_o}{v_{in}}$


$$i_{in} = \frac{v_{in}}{R_1}$$

$$\frac{v_o}{v_{in}} = \frac{v_o}{i_{in}} \cdot \frac{1}{R_1} = -\frac{R_2}{R_1} = -9 = \frac{v_o}{v_{in}}$$

Shunt-Shunt Example (Cont.)

$$R_{OUT} = \frac{r_o}{1 + T} = \frac{10k}{1.1 \times 10^4} \approx 0.9\Omega$$

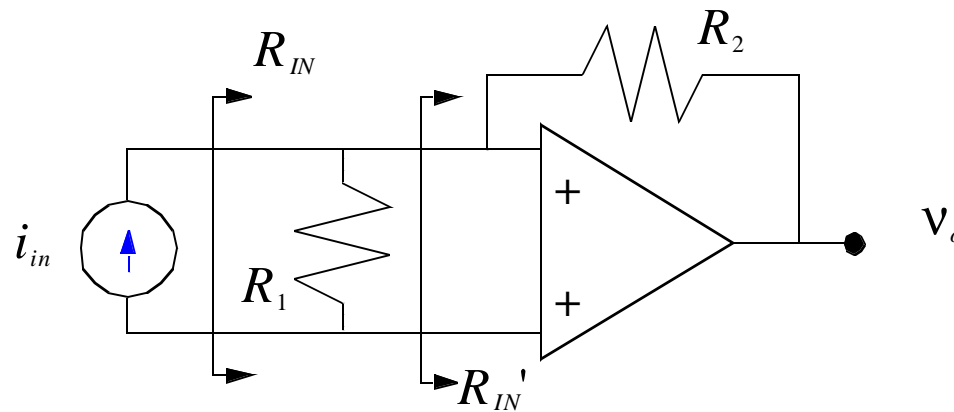
$$R_{IN} = \frac{R_1}{1 + T} = \frac{R_1}{1 + a_v \cdot \frac{R_1}{R_2}}$$



But R_{IN} is not what we want.

Shunt-Shunt Example (Cont.)

FB-29

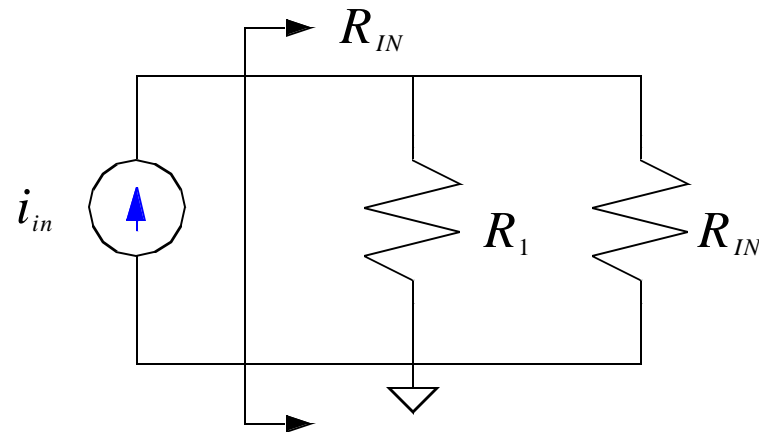

$$R_{IN} = \frac{R_2}{a_v}$$

$$R_{IN} = \frac{R_1 \cdot R_{IN}'}{R_1 + R_{IN}'} = \frac{R_1 \cdot R_2}{R_2 + a_v \cdot R_1}$$


$$(\cancel{R_1} \cdot R_{IN}') \cdot (R_2 + a_v \cdot R_1) = (\cancel{R_1} \cdot R_2) \cdot (R_1 \cdot R_{IN}')$$

$$R_{IN}' \cdot (\cancel{R_2} - \cancel{R_2} + a_v \cdot R_1) = R_2 \cdot R_1$$

$$R_{IN}' = \frac{R_2}{a_v}$$

Shunt-Shunt Example (Cont.)

FB-30

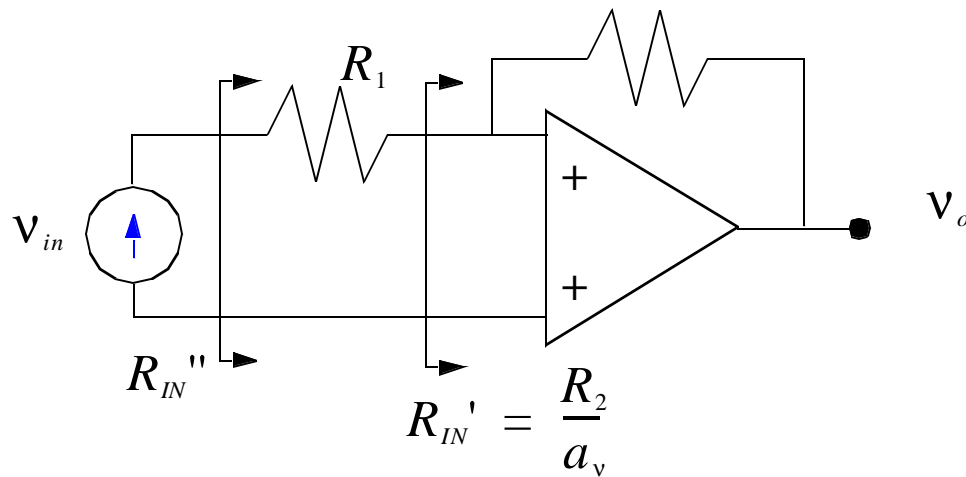

$$R_{IN}' = \frac{R_2}{a_v}$$


$$R_{IN}'' = R_1 + R_{IN}' = R_1 + \frac{R_2}{a_v}$$

R_{IN}'' is the real input resistance we want, but it doesn't come out directly since we used the Norton equivalent circuit at the input

Series-Shunt Example (With Loading)

FB-31

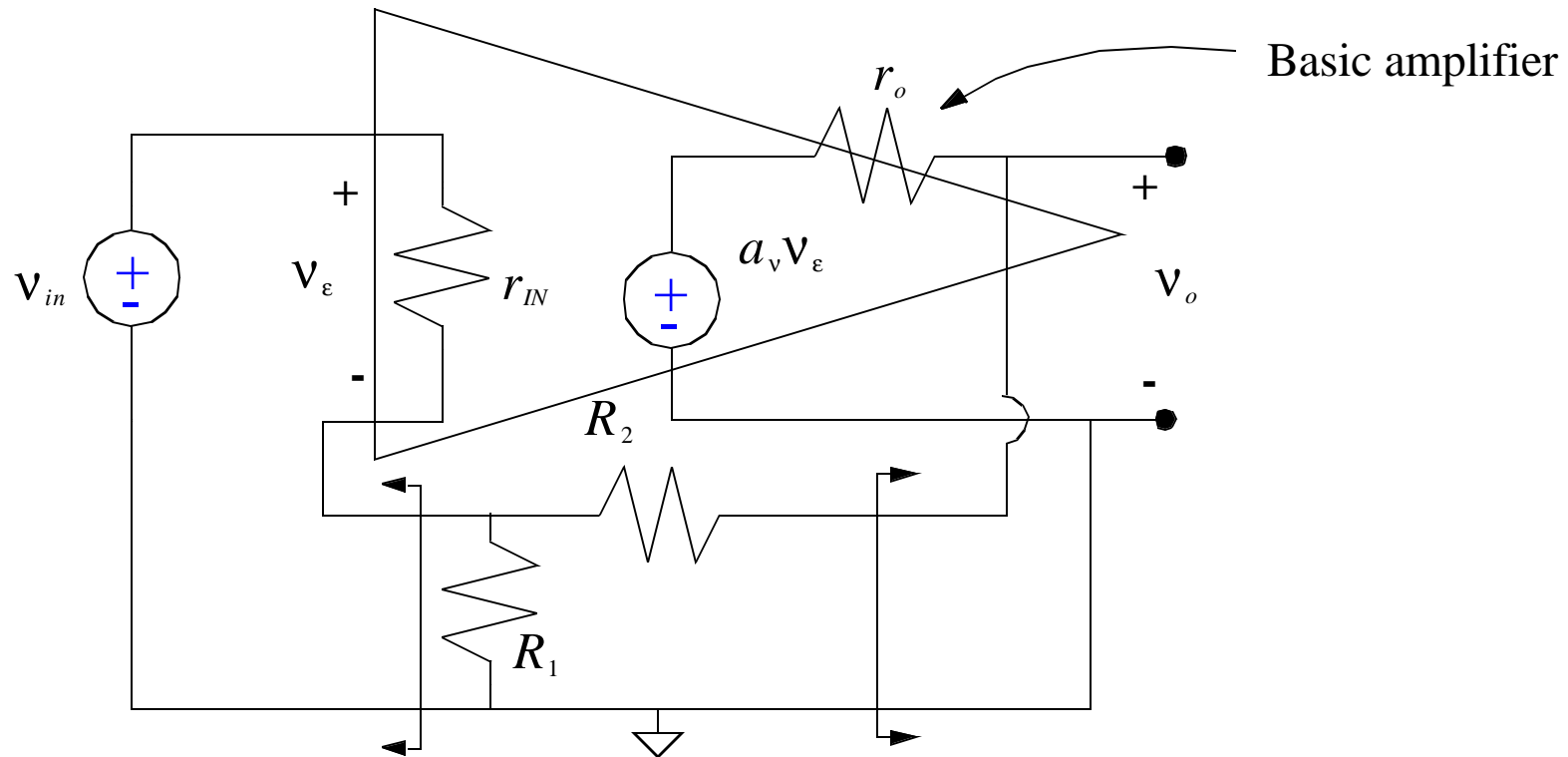Series - Shunt with loading effects of feedback circuit on the basic amplifier.




For loading at OUTPUT
assume open

For loading at INPUT assume short

Series-Shunt Example (Cont.)

FB-32

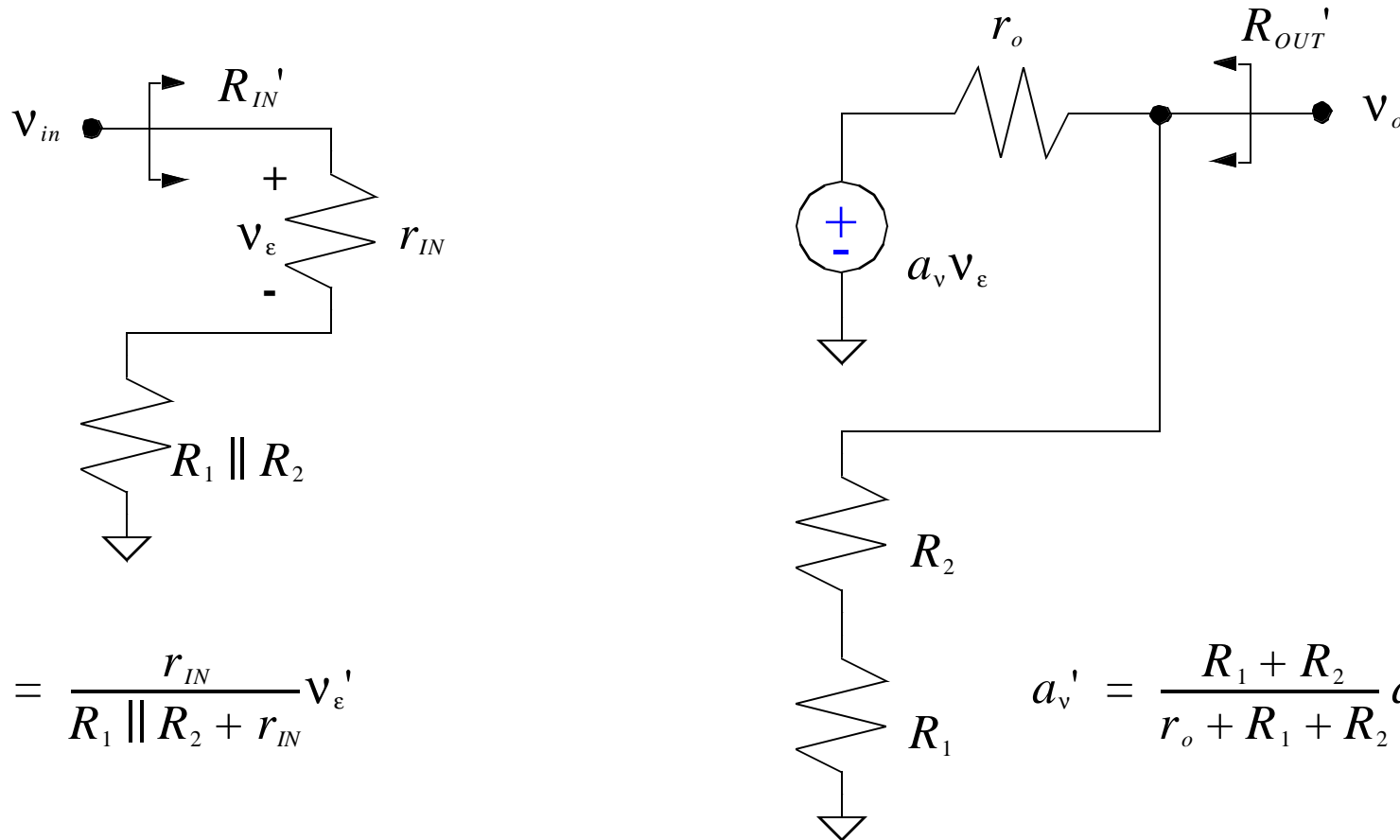


$$v_\epsilon = \frac{r_{IN}}{R_1 \parallel R_2 + r_{IN}} v_\epsilon'$$

$$a_v' = \frac{R_1 + R_2}{r_o + R_1 + R_2} a_v$$

Series-Shunt Example (Cont.)

Basic amp with loading :

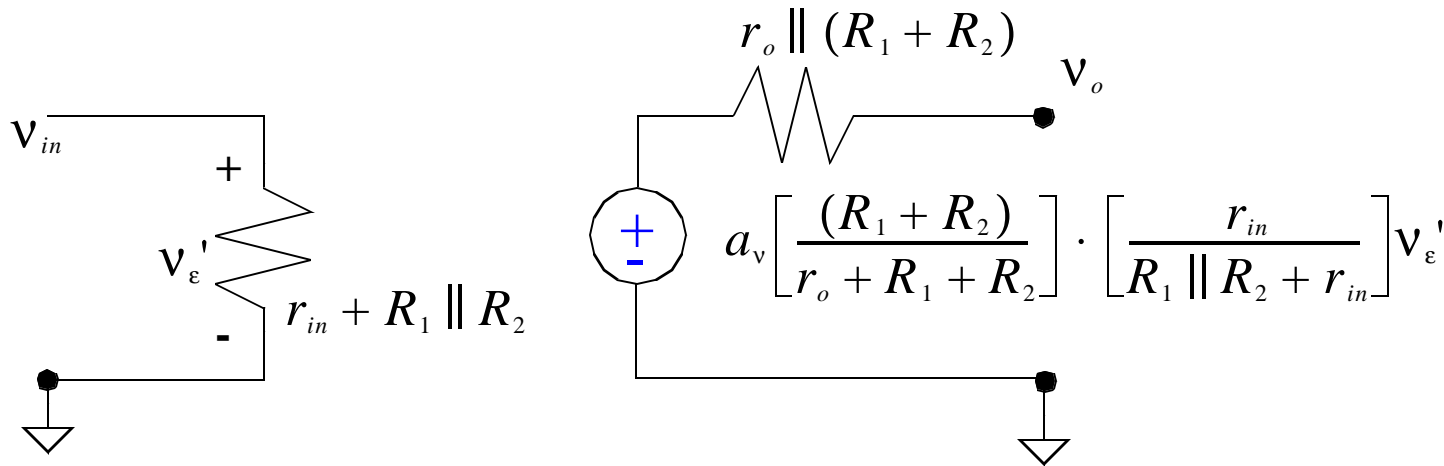

$$a_v' = a_v \left[\frac{(R_1 + R_2)}{r_o + R_1 + R_2} \right] \cdot \left[\frac{r_{in}}{R_1 \parallel R_2 + r_{in}} \right]$$

$$r_{in}' = r_{in} + (R_1 \parallel R_2)$$

$$r_o' = r_o \parallel (R_1 + R_2)$$

Series-Shunt Example (Cont.)

FB-35

$$R_{IN} = (r_{in} + R_1 \parallel R_2) \cdot (1 + T')$$

$$T' \gg 1$$

$$R_{IN} = (r_{in} + R_1 \parallel R_2) \cdot \left(\frac{r_{in} \cdot a_v}{r_{in} + R_1 \parallel R_2} \right) \cdot \left(\frac{R_1 + R_2}{r_o + R_1 + R_2} \right) \cdot \left(\frac{R_1}{R_1 + R_2} \right)$$


$$R_{IN} = r_{in} \cdot T \cdot \left(\frac{R_1 + R_2}{r_o + R_1 + R_2} \right)$$

$$R_{OUT} = \frac{r_o'}{1 + T'} = \frac{\frac{r_o \cdot (R_1 + R_2)}{r_o + R_1 + R_2}}{a_v \cdot \left(\frac{r_{in}}{r_{in} + R_1 \parallel R_2} \right) \cdot \left(\frac{R_1}{r_o + R_1 + R_2} \right)}$$

$$R_{OUT} = \frac{r_o}{T \cdot \left(\frac{r_{in}}{r_{in} + R_1 \parallel R_2} \right)}$$


Shunt-Shunt Example (With Loading)

FB-36

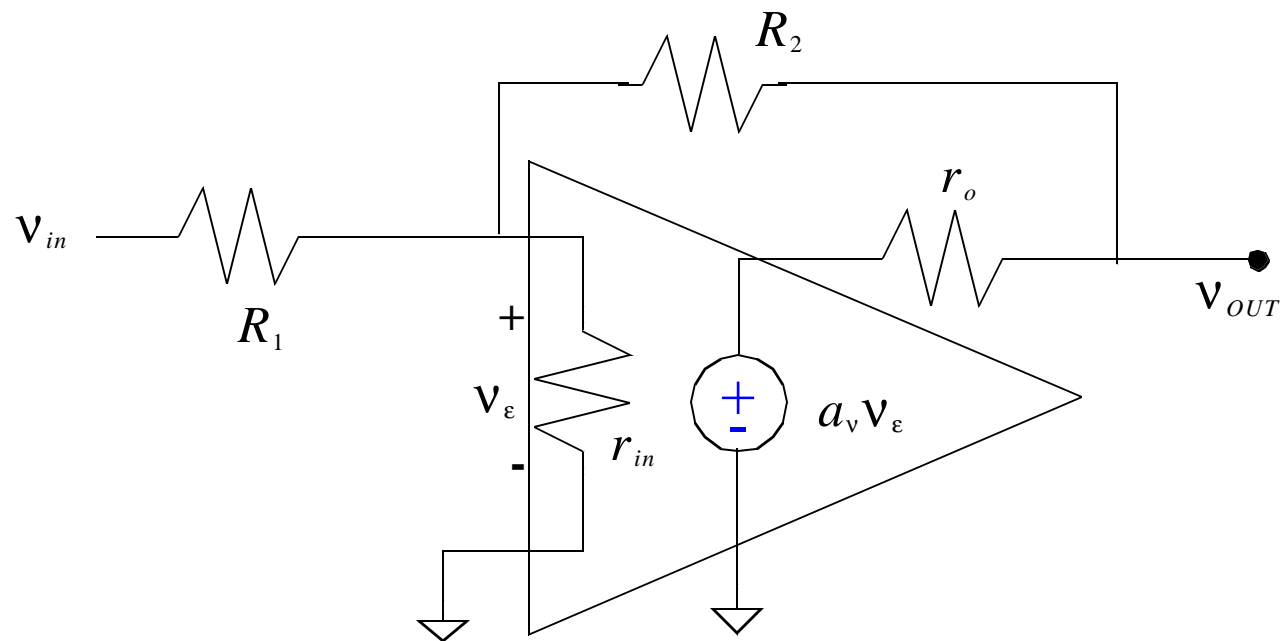

Shunt-Shunt Example (Cont.)


Transforming to current source input :

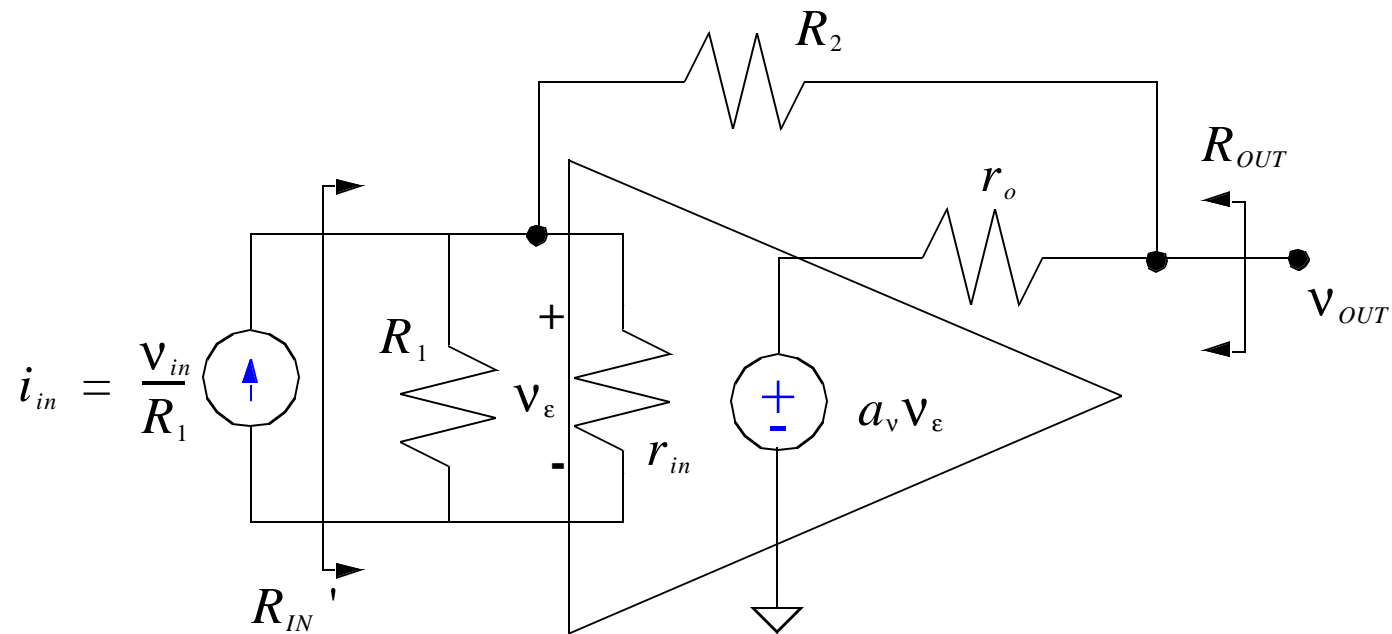

Shunt-Shunt Example (Cont.)


FB-38

Redrawing :

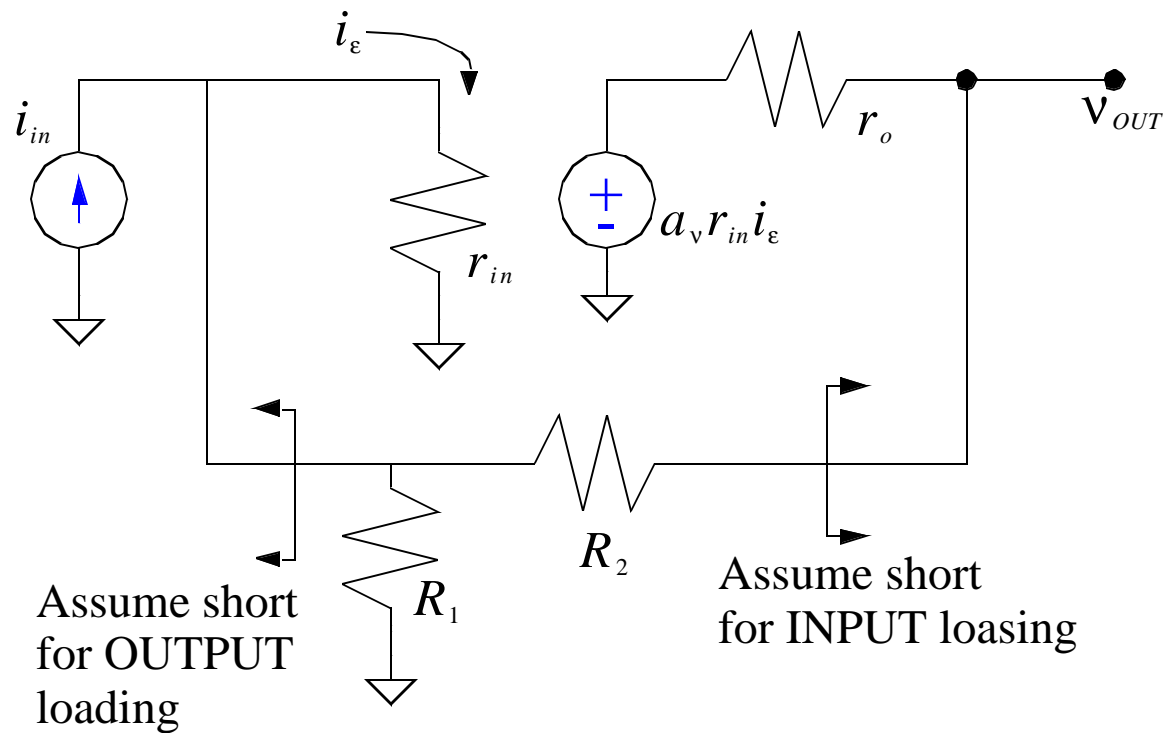

Shunt-Shunt Example (Cont.)

Basic amplifier with loading :

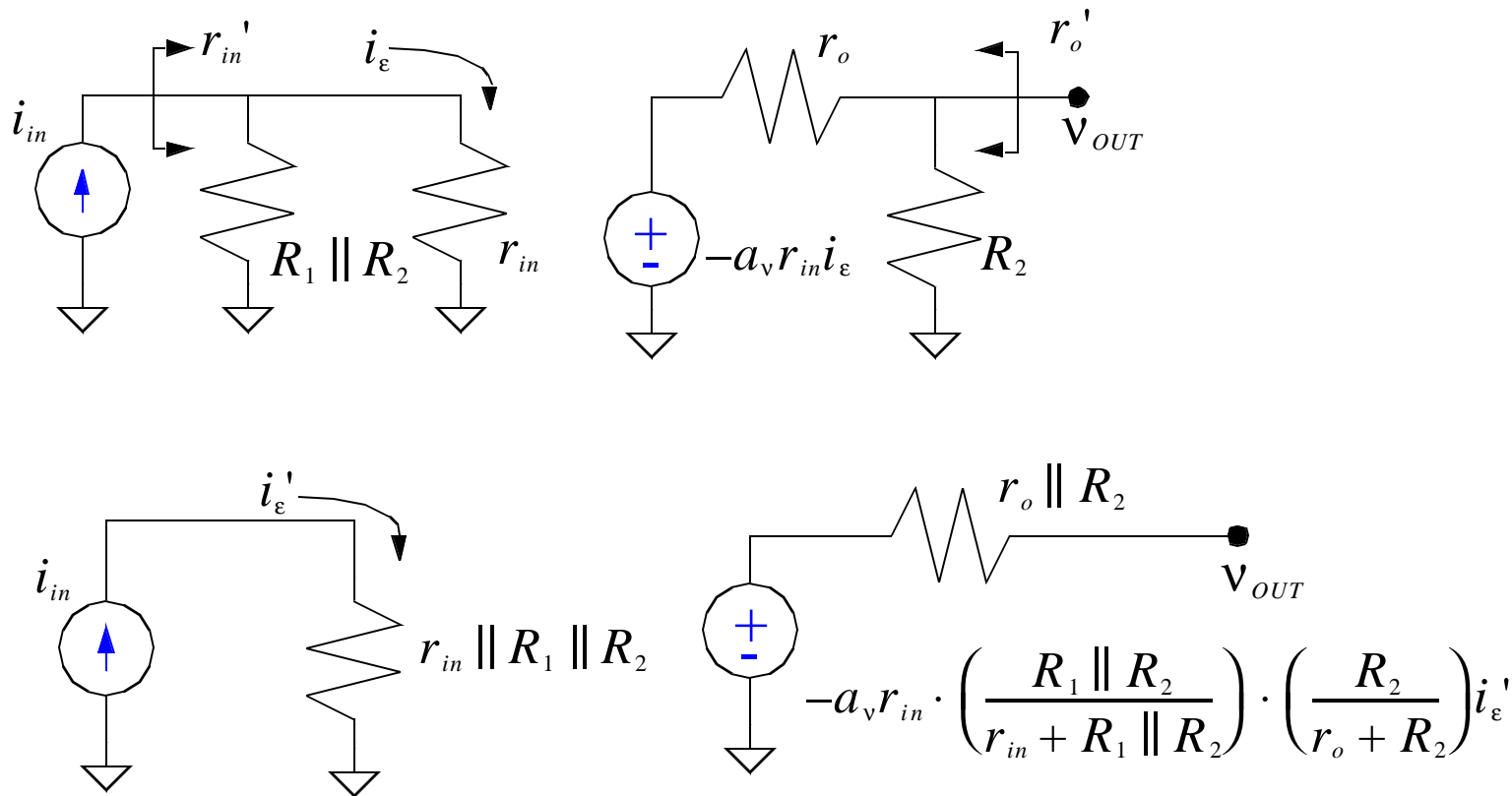


Shunt-Shunt Example (Cont.)

FB-40

$$a_R' = -a_v \cdot r_{in} \cdot \left(\frac{R_1 \parallel R_2}{r_{in} + R_1 \parallel R_2} \right) \cdot \left(\frac{R_2}{r_o + R_2} \right) = -a_v \cdot (r_{in} \parallel R_1 \parallel R_2) \cdot \left(\frac{R_2}{r_o + R_2} \right)$$

$$r_{in}' = r_{in} \parallel R_1 \parallel R_2$$

$$r_{OUT}' = R_2 \parallel r_o$$

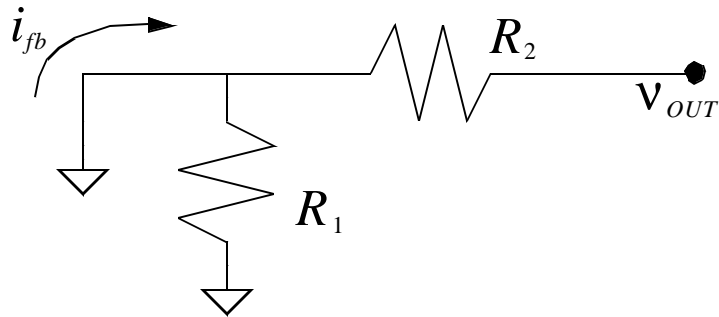

$$f_G = \frac{i_{fb}}{v_{OUT}} = -\frac{1}{R_2}$$

Shunt-Shunt Example (Cont.)

FB-41

Finally we get :

$$\frac{V_{OUT}}{i_{in}} = \frac{1}{f_G} \cdot \left(\frac{T'}{1 + T'} \right)$$

$$T' = a_{R'} \cdot f_G = a_v \cdot \frac{r_{in}}{R_2} \cdot \left(\frac{R_1 \parallel R_2}{r_{in} + R_1 \parallel R_2} \right) \cdot \left(\frac{R_2}{r_o + R_2} \right)$$

$$\frac{V_{OUT}}{V_{in}} = \frac{1}{R_1} \cdot \left(\frac{V_{OUT}}{i_{in}} \right)$$

$$\frac{V_{OUT}}{V_{in}} = \left(\frac{R_2}{R_1} \right) \cdot \left(\frac{T'}{1 + T'} \right)$$

Shunt-Shunt Example (Cont.)

FB-42

$$T' \gg 1$$


$$R_{IN}' = \frac{r_{in}'}{1 + T'} = \frac{r_{in} \parallel R_1 \parallel R_2}{a_v \cdot \frac{r_{in}}{R_2} \cdot \left(\frac{R_1 \parallel R_2}{r_{in} + R_1 \parallel R_2} \right) \cdot \left(\frac{R_2}{r_o + R_2} \right)}$$

$$R_{IN}' = \frac{r_o + R_2}{a_v} \quad \text{independent of } R_1$$

$$R_{IN}'' = R_1 + R_{IN}' \quad \text{at } v_{in}$$

$$R_{OUT} = \frac{r_{OUT}'}{1 + T'} = \frac{R_2 \parallel r_o}{1 + T'} = \frac{r_o}{a_v \cdot f_G \cdot (r_{in} \parallel R_1 \parallel R_2)} = R_{OUT}'$$

FB-43

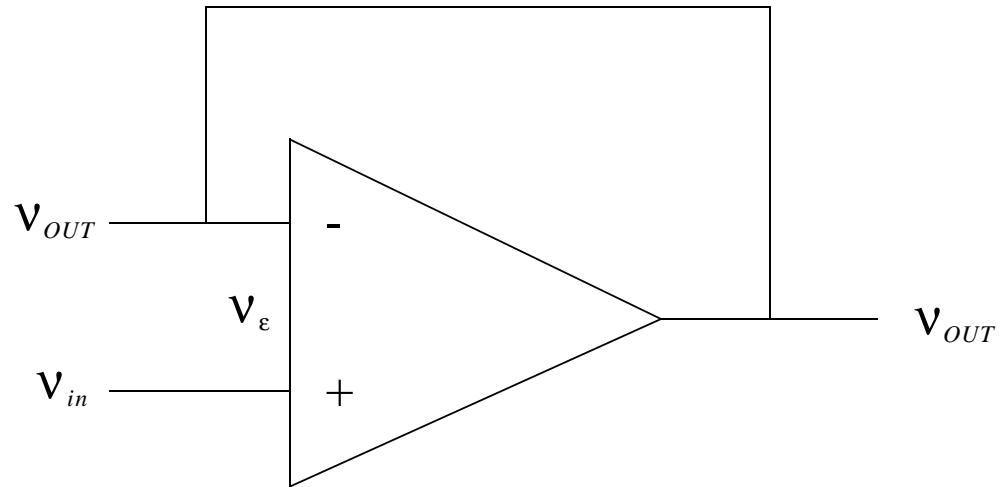


$$V_{\epsilon} = V_{in} - V_{OUT}$$

$$= V_{in} - V_{fb} = V_{in} - f \cdot V_{OUT}$$

$$f = 1$$

Series - Shunt

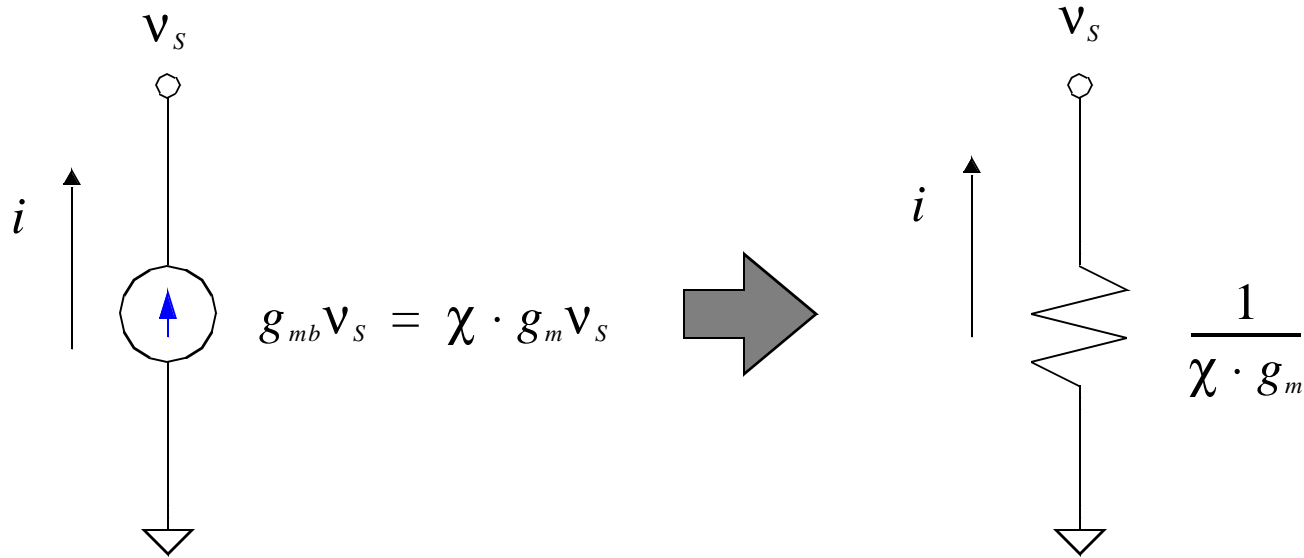Replacing current sources with resistances :






$$i = g_{mb} v_S$$

$$\frac{v_S}{i} = \frac{1}{g_{mb}} = \frac{1}{\chi \cdot g_m}$$

Single Transistor : Series - Shunt

FB-45

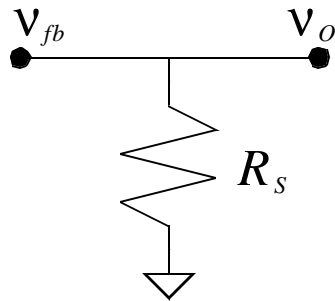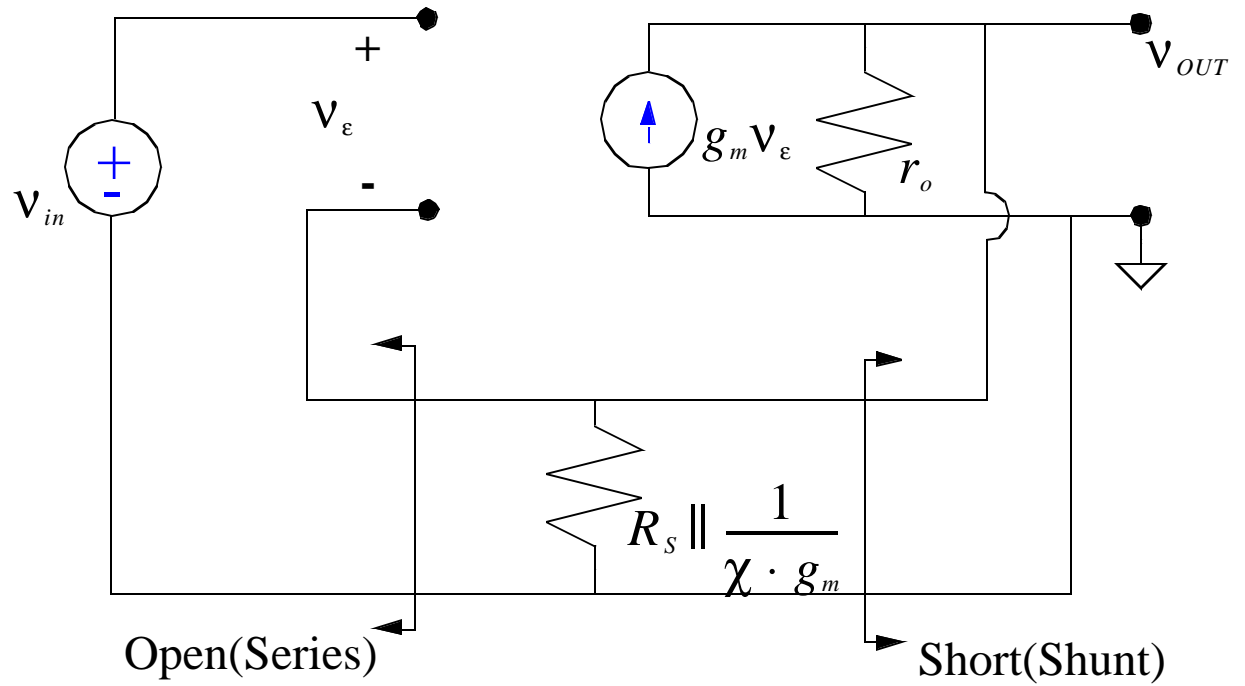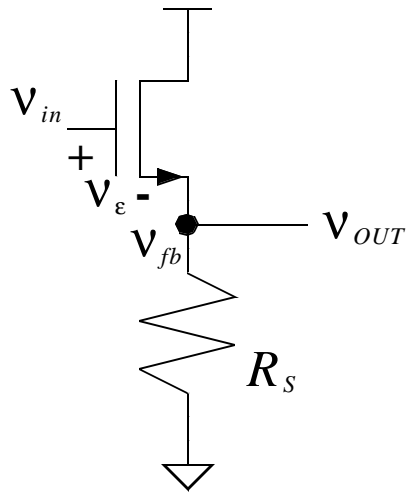


$$f_v = \frac{V_{fb}}{V_o} = 1$$

Single Transistor : Series - Shunt (Cont.)

FB-46

With Loading :

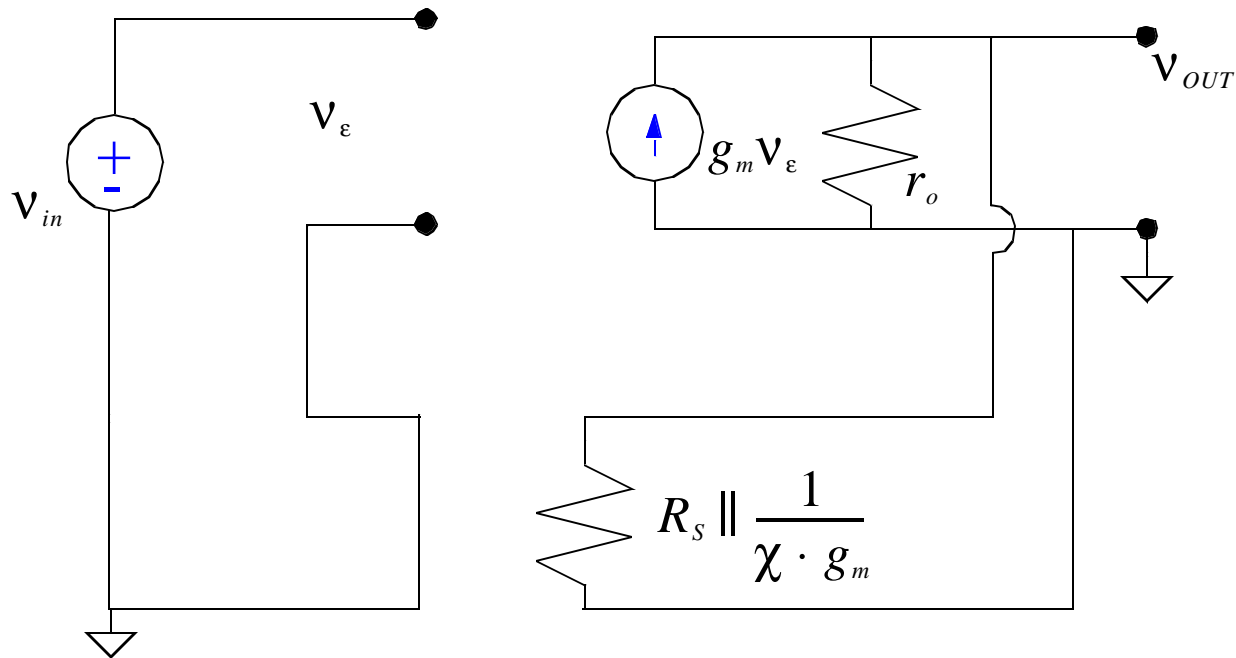

Single Transistor : Series - Shunt (Cont.)

FB-47

$$a_v' = g_m \cdot \left(r_o \parallel R_s \parallel \frac{1}{\chi \cdot g_m} \right) = T' \quad \text{since } f_v = 1$$

$$r_o \gg R_s$$

$$A_v = \frac{1}{f_v} \cdot \frac{T'}{1 + T'} \approx \frac{g_m \cdot \left(R_s \parallel \frac{1}{\chi \cdot g_m} \right)}{1 + g_m \cdot \left(R_s \parallel \frac{1}{\chi \cdot g_m} \right)} = \frac{g_m \cdot R_s}{1 + g_m \cdot R_s \cdot (1 + \chi)} = A_v'$$

$$r_{OUT}' = r_o \parallel R_s \parallel \frac{1}{\chi \cdot g_m} \approx R_s \parallel \frac{1}{\chi \cdot g_m}$$


$$r_{in}' = \infty$$

$$R_{OUT} = \frac{r_{OUT}'}{1 + T'} = \frac{R_s \parallel \frac{1}{\chi \cdot g_m}}{1 + g_m \cdot \left(R_s \parallel \frac{1}{\chi \cdot g_m} \right)} = \frac{R_s}{1 + g_m \cdot (1 + \chi) \cdot R_s}$$


$$= R_s \parallel \frac{1}{g_m \cdot (1 + \chi)} = R_{OUT}$$

Series - Series with Degeneration

FB-48





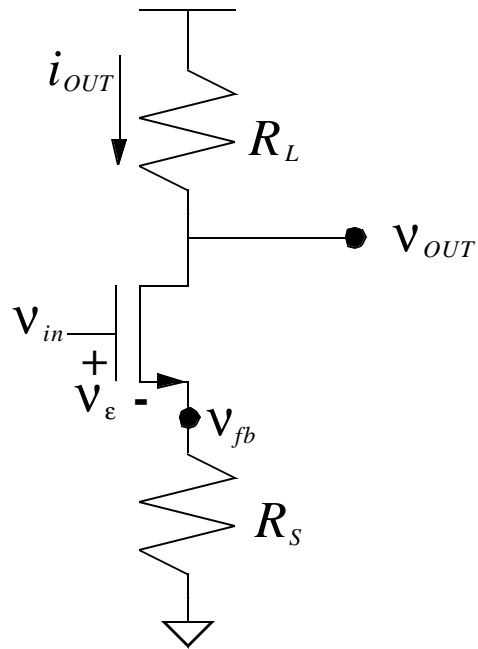


For Simplicity, $\chi = 0$

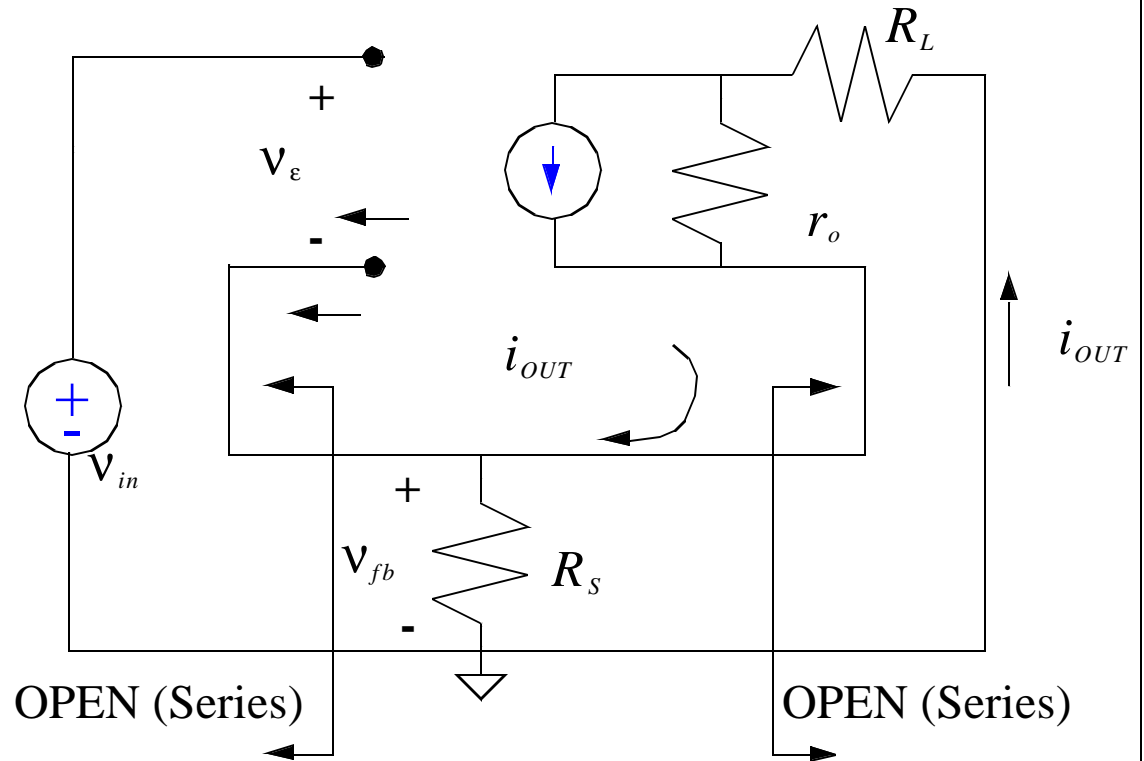

Series - Series Degeneration (Cont.)

FB-49

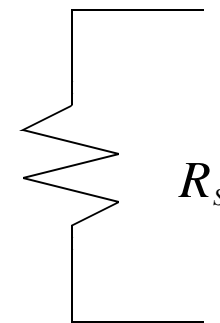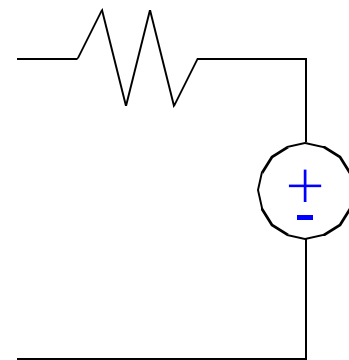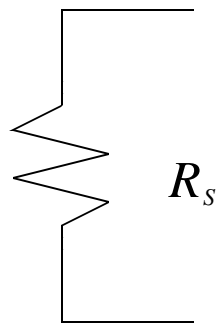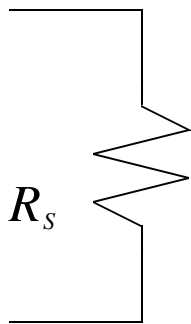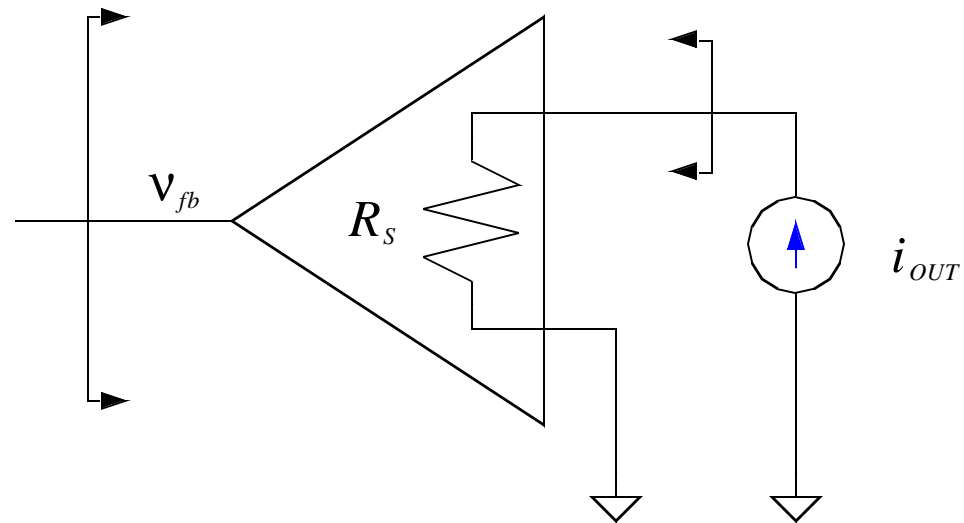


$$v_{fb} = i_{OUT} R_s$$


Series - Series Degeneration (Cont.)

FB-50

Basic amplifier with loading :

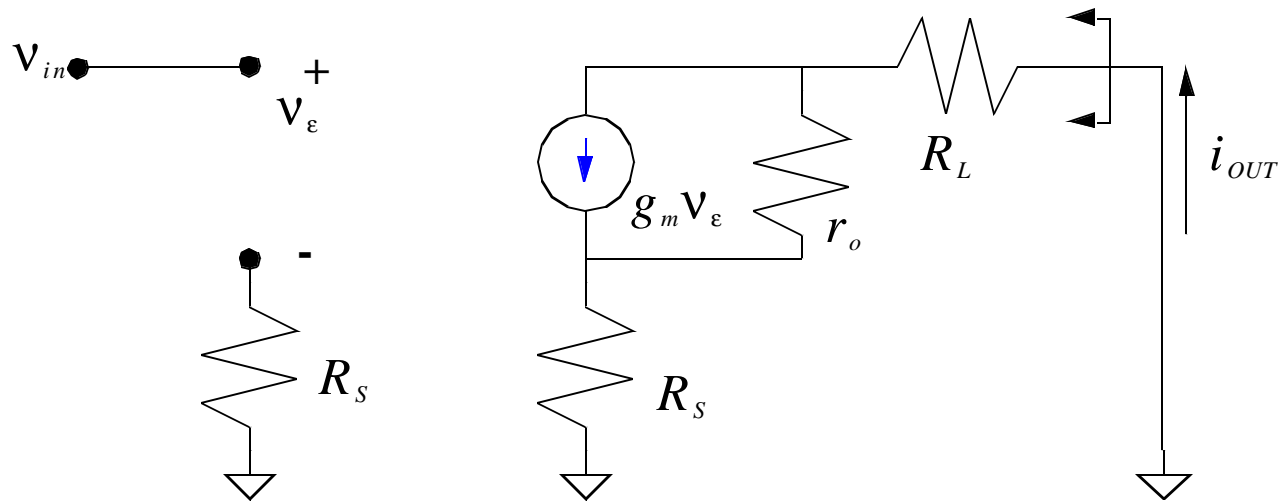


Redrawn :

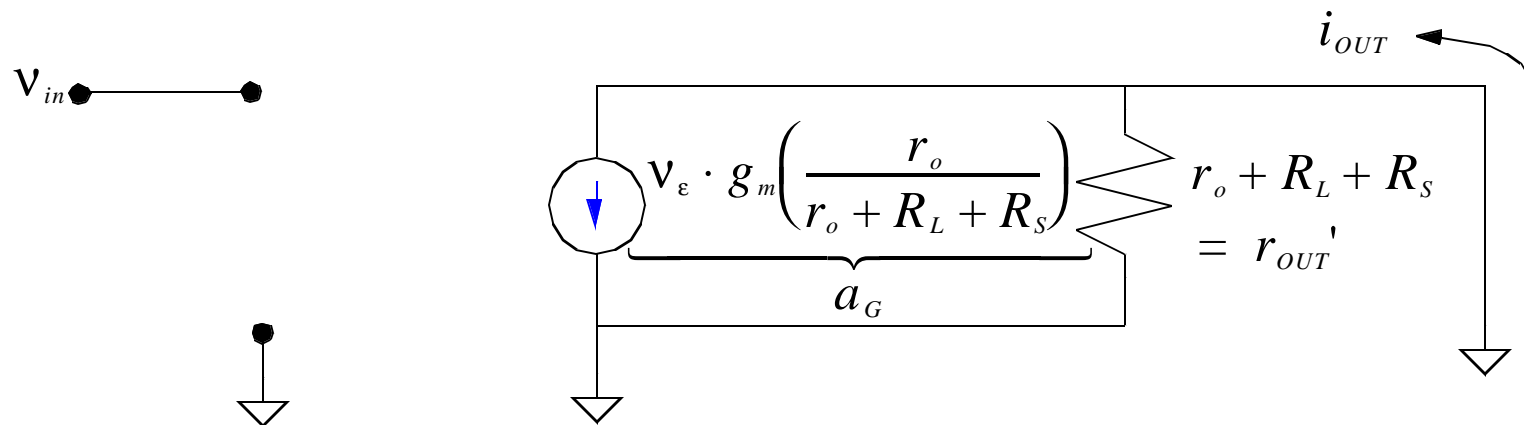

Series - Series Degeneration (Cont.)

FB-51

Feedback Network :

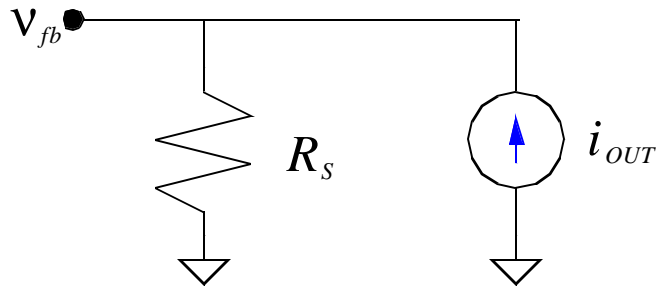

$$f_R = \frac{v_{fb}}{i_{OUT}} = R_s$$

$$T' = a_G \cdot f_G = g_m \cdot \left(\frac{r_o}{r_o + R_L + R_s} \right) \cdot R_s$$

$$\begin{aligned} R_{OUT}' &= r_{OUT}' \cdot (1 + T') = (r_o + R_L + R_s) \cdot \left(1 + g_m \cdot \frac{r_o \cdot R_s}{r_o + R_L + R_s} \right) \\ &= r_o + R_L + R_s + g_m \cdot r_o \cdot R_s = R_L + R_s + (1 + g_m \cdot R_s) \cdot r_o \end{aligned}$$

Series - Series Degeneration (Cont.)

FB-52

$$G_M = \frac{i_{OUT}}{v_{in}} = \frac{1}{f_R} \cdot \frac{T'}{1 + T'}$$


$$= \left(\frac{1}{R_S} \cdot \frac{g_m \cdot \frac{r_o \cdot R_S}{r_o + R_L + R_S}}{1 + \frac{g_m \cdot r_o \cdot R_S}{r_o + R_L + R_S}} = \frac{g_m \cdot r_o}{r_o + R_L + R_S + g_m \cdot r_o \cdot R_S} \right)$$

$$G_M = \frac{g_m \cdot r_o}{R_L + R_S + r_o \cdot (1 + g_m \cdot R_S)} \approx \frac{g_m}{(1 + g_m \cdot R_S)}$$

$$r_o \gg R_L, R_S$$


FB-53

Shunt - Shunt

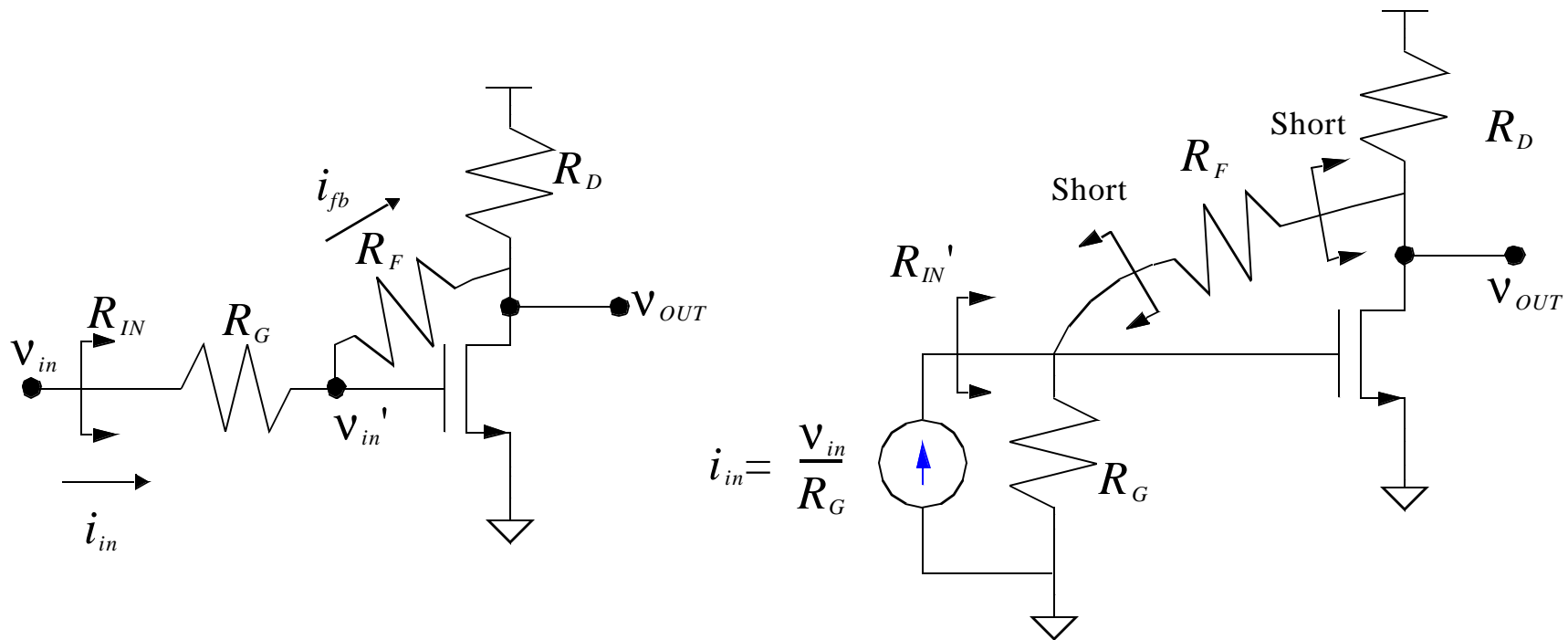

Shunt - Shunt (Cont.)

Basic amp with loading :

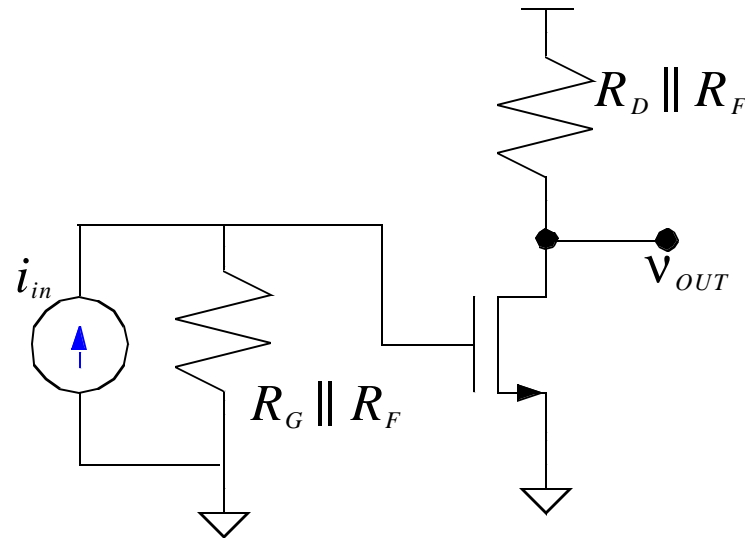


$$V_{OUT} = -i_{in} \cdot (R_G \parallel R_F) \cdot g_m \cdot (R_D \parallel R_F \parallel r_o)$$

$$a_R' = \frac{V_{OUT}}{i_{in}} = -(R_G \parallel R_F) \cdot g_m \cdot (R_D \parallel R_F \parallel r_o)$$

$$r_{in}' = R_G \parallel R_F \quad r_{OUT}' = R_D \parallel R_F$$

Shunt - Shunt (Cont.)

FB-55

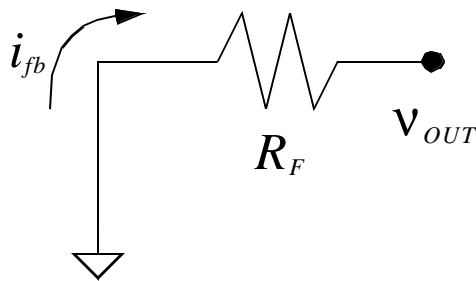

$$f_G = \frac{v_{OUT}}{i_{fb}} = -\frac{1}{R_F}$$

$$T' = a_R \cdot f_G = \frac{1}{R_F} \cdot (R_G \parallel R_F) \cdot g_m \cdot (R_D \parallel R_F \parallel r_o)$$

$$T' \gg 1$$

$$R_{IN}' = \frac{r_{in}'}{1 + T'} = \frac{R_G \parallel R_F}{\frac{1}{R_F} \cdot (R_G \parallel R_F) \cdot g_m \cdot (R_D \parallel R_F \parallel r_o)}$$

$$= \frac{R_F}{g_m \cdot (R_D \parallel R_F \parallel r_o)} \approx \frac{R_F}{a_v}$$

Shunt - Shunt (Cont.)

$$\text{At } v_{in} \quad a_v = \frac{v_{OUT}}{v_{in}'}$$

$$R_{IN} = R_G + R_{IN}' = R_G + \frac{R_F}{a_v} \approx R_G$$

$$T' \gg 1$$

$$R_{OUT} = \frac{r_{OUT}'}{1 + T'} = \frac{(R_D \parallel R_F \parallel r_o)}{\frac{1}{R_F} \cdot (R_G \parallel R_F) \cdot g_m \cdot (R_D \parallel R_F \parallel r_o)}$$

$$= \frac{1}{g_m \cdot \left(\frac{R_G}{R_F + R_G} \right)}$$